


Name _____ Box _____

Due date: Tues. March 6

EC130-02/03 Homework #1 (Switching circuit)

Spring 2001

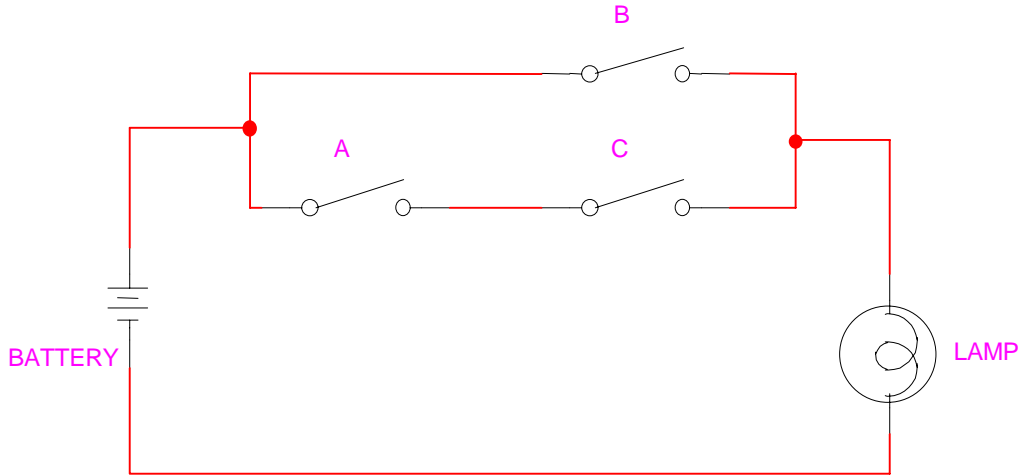1. Fill in the logic function table for the circuit below. The switches have two states: open and closed. The lamp has two states: off and on.



A	B	C	LAMP
Open	Open	Open	Off