

- 1 Design a combinational circuit whose inputs are two 4-bit unsigned binary integers, X and Y, and a control signal MIN/MAX. The output of the circuit is a 4-bit unsigned binary integer Z such that $Z=0$ if $X=Y$; otherwise, $Z=\min(X,Y)$ if $\text{MIN/MAX}=1$, and $Z=\max(X,Y)$ if $\text{MIN/MAX}=0$.

Use a 74LS85 and a 74LS157 and necessary gates to implement your design on LogicWorks 4. Use buses to connect data lines. Use hex keypads and hex display to verify your design.

Connect input pins A>Bin and A<Bin to “0” and A=B to “1”.

Submit a paper copy of your solution and also email your solution to Jianjian.song@rose-hulman.edu. Your solution should contain your LogicWorks 4 schematic and your design procedure and explanation.

The following circuit was discussed in class and its LogicWork file is sent to you by email.

