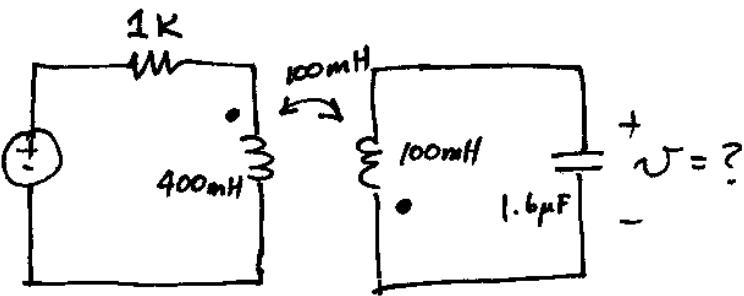



Example 1

$$5 \cos(2500t - 30^\circ) V$$




\* Convert to phasor circuit:
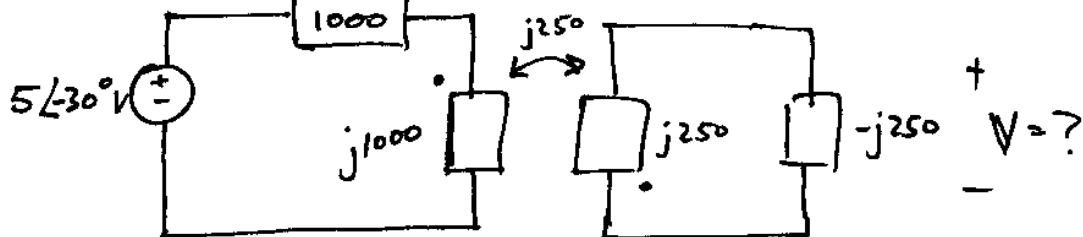
$$\begin{aligned} 400 \text{ mH} @ \omega = 2,500 \text{ rad/s} &\rightarrow j1000\Omega \\ 100 \text{ mH} &\rightarrow j250\Omega \\ 1.6 \mu\text{F} &\rightarrow -j250\Omega \end{aligned}$$



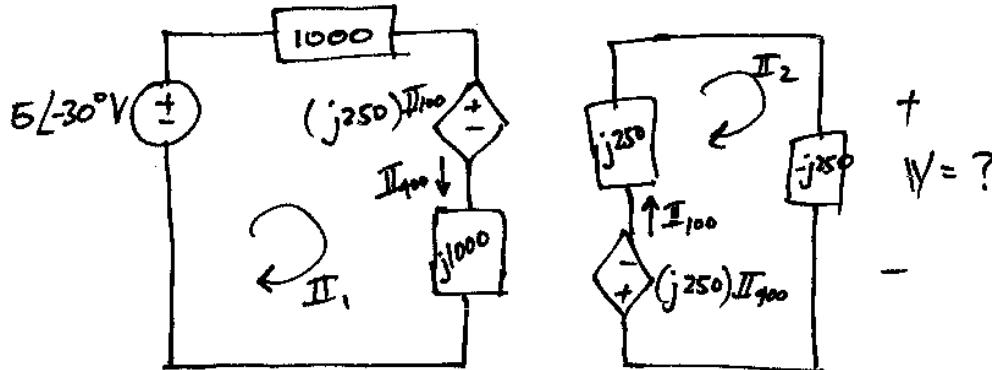\* Insert circuit model for coupled coils:



\* Use mesh analysis:

$$\text{Mesh 1: } -5 \angle -30^\circ + 1000\text{II}_1 + j250\text{II}_{100} + j1000\text{II}_2 = 0$$

$$\text{Mesh 2: } j250\text{II}_{100} + j250\text{II}_2 - j250\text{II}_1 = 0$$


$$\text{Control currents: } \text{II}_{100} = \text{II}_1 \text{, } \& \text{ II}_{100} = \text{II}_2$$

\* Solve system:

$$\text{II}_1 = 0 \quad \& \quad \text{II}_2 = 20 \angle -120^\circ \text{ mA}$$

$$\text{* Solve for V: } V = -j250\text{II}_2 = 5 \angle -210^\circ \text{ V}$$

$$\begin{aligned} \mathcal{S}(t) &= \\ 5 \cos(2500t - 210^\circ) & \end{aligned}$$

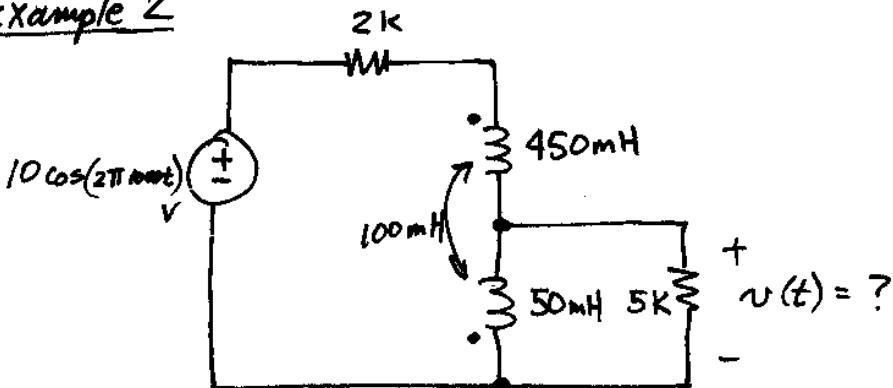
Example 2

\* Convert to phasor circuit:

$$450\text{mH} @ \omega = 2\pi/1000 \text{ rad/s} \rightarrow j2.83\text{k}$$

$$100\text{mH} @ " \rightarrow j628\text{\Omega}$$
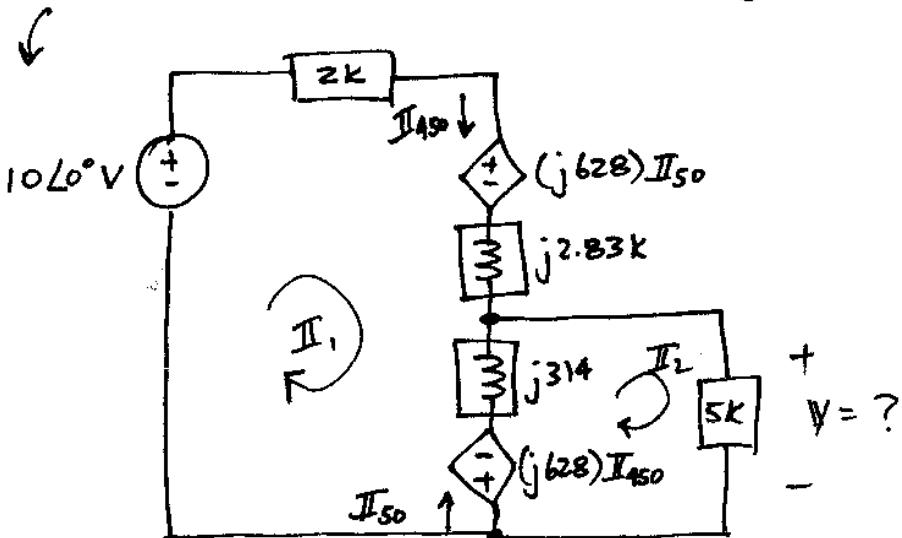
$$50\text{mH} @ " \rightarrow j314\text{\Omega}$$



\* Use mesh analysis (usually the better choice, since the dependent sources introduce more nodes)

$$\begin{aligned} \text{Mesh 1: } & -10 + 2000I_1 + j628I_{450} + (j2.83k)I_1 \\ & + j314(I_1 - I_2) - (j628)I_{450} = 0 \end{aligned}$$

$$\text{Mesh 2: } j628(I_2 - I_1) + j314(I_2 - I_1) + 5000I_2 = 0$$

$$\text{Control currents: } I_{450} = I_1 \quad \therefore I_{50} = I_2 - I_1$$

\* Solve system for  $I_1$ ,  $I_2$ , then  $V = 5000I_2$ . Convert  $V$  to  $v(t)$ . (see next page)

## Example 2, cont'd :

Equations from mesh current analysis, involving the initial conditions:

> restart:

Digits := 4:

alias(I=I, j=sqrt(-1)):

eqs := {

-10 + 2000\*I1 + j\*628\*I50 + j\*2.83E3\*I1 + j\*314\*(I1-I2) -  
j\*628\*I450,  
j\*628\*(I2-I1) + j\*314\*(I2-I1) + 5000\*I2,  
I450 = I1,  
I50 = I2 - I1  
};

eqs := { $I_{450} = II$ ,  $-10 + 2000 II + 628j I_{50} + 2830.j II + 314j(II - I2) - 628j I_{450}$ ,  
 $I_{50} = I2 - II$ ,  $942j(I2 - II) + 5000 I2$ }

Solve the system of equations:

> soln := solve(eqss);

soln := { $I_{50} = -.002074 + .002964j$ ,  $I_{450} = .002633 - .002573j$ ,  $I2 = .0005583 + .0003908j$ ,  
 $II = .002633 - .002573j$ }

> assign(soln);


Display the voltage of interest:

> V := 5000\*I2;


$$V := 2.792 + 1.954j$$

$$= 3.40 \angle 35^\circ V$$

$$\Rightarrow V(t) = 3.40 \cos(2\pi \cdot 1000t + 35^\circ) V$$

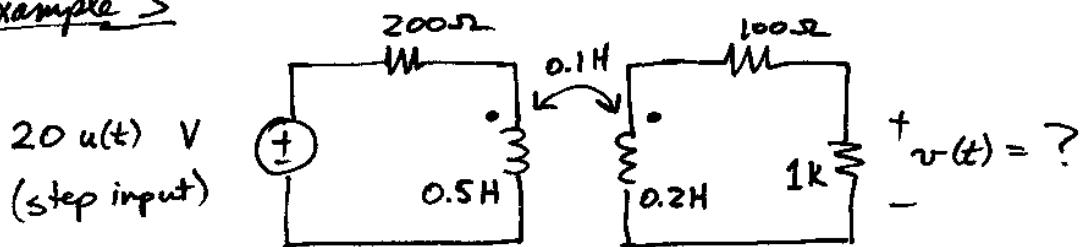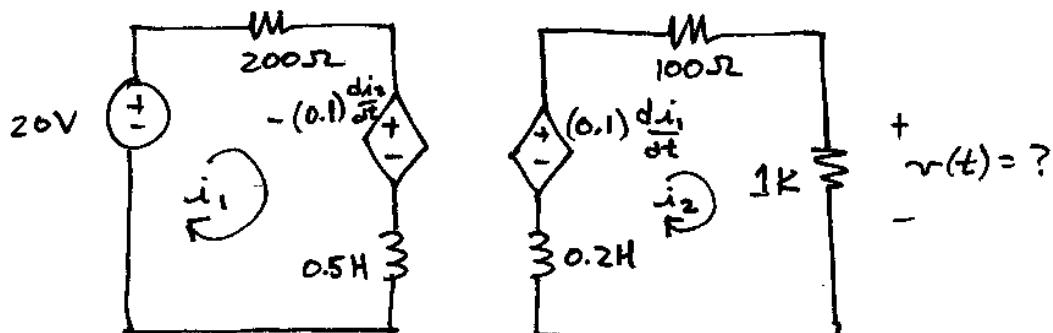Example 3

\* Circuit for  $t \geq 0$  (initial conditions are all zero):



\* Mesh analysis:

$$\text{Mesh 1: } -20 + 200i_1 - 0.1 \frac{di_2}{dt} + 0.5 \frac{di_1}{dt} = 0$$

$$\text{Mesh 2: } 0.2 \frac{di_2}{dt} - 0.1 \frac{di_1}{dt} + 100i_2 + 1000i_2 = 0$$

$$\text{Initial conditions: } i_1(0) = 0, i_2(0) = 0$$

\* Solve the system for  $i_1(t)$ ,  $i_2(t)$ , & find  $v(t) = 1000i_2(t)$ :

$$v(t) = 3.90 e^{-397t} - 3.90 e^{-6159t} \quad \checkmark$$

(See next page for Maple worksheet)

## Worksheet for Example 3

Equations from mesh current analysis, including the initial conditions:

```
> restart:  
Digits := 4:  
eqs := {  
-20 + 200*i1(t) - 0.1*diff(i2(t),t) + 0.5*diff(i1(t),t),  
0.2*diff(i2(t),t) - 0.1*diff(i1(t),t) + 1100*i2(t),  
i1(0) = 0,  
i2(0) = 0  
};  
  
eqs := { -20 + 200 i1(t) - .1  $\left(\frac{\partial}{\partial t} i2(t)\right)$  + .5  $\left(\frac{\partial}{\partial t} i1(t)\right)$ , .2  $\left(\frac{\partial}{\partial t} i2(t)\right)$  - .1  $\left(\frac{\partial}{\partial t} i1(t)\right)$  + 1100 i2(t),  
i1(0)=0, i2(0)=0 }
```

Mesh current names:

```
> currents := {i1(t),i2(t)};  
currents := {i1(t),i2(t)}
```

Solve the system of differential equations:

```
> soln := dsolve(eqns, currents, method=laplace);  
soln := {i1(t) = .1000 - .1000 e(-3278. t) cosh(2881. t) - .09838 e(-3278. t) sinh(2881. t),  
i2(t) = .007717 e(-3278. t) sinh(2881. t)}
```

```
> assign(soln);
```

Display the voltage of interest:

```
> v(t) := 1000*i2(t);  
v(t) := 7.717 e(-3278. t) sinh(2881. t)
```

Show in a simpler form (eliminate the hyperbolic terms):

```
> v(t) := simplify(expand(convert(v(t), exp)));  
v(t) := 3.859 e(-397. t) - 3.859 e(-6159. t)
```

Plot the voltage vs. time:

```
> plot(v(t), t=0..5E-3);
```

