

$$(2.1) \quad \#1: \frac{V_1 - V_2}{R_1} + \frac{V_1 - V_3}{R_2} + \frac{V_1}{R_3} = 0$$

$$\#2 \& \#4: \begin{cases} \frac{V_2 - V_1}{R_1} + \frac{V_2 - V_3}{R_5} + \frac{V_4 - V_3}{R_4} - I_2 = 0 \\ V_2 - V_4 = V_A \end{cases}$$

$$\#3: \frac{V_3 - V_1}{R_2} + \frac{V_3 - V_2}{R_5} + \frac{V_3 - V_4}{R_4} - I_1 = 0$$

(2.2)


$$\#1: R_1 I_1 + R_2 (I_1 - I_2) + V_A + R_3 I_1 = 0$$

$$\#2: R_4 I_2 + V_B + R_2 (I_2 - I_1) = 0$$

$$\#3: -V_A - V_B + R_6 (I_3 - I_4) + R_5 I_3 = 0$$

$$\#4: I_4 = I_A$$

(3.1) (a)

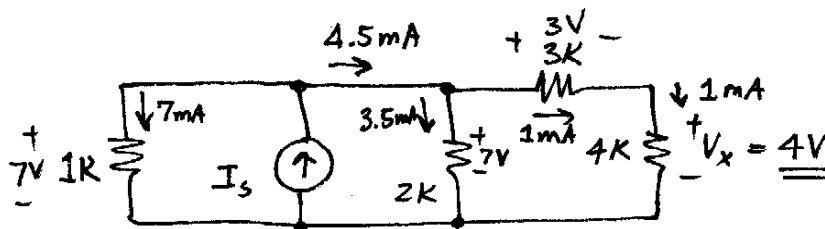


$$I_s = 7 + 4.5 = 11.5 \text{ mA}$$

$$K = \frac{V_x}{I_s} = \frac{4 \text{ V}}{11.5 \text{ mA}} = 348 \Omega$$


$$(b) \quad \boxed{V_x = K I_s = 348 (50 \text{ mA}) = 17.4 \text{ V}}$$

3.2

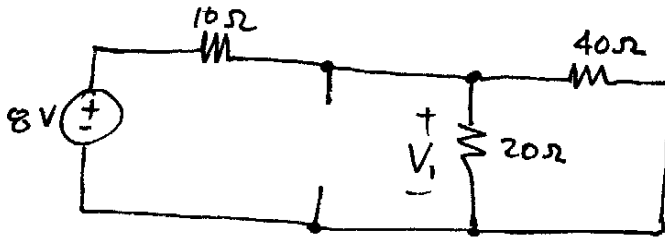


$$V_1 = \frac{20 \parallel 40}{20 \parallel 40 + 10} 8 = \underline{4.57V}$$

→

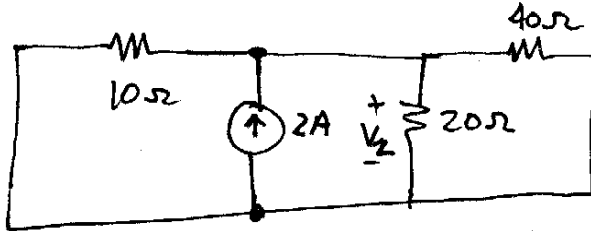

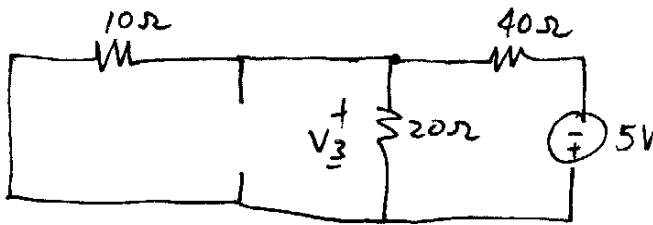
$$\begin{aligned} V_2 &= 2(10 \parallel 20 \parallel 40) \\ &= 2(5.71) \\ &= \underline{11.4V} \end{aligned}$$




$$\begin{aligned} V_3 &= -\frac{20 \parallel 10}{20 \parallel 10 + 40} 5 \\ &= \underline{-0.714V} \end{aligned}$$

$$V = V_1 + V_2 + V_3 = 15.3V$$

4.1

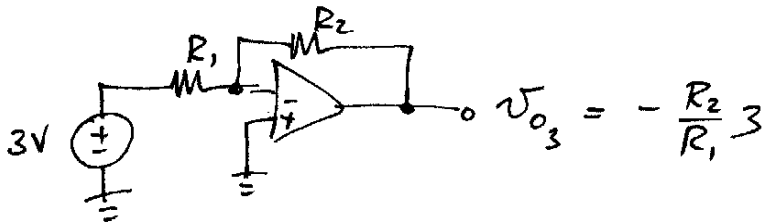

$$V_{0_3} = -\frac{R_2}{R_1} 3$$

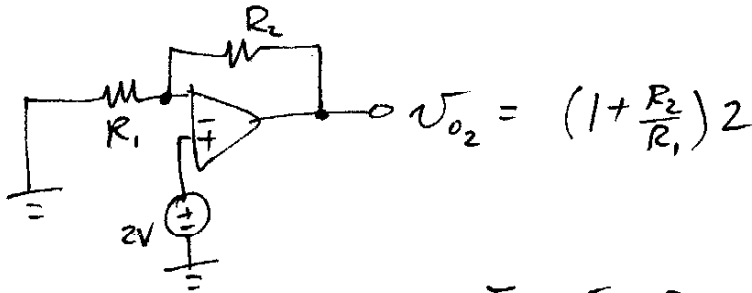


$$V_{0_2} = \left(1 + \frac{R_2}{R_1}\right) 2$$

$$V_0 = V_{0_3} + V_{0_2} = -\frac{R_2}{R_1} 3 + 2 + \frac{R_2}{R_1} 2$$

$$V_0 = 2 - \frac{R_2}{R_1}$$



4.2 Circuit model:

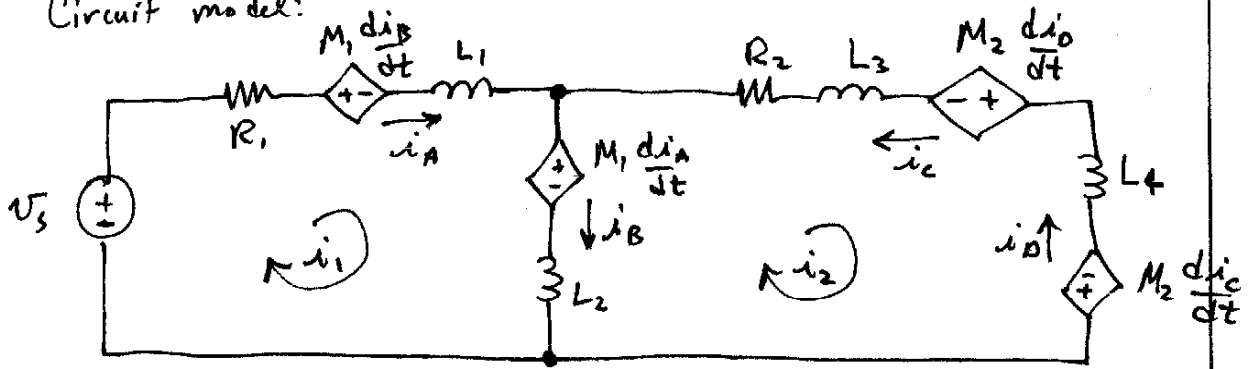

$$\#1: -v_s + R_1 i_1 + M_1 \frac{di_B}{dt} + L_1 \frac{di_1}{dt} + M_1 \frac{di_A}{dt} + L_2 \frac{d(i_1 - i_2)}{dt} = 0$$

$$\#2: L_2 \frac{d(i_2 - i_1)}{dt} - M_1 \frac{di_A}{dt} + R_2 i_2 + L_3 \frac{di_2}{dt} - M_2 \frac{di_D}{dt} + L_4 \frac{di_2}{dt} - M_2 \frac{di_C}{dt} = 0$$

Control

Currents:


$$i_A = i_1$$

$$i_B = i_1 - i_2$$

$$i_C = -i_2$$

$$i_D = -i_2$$

5.1

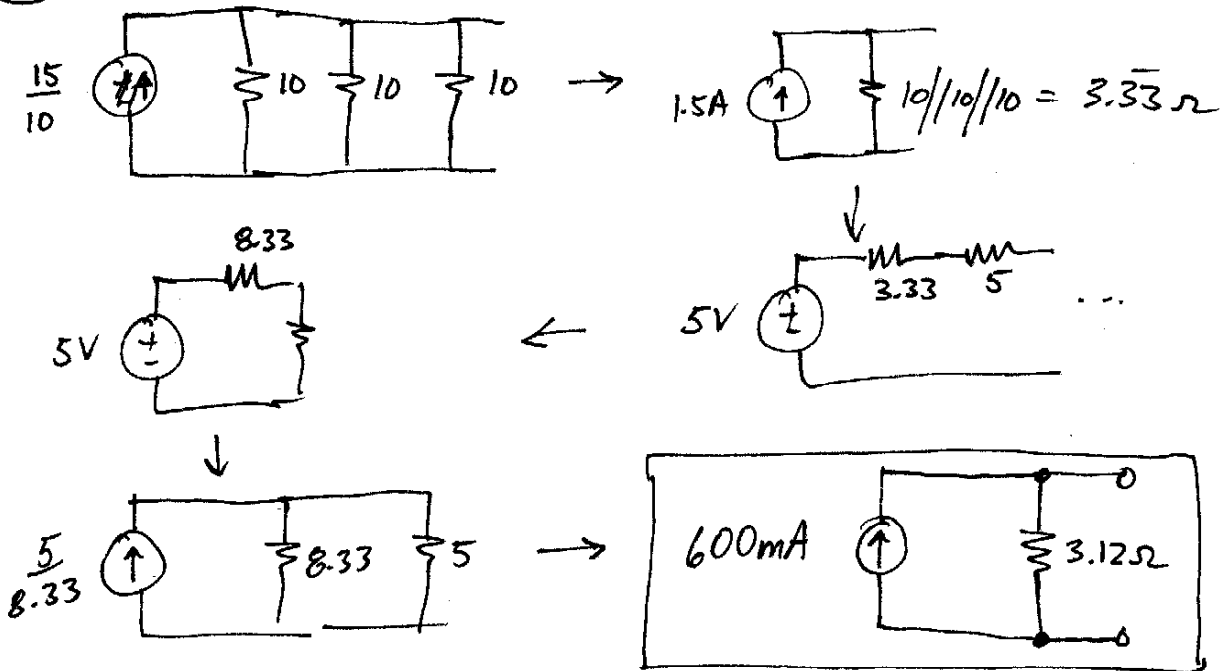


5.2

$$V_{oc} = 200 \text{ V} , I_{sc} = 4 \text{ A}$$
$$\text{" } V_T \quad \text{" } I_N$$

Since $V_{oc} = R_T I_{sc}$, $R_T = \frac{V_{oc}}{I_{sc}} = \frac{200}{4} = 50 \Omega$
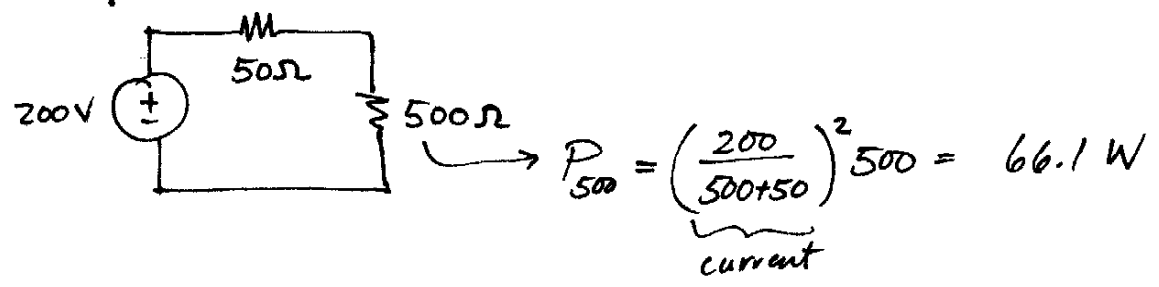
$$P_{max} = \frac{V_T^2}{4 R_T} = \frac{200^2}{4 \cdot 50} = 200 \text{ W}$$



$$\frac{P_{500}}{P_{max}} \times 100\% = \frac{66.1}{200} \times 100\% = \boxed{33\%}$$

22-103 50 SHEETS
22-102 100 SHEETS
22-100 200 SHEETS

