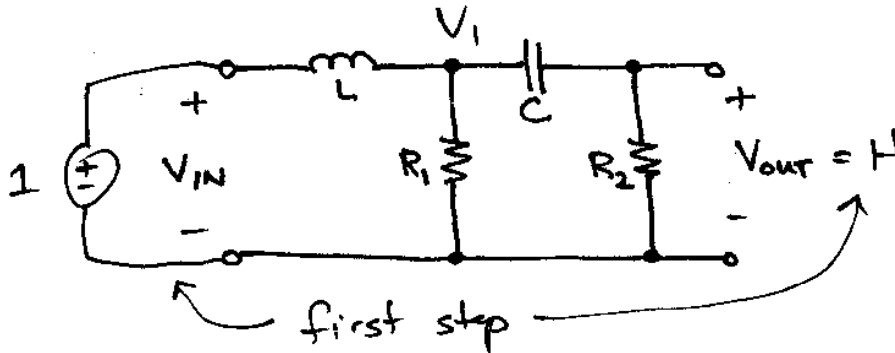


- ① Find the voltage transfer function  $H(s) = \frac{V_{out}}{V_{in}}$ . (See below)  
 Express your result as a ratio of two polynomials in  $s$ , with a unity coefficient on the highest order denominator term.



Nodal analysis (can use other techniques, too):

$$\left. \begin{aligned} \frac{V_1 - 1}{Ls} + \frac{V_1}{R_1} + \frac{V_1 - H}{1/cs} = 0 \end{aligned} \right\} \begin{array}{l} \text{SOLVE} \\ \rightarrow \end{array}$$

$$\frac{H - V_1}{1/cs} + \frac{H}{R_2} = 0$$

$$\Rightarrow H(s) = \frac{R_1 C s R_2}{\underbrace{R_1 C s R_2 + R_1 + L s^2 C R_2 + L s + C s^2 L R_1}_{\text{combine}}}$$

$$= \frac{R_1 R_2 C s}{s^2 (L C R_2 + L C R_1) + s (R_1 R_2 C + L) + R_1}$$

$$H(s) = \frac{R_1 R_2 C}{L C R_2 + L C R_1} s$$

$$s^2 + \frac{R_1 R_2 C + L}{L C R_2 + L C R_1} s + \frac{R_1}{L C R_1 + L C R_2}$$

$$\frac{R_1 R_2}{L} s = \frac{R_1 R_2}{L} s + \frac{1}{L C (R_1 + R_2)} s + \frac{1}{L C (R_1 + R_2)}$$

~~Handwritten scribbles~~

22-141 50 SHEETS  
 22-142 100 SHEETS  
 22-144 200 SHEETS



② Plot the pole-zero diagram for the impedance function  $Z(s)$ :

$$\frac{16s^3 + 64s^2 + 128s}{s^4 + 10s^3 + 29s^2 + 40s + 100} = Z(s)$$

→ Factor the numerator:  $16(s+2+j2)(s+2-j2)s$

\* Factor the denominator:  $(s+5)^2(s+j2)(s-j2)$

