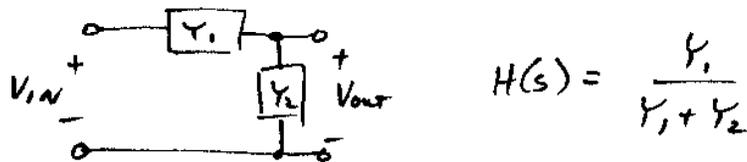


- ① Design a passive circuit (no opamps) based on a single capacitor of size 10nF (\neq resistors as needed) that implements $H(s) = \frac{s+4,000}{s+10,000}$.

* Start with voltage divider expressed as admittances:



* Choose parallel RC for Y_1 , which then requires a resistor for Y_2 :

$$H(s) = \frac{C_1 s + \frac{1}{R_1}}{(C_1 s + \frac{1}{R_1}) + \frac{1}{R_2}}$$

* Match terms to specified function after converting to same form:

$$H(s) = \frac{C_1 s + \frac{1}{R_1}}{C_1 s + \frac{1}{R_1} + \frac{1}{R_2}} = \frac{s + \frac{1}{R_1 C_1}}{s + (\frac{1}{R_1 C_1} + \frac{1}{R_2 C_1})} = \frac{s + 4,000}{s + 10,000}$$


$$\Rightarrow \frac{1}{R_1 C_1} = 4000 \quad ; \quad \frac{1}{R_1 C_1} + \frac{1}{R_2 C_1} = 10,000$$

* Choose component values (C_1 already specified as 10nF):

$$R_1 = \frac{1}{4000 C_1} = \frac{1}{(4000)(10\text{E-}9)} = 25\text{K}$$

$$R_2 = \left[\underbrace{\left(10,000 - \frac{1}{R_1 C_1}\right)}_{6,000} C_1 \right]^{-1} = 16.7\text{K}$$

* Finished design:

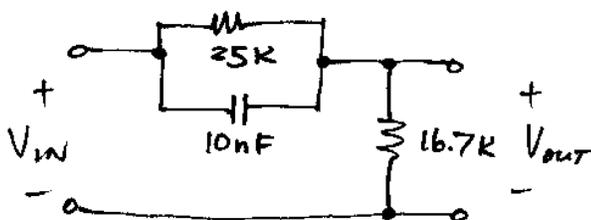

OVER



② Plot the frequency response (one plot for magnitude, another plot for phase) of the two systems below. Include some specific values to calibrate your graphs.

(a) A differentiator, with transfer function $H_1(s) = s$

(b) An integrator, with transfer function $H_2(s) = \frac{1}{s}$

* Part (a):

$$H_1(s) \Big|_{s=j\omega} = \underbrace{j\omega}_{\text{freq. response } H_1(j\omega)} \quad |H_1(j\omega)| = \omega, \quad \angle H_1(j\omega) = +90^\circ$$

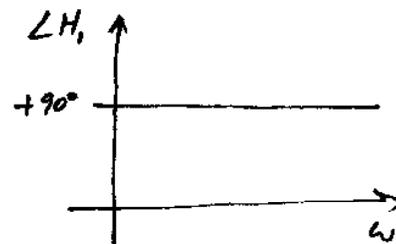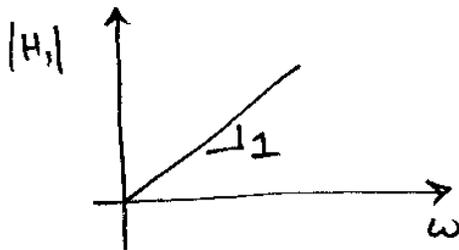

* Part (b):

$$H_2(s) \Big|_{s=j\omega} = H_2(j\omega) = \frac{1}{j\omega} = -j\frac{1}{\omega}$$

$$|H_2(j\omega)| = \frac{1}{\omega} \quad \angle H_2(j\omega) = -90^\circ$$

