

Name _____ Box _____


Due date: Tuesday, 5 Dec.

EC333

Homework #1

Winter 2000-2001

 1 Find a simplified logic expression and fill in the truth table for the circuit below.



A	B	C	Z
0	0	0	
0	0	1	
0	1	0	
0	1	1	
1	0	0	
1	0	1	
1	1	0	
1	1	1	

2 Design minimal sum-of-products logic to produce $Z=1$ if at least two bits in ABCD are 1s. Present logic expression and draw gate level implementation.

ABCD	Z
0000	
0001	
0010	
0011	
0100	
0101	
0110	
0111	
1000	
1001	
1010	
1011	
1100	
1101	
1110	
1111	

		AB			
		00	01	11	10
CD	00	0	4	12	8
	01	1	5	13	9
	11	2	7	15	11
	10	3	6	14	10

- 3 Design a controller with one 74LS193 4-bit counter and necessary gates for the 4-bit multiplier in Lab #1. Your controller should generate the following signals for the six select lines. See the attached data sheet for 74LS193.
- (A) A master reset switch will start the controller.
 - (B) Ten states are generated in sequence as follows. The controller should hold the result after the sequence.

Register	Clock cycle									
	1	2	3	4	5	6	7	8	9	10
A	hold	Load	LS	Load	LS	Load	LS	Load	LS	Hold
B	Don't Care	Hold	LS	Hold	LS	Hold	LS	Hold	LS	Hold
C	Load	Hold	LS	Hold	LS	Hold	LS	Hold	LS	Hold

From a controller's point of view, the events can be set up as follows.

Register	S1 S0									
	1	2	3	4	5	6	7	8	9	10
A	00	11	10	11	10	11	10	11	10	00
B	XX	00	10	00	10	00	10	00	10	00
C	11	00	10	00	10	00	10	00	10	00

- Hints: (1) Choose a natural sequence from the four outputs of the counter to represent the select signals.
- (2) The optimum implementation may not need any gate other than inverters for the control lines.
- (3) Extra logic is needed to hold the product after the 9th clock pulse.