 



PROBLEM 1 : You are given the following information for a handshaking design:

main controller



"GO" & "DONE" are active high

 Portion of main controller state transition diagram:




note that "GO" signal is generated in the same state as the wait for "DONE"

- Design the state transition diagram for the "6-cycle ~~dead~~ delay" device that will make the main controller stay in state m_5 for exactly six cycles.
- Draw the complete timing diagram that shows the handshaking signals as well as the states of the controller & 6-cycle delay.

PROBLEM 2 : Wakerly 8.20 (read 8.9.1 - 8.9.4)

 PROBLEM 3: Design a data unit and controller for a system that counts the number of bits in a 128-bit input value that are logic "1":



- START is active high of duration one clock period
- DONE is normally high. DONE drops low while Bit Counter is processing the input, then goes high again when processing is complete.
- ^{present your} Controller design as a state transition diagram
- Present a detailed block diagram of the data unit
- Clearly show all control signals from controller to data unit, and show all condition signals from data unit to controller.
- ~~*Data unit elements and controller FSM must all trigger on the rising edge of the clock input~~
- Write a paragraph that summarizes your overall approach to the design of this system