

GIVEN 74HC 74VHC devices can operate with a 3.3V supply

FIND Power savings compared to 5volt operation

SOLN

Dynamic $\propto V_{cc}^2$

$$5V \text{ supply} \Rightarrow V_{cc}^2 = 25 V^2$$

$$3.3V \text{ supply} \Rightarrow V_{cc}^2 = (3.3V)^2 = 10.9 V^2 \quad \left. \vphantom{3.3V} \right\} \text{key results}$$


$$\Rightarrow \frac{10.9 - 25}{25} \times 100\% = -56\%$$

\Rightarrow power is reduced a little more than a factor of two, ~~for~~ a drop by 56%.

(there are multiple ways to compare the two numbers!)

GIVEN

LED driven circuit :

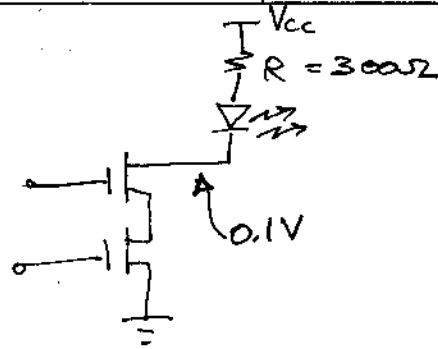

FIND:

- current flowing through LED
- how much power is dissipated by the pullup resistor

SOLN

* Assume that LED forward bias voltage is 1.6V
(see p.130 of text), & that V_{cc} is 5.0V (also see p.130)

$$\Rightarrow \text{voltage across resistor is } 5 - (1.6 + 0.1) = 5 - 1.7 \\ = 3.3 \text{ V}$$

$$\Rightarrow \text{current through resistor is } \frac{3.3}{300} = \boxed{11 \text{ mA}} \text{ (a)}$$

($\hat{=}$ also through LED)


(b) Power dissipated by resistor is (current)²(resistance)
or $\frac{(\text{voltage})^2}{\text{resistance}} = (11 \text{ mA})^2 (300) = \boxed{36.3 \text{ mW}} \text{ (b)}$

GIVEN Input waveform (see below)


FIND

- (a) Standard inverter response assuming 3.0V ^{transition} threshold
- (b) Schmitt trigger inverter response (L to H threshold = 3.0V, H to L threshold = 2.0V)


SOLN

 

 ← (approximate version of waveform on the HW sheet.)
times are not completely precise)



 ← [remember to make complete graphs... axis labels, scales, units]



← switches first time input rises above 3.0V.

← switches first time waveform falls below 2.0V

- GIVEN
- (a) 7" of coaxial cable
 - (b) 3 yards of coaxial cable
 - (c) 5" of PCB tracing, outer surface

FIND Minimum permissible rise time to consider each system a "lumped" system

SOLN

* Assume the following propagation delays:

coax cable \rightarrow 120 ps/in

FR4 PCB, outer trace \rightarrow 140 ps/in (could also be as high as 180 ps/in)

* Need the t-line to be less than $l/6$ in length,

where $l = \frac{\text{rise time}}{\text{delay}}$

$$\Rightarrow \frac{t_r}{6 \cdot \text{delay}} < L \quad (L = \text{t-line length})$$

$$\text{or } t_r > L \cdot 6 \cdot \text{delay}$$

$$(a) \quad t_r > (7") (6) (120 \text{ ps/in}) = 5.04 \times 10^3 \text{ ps} = \boxed{5.04 \text{ ns}}$$

$$(b) \quad t_r > (3 \text{ yd}) \left(3 \frac{\text{ft}}{\text{yd}} \right) \left(\frac{12 \text{ in}}{\text{ft}} \right) (6) (120 \text{ ps/in}) = \boxed{78 \text{ ns}}$$

$$(c) \quad t_r > (5") (6) (140 \text{ ps/in}) = \boxed{4.2 \text{ ns}}$$

GIVEN

T-line Java applet

$Z_0 = 100\Omega$, look at voltage at end of line ($x=100$)

Source termination methods:

- (a) $Z_S = 20\Omega$, $Z_L = \infty$
- (b) $Z_S = 20\Omega$, $Z_L = 20\Omega$
- (c) $Z_S = 20\Omega$, $Z_L = 100\Omega$
- (d) $Z_S = 100\Omega$, $Z_L = \infty$
- (e) $Z_S = 100\Omega$, $Z_L = 100\Omega$

FIND - Evaluate each termination technique, specifically in terms of ① how quickly signal settles down, whether or not CMOS gate would get multiple transitions, & ③ whether or not the CMOS gate sees a solid HIGH level after transient has died out.

- Include waveform sketches.

SOLN

- See next page for plots
& individual evaluations

Overall best results obtained for cases (c) & (d).

In both cases, only one end of the t-line is terminated by a matched load.

If termination^{resistance} is the same as the source resistance, then the potential stabilizes to only half of the source voltage (voltage divider effect)

22-141 50 SHEETS
 22-142 100 SHEETS
 22-144 200 SHEETS




CRITERIA:

① Settling Time

② Multiple Transitions


③ Solid HIGH

 

LONG

MANY


YES

 

LONG

NONE


No

 

FAST

NONE


YES
(slightly low)

 

FAST

NONE

YES

 

FAST

NONE

No

(a) Electro-Magnetic Compatibility

(b) See <http://signalintegrity.com/Pubs/news/noEMC.htm>

(c) Looking for a thoughtful response here!