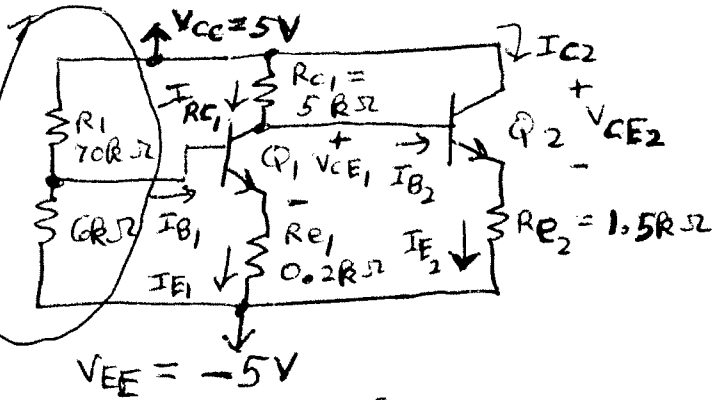



ECE250 Two-BJT Circuit Analysis Example

(Part A for finite β_F
Part B for $\beta_F \rightarrow \infty$)



Both BJTs have $\beta = 125$
 $(V_{BE})_{ON} = 0.7V$
 $(V_{CE})_{SAT} = 0.1V$

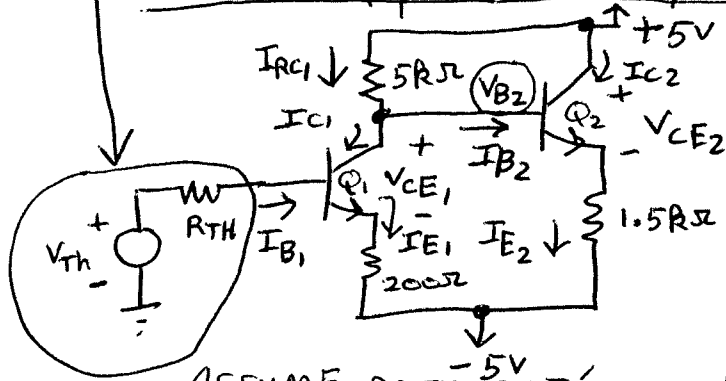A. Find Q points of Q_1 and Q_2 ($V_{CE1}, I_{C1}; V_{CE2}, I_{C2}$)



① Find V_{Th} by writing a Node Voltage eqn:

$$\frac{V_{Th} - 5}{70k} + \frac{V_{Th} - (-5)}{6k} = 0 \Rightarrow V_{Th} = -4.211V$$

② Find $R_{Th} = \frac{1}{\frac{1}{70k} + \frac{1}{6k}} = 5.526k\Omega$

ASSUME BOTH BJTs are FWD Active

③ Find I_{B1} by KVL around b-e loop of Q_1 :

$$V_{Th} = I_{B1} R_{Th} + 0.7V + 200(\beta_F + 1)I_{B1} + (-5V) \Rightarrow I_{B1} = 2.912\mu A$$

④ Write equations for V_{B2} (V_{B2} can be calculated 2 different ways:)

(a) $V_{B2} = +5V - (\beta_F I_{B1} + I_{B2}) 5k$

(b) $V_{B2} = 0.7V + I_{B2}(\beta_F + 1) 1.5k + (-5V)$

Solve Simultaneously

$$I_{B2} = 38.56\mu A$$

$$V_{B2} = 2.987V$$

⑤ $V_{CE1} = [5V - (\beta_F I_{B1} + I_{B2})(5k)] - [(\beta_F + 1)I_{B1}(200\Omega) + (-5V)]$

$$V_{CE1} = 7.91V$$

$$I_{C1} = \beta_F I_{B1} = 0.364mA$$

⑥ $V_{CE2} = [5V] - [(\beta_F + 1)I_{B2}(1.5k) + (-5V)] = 2.713V$ $I_{C2} = \beta_F I_{B2} = 4.82mA$

B. Repeat for $\beta_F \rightarrow \infty \Rightarrow I_B = \frac{I_C}{\infty} = 0$, and thus $I_E = I_C$ (For Both BJTs)

① $I_{E1} = I_{C1} = \frac{(V_{Th} - 0.7V) - (-5V)}{200\Omega} = 0.447mA$ (Note: Since $I_{B1} = 0$, there is no voltage drop across R_{Th} .)

② $V_{B2} = 5V - I_{C1} \cdot 5k = 2.763V$

③ $I_{E2} = I_{C2} = \frac{(V_{B2} - 0.7V) - (-5V)}{1.5k} = 4.71mA$

④ $V_{CE1} = (5 - I_{C1} \cdot 5k) - (V_{Th} - 0.7V) = 7.679V$

⑤ $V_{CE2} = 5 - (V_{B2} - 0.7V) = 2.933V$

Note: Part B ($\beta_F \rightarrow \infty$) is easier, and results are \approx close to Part A ($\beta_F = 125$)