

HW 8 Sample ECE250 Test 2 (KEH) 10 points,max (Each problem worth 0.1 x marked point value)
Allowed: 2 Pre-Published Formula Sheets & Open Laptop MAPLE (Duration: 160 Minutes)

Name: _____ CM# _____

Important Notes:


- i. You may use MAPLE on this test and/or a calculator, but to receive full credit, you must **show all key steps** in your problem solution in the space provided in order to properly document your solution.*
- ii. If you need more space, continue your work on the back of the page.*
- iii. All currents and voltages referred to in your solution must be clearly marked, along with polarity or reference direction, on the accompanying schematic diagram.*
- iv. Unless otherwise indicated in a specific problem, assume that all circuits are at room temperature ($V_T = 26 \text{ mV}$), all BJTs (whether NPN or PNP) have $n = 1$, $\beta_F = 100$, $\beta_R = 5$, $V_A = \infty$, and the NPN BJTs have $V_{BEon} = 0.7 \text{ V}$, $V_{CESat} = 0.2 \text{ V}$ while the PNP BJT's have $V_{EBon} = 0.7 \text{ V}$ and $V_{ECsat} = 0.2 \text{ V}$.*
- v. Remember to append the correct UNITS to your answer, where units are appropriate.*

1. (16 points---Each of the 4 circuits is worth 4 points) **Bipolar Junction Transistor (BJT) DC Analysis**


Find the indicated output voltage for each of the NPN or PNP BJT circuits below. Also indicate the operating mode of the BJT (forward active, reverse active, cutoff, or saturated)

Scrambled Answers: 0.2 V, Sat; 5.40 V, Fwd Active; 6.74 V, Fwd Active; 7.62 V, Fwd Active.

Circuit 1(a)

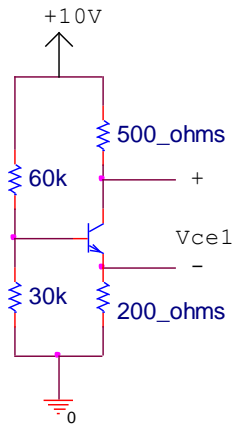

Circuit 1(b)


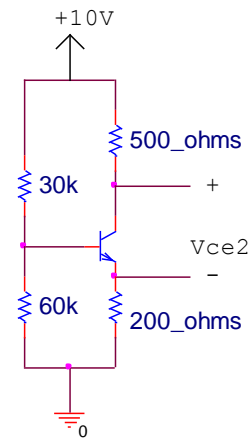


Vce1 = _____

Mode= _____

Vce2 = _____

Mode = _____

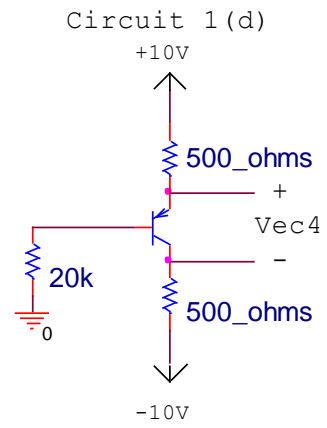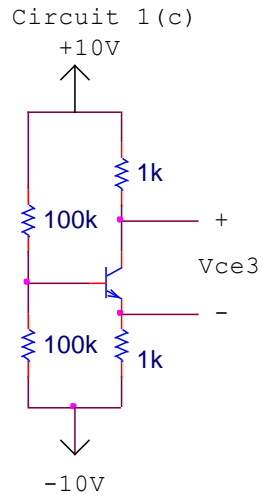

Vce3 = _____

Mode = _____


Vec4 = _____

Mode = _____

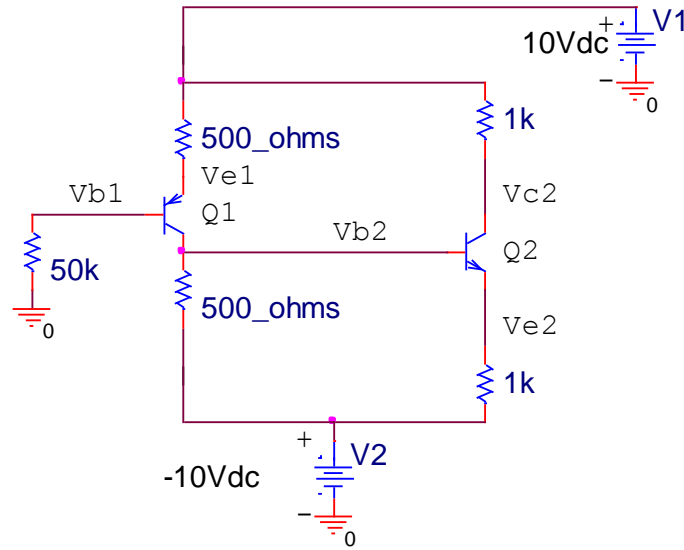2. (14 points) **Multiple-Transistor Bipolar Junction Transistor (BJT) DC Analysis**

Find the indicated node voltages in the circuit below that contains both an NPN and a PNP BJT, assuming the transistor parameters that are listed at the beginning of this exam.


Scrambled Answers: -6.093 V, 4.627 V, 6.131 V, 5.327 V, -5.393 V



Vb1 = _____ Ve1 = _____ Vb2 = _____ Vc2 = _____ Ve2 = _____

3. (14 points) **BJT Inverter Design.** A BJT inverter is shown in Fig. P2, along with its voltage transfer curve. Scrambled Answers: 0.2 V, 7.5 kohm, 0.7 V

Figure P2. BJT Inverter and its associated VTC

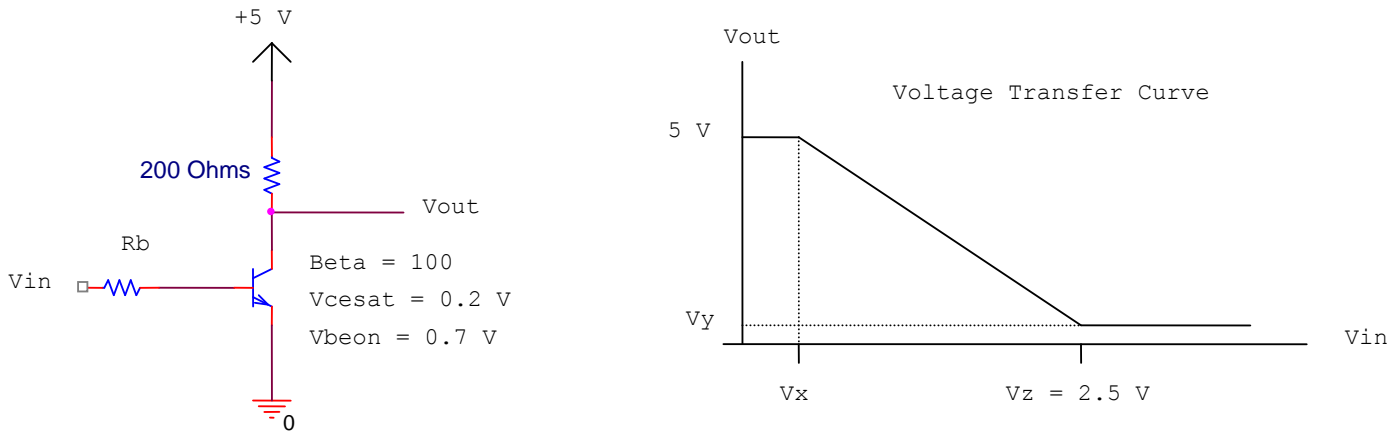

(a) (8 pts) Find the value of V_x , V_y , and also find the value of R_b that will make $V_z = 2.5 \text{ V}$.

$$V_x = \underline{\hspace{2cm}}$$

$$V_y = \underline{\hspace{2cm}}$$


$$R_b = \underline{\hspace{2cm}}$$

(b) (6 pts) Draw a circuit diagram in the space below that interconnects **FOUR NPN BJTs** that are identical to the BJT in Part (2a), two 200 ohm resistors, and four resistors of the value “ R_b ” that was calculated above in order to form an **S-R Latch** that is the same as the one you built and demonstrated in Lab 5. Be sure to clearly label the S and R inputs as well as the Q output of the SR latch on your diagram.

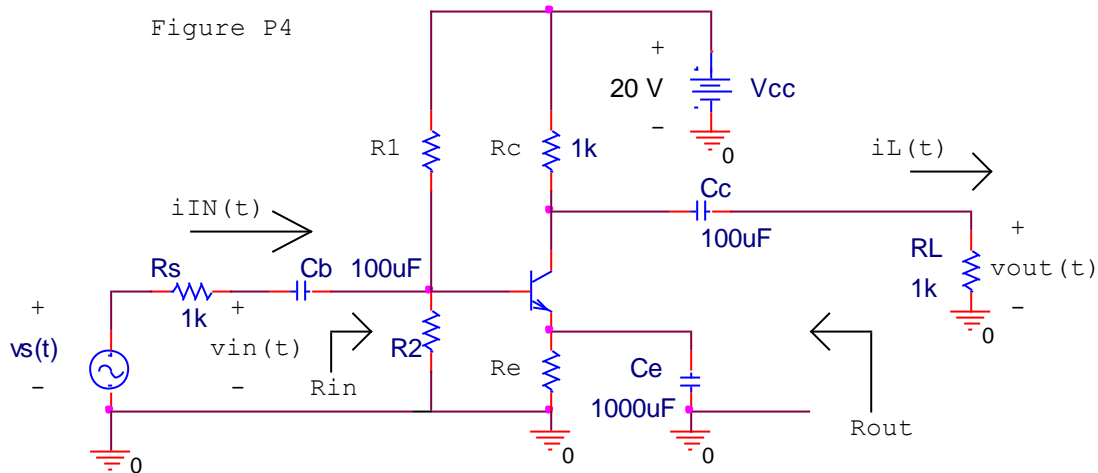4. (24 points) **Common-Emitter Amplifier**

See Figure P4 below. Assume the BJT parameters given at the beginning of this test, except (just for this problem) assume that the BJT has an Early Voltage of $V_A = 50 \text{ V}$.

Scrambled Answers: 1.374 kohm, 123.7 ohms, 13.89 kohm, 862.1 ohm, 258.0 ohms, -265.3, 1073, -36.75, -142.45, -29.21, 10.5 V, 3.47 V, 6.94 Vpp, 325 ohms, 0.308 S, 6.25 kilohm



Assume C_b , C_c , and C_e are all large enough that they may be considered short circuits at the signal frequencies being amplified.

(A) (8 pts) Find the values of R_e , R_1 , and R_2 so that the BJT's Q point will be $V_{ceq} = 11 \text{ V}$ and $I_{cq} = 8 \text{ mA}$, and so that the Q-point will be "reasonably stable" by following the "design rule of thumb" that was proposed in the course lecture notes: $(\beta + 1)R_e = 10 \cdot (R_1 \parallel R_2)$. (As we have done in class, ignore V_A when performing the dc modeling of the BJT.)

$R_e =$ _____

$R_1 =$ _____

$R_2 =$ _____

(B) (3 pts) Recalling that for this problem, $V_A = 50 \text{ V}$, calculate the small-signal BJT model parameters r_{pi} , g_m , and r_o . *Remember to include appropriate units, as with all of the answers on this test!*

$$r_{pi} = \underline{\hspace{2cm}}$$

$$g_m = \underline{\hspace{2cm}}$$

$$r_o = \underline{\hspace{2cm}}$$

(C) (4 pts) Draw the small-signal (ac) model of this circuit, and calculate the amplifier circuit's input resistance R_{in} , output resistance R_{out} , and the unloaded voltage gain $A_{vo} = (v_{out}/v_{in})_{R_L \text{ removed}}$. Remember to include "ro" in your model!

$$R_{in} = \underline{\hspace{2cm}}$$

$$R_{out} = \underline{\hspace{2cm}}$$

$$A_{vo} = \underline{\hspace{2cm}}$$

(D) (4 pts) Draw the *general voltage amplifier model* (consisting of the R_{in} , R_{out} , and A_{vo} values obtained above), and then terminate it with the load resistance of $R_L = 1\text{ k}\Omega$ at the output, and with the generator (consisting of $v_s(t)$ in series with R_s) at the input. From this model, determine the overall small-signal “ac” voltage gain $A_v = v_{out}/v_s$, the transducer voltage gain $A_{vt} = v_{out}/v_{in}$, the ac current gain $A_i = i_L/i_{IN}$, and the ac power gain $A_p = P_{load}/P_{source}$.


$$A_v = \underline{\hspace{2cm}}$$

$$A_{vt} = \underline{\hspace{2cm}}$$

$$A_i = \underline{\hspace{2cm}}$$

$$A_p = \underline{\hspace{2cm}}$$

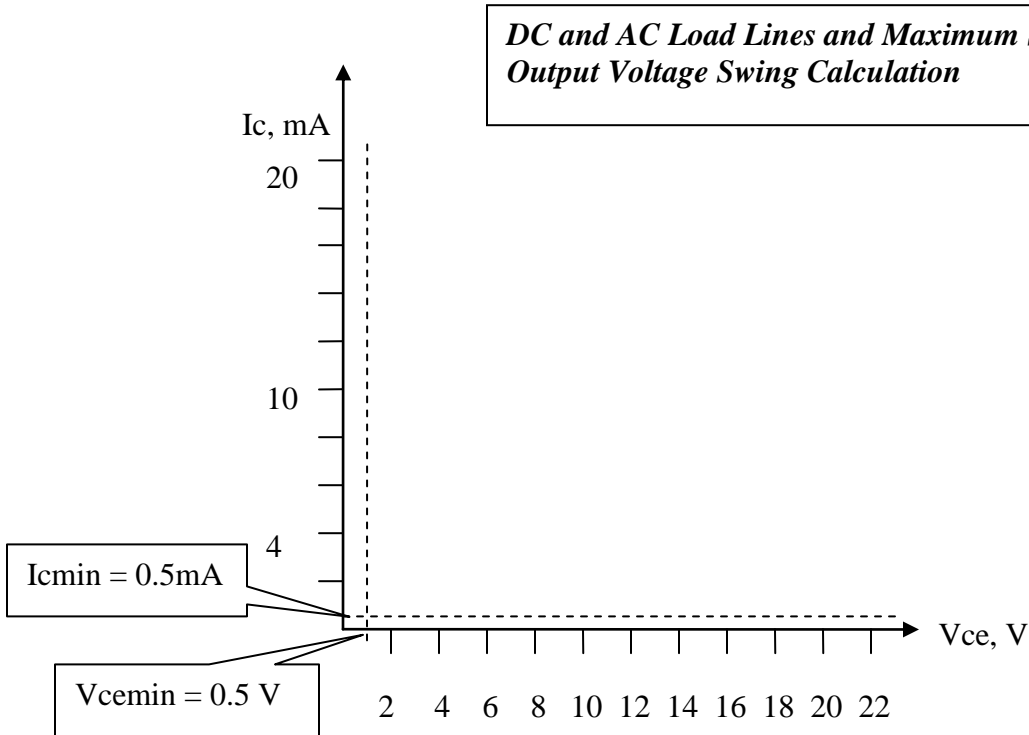(E) (5 pts) On the $I_c(t)$ vs. $V_{ce}(t)$ axes drawn below, plot the Q-point (V_{ceQ} and I_{CQ}). Then plot the dc and ac load lines. In order to promote better amplifier linearity, assume that we desire to restrict the minimum allowable value of I_c to $I_{c_{MIN}} = 0.5 \text{ mA}$ and the maximum allowable value of V_{ce} to $V_{ce_{MIN}} = 0.5 \text{ V}$. Calculate how far $V_{ce}(t)$ may swing both above and below the V_{ceQ} value. From these two results, determine the *maximum (peak-to-peak) symmetrical output voltage swing* exhibited by this amplifier.




Amount V_{ce} may swing ABOVE $V_{ceq} =$ _____ V

Amount that V_{ce} may swing BELOW $V_{ceq} =$ _____ V

Max Symmetrical Output Voltage Swing = _____ V,pp

Figure P5. Common-Collector (Emitter Follower) Amplifier

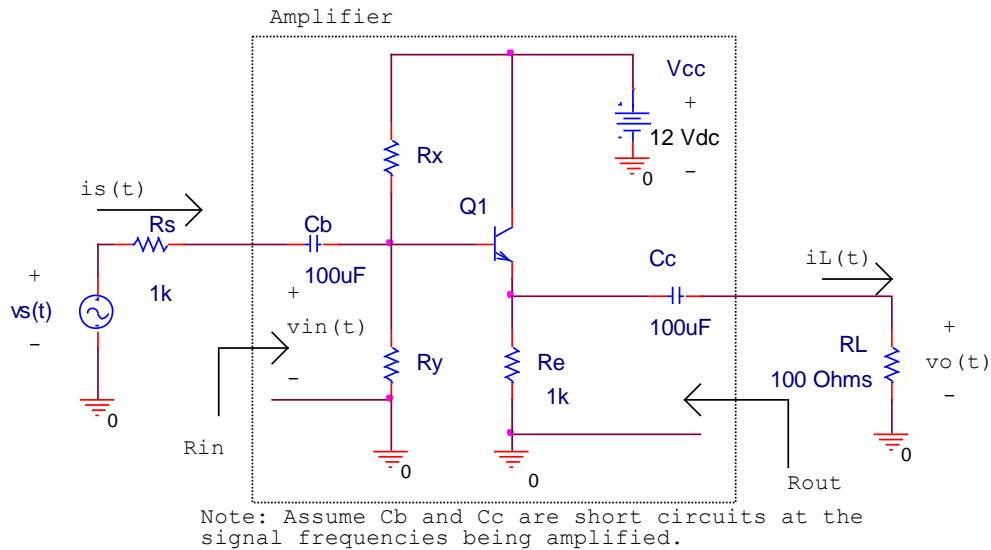

5. (20 points) **Common-Collector Amplifier**

Scrambled Answers: 7.752 V, 4.206 mA, 618 ohms, infinite ohms, 0.162 S, 0.994, 154 ohms, 20 kilohms, 7 kilohms, 54.1, 65.96, 0.820, 0.861

- A. (4 pts) Consider the circuit shown in Fig. P5. If $R_x = 50 \text{ k}\Omega$ and $R_y = 50 \text{ k}\Omega$ and the BJT has the parameters listed at the beginning of the test (note that V_A is once again infinity), calculate the Q-point in the space below, showing **clearly** that the Q-point is **$V_{ceq} = 7.75 \text{ V}$** and **$I_{cq} = 4.21 \text{ mA}$** .

- B. (1 pt) Recall the design rule for an excellent “ β – stable Q-point” was found to be $(\beta+1)R_e \gg R_{th}$. Based on this conclusion, how would you rate the stability of the Q-point of this circuit with respect to β ?

(a) Excellent (b) moderate (c) poor

Defend your choice in the space below (evaluate both sides of the design rule stated above.)

- C. (3 pts) Assuming that $V_A = \infty$ in this problem, determine the BJT ac model small-signal ac parameters r_{pi} , g_m , and r_o . Draw the ac model of the BJT, clearly marking the B, C, and E terminals.

$$r_{pi} = \underline{\hspace{2cm}}$$

$$g_m = \underline{\hspace{2cm}}$$

$$r_o = \underline{\hspace{2cm}}$$

- D. (8 pts) Draw the AC model of the entire circuit, and calculate the input resistance with, and without, the load resistor R_L attached, the output resistance R_{out} , and the unloaded voltage gain $A_{vo} = (v_{out}/v_{in})_{R_L \text{ removed}}$

$$R_{in_noRL} = \underline{\hspace{2cm}}$$

$$R_{in_withRL} = \underline{\hspace{2cm}}$$

$$R_{out} = \underline{\hspace{2cm}}$$

$$A_{vo} = (v_{out}/v_{in})_{R_L \text{ removed}} = \underline{\hspace{2cm}}$$

E. (4 pts) Draw the **general voltage amplifier model** (in terms of R_{in} , R_{out} , and A_{vo}) and determine the overall voltage gain $A_v = v_{out}/v_s$ (*be careful about which value of R_{in} that you use!*) and the transducer voltage gain $A_{vt} = v_{out}/v_{in}$. Also find the current gain $A_i = i_L/i_s$ (*be careful about which value of R_{in} that you use!*), and finally find the power gain $A_p = P_{LOAD}/P_{SOURCE}$

$$A_v = \underline{\hspace{2cm}}$$

$$A_{vt} = \underline{\hspace{2cm}}$$

$$A_i = \underline{\hspace{2cm}}$$

$$A_p = \underline{\hspace{2cm}}$$

(12 points) **Concept Questions.** (2/3 point per blank) Circle the ONE best answer per blank.

A. As V_{ce} is increased across a forward-active BJT, the width of the depletion region of the reverse-biased base-collector junction Blank 0 so that its effective base width Blank 1 so that its β Blank 2. Therefore its I_c vs V_{ce} family of curves (each curve drawn for a constant base current value) tend to Blank 3 as V_{ce} is increased. If the straight part of each of these curves is extended back, they all intersect the V_{ce} axis at Blank 4, and this so-called “base width modulation effect” is accounted for in the ac model of a BJT by adding a relatively large resistor “ r_o ” across Blank 5.

- Blank 0: a. decreases b. increases c. stays the same
 Blank 1: a. decreases b. increases c. stays the same
 Blank 2: a. decreases b. increases c. stays the same
 Blank 3: a. slope slightly downward b. slope slightly upward c. remain horizontal
 Blank 4: a. $-r_o$ b. $-g_m$ c. $-\pi$ d. V_{CEsat} e. $-V_A$
 Blank 5: a. $r\pi$ b. the C-E terminals c. the C-B terminals d. the B – E terminals.

B. Removing the emitter bypass capacitor that is across the emitter resistor in a common-emitter BJT amplifier will Blank 1 and also Blank 2.

- Blank 1: a. increase I_{cQ} b. decrease I_{cQ} c. increase its A_{vo} d. decrease its A_{vo}
 Blank 2: a. increase its R_{in} b. decrease its R_{in} c. increase its R_{out} d. decrease its R_{out}

C. Let us compare the common-emitter (CE) and the common-collector (emitter-follower) (CC) BJT amplifier configurations.

- i. Which amplifier configuration is known for its relatively low output resistance, and would therefore be the best choice for a stage whose output connects to a relatively low-impedance load (such as a loudspeaker in a PA system like the one considered in lab)?
 a. CE b. CC
 ii. Which amplifier configuration is known for its relatively high voltage gain, and would therefore be the best choice for a microphone voltage preamplifier stage in a PA system such as the one built in lab?
 a. CE b. CC
 iii. Which amplifier configuration is known for its relatively high input resistance, and would therefore not significantly “load down” the output voltage from a high-impedance signal source or transducer?
 a. CE b. CC

D. In a forward-active **PNP** BJT, the principle current conduction mechanism is Blank 1 diffusing from the Blank 2 region, through the very thin Blank 3 region, and then being SWEEPED across the reverse-biased Blank 4 junction by the intense electric field that exists in the depletion region of that junction.

- Blank 1: a. electrons b. holes c. positrons d. Neutral silicon atoms
 Blank 2: a. emitter b. base c. collector
 Blank 3: a. emitter b. base c. collector
 Blank 4: a. base-emitter b. base-collector c. collector-emitter

E. In order to optimize the operation of a modern BJT, its Blank 1 region is typically doped much **more** intensely than its Blank 2 region, which in turn is doped much **more** intensely than its Blank 3 region.

- Blank 1: a. emitter b. base c. collector
 Blank 2: a. emitter b. base c. collector
 Blank 3: a. emitter b. base c. collector