

EC250 Laboratory Project #2

PN Junction Diode Modeling

Team Members: _____

Date Performed: _____ Lab Station #: _____

Parts needed: 1N4148 small-signal (small glass package) diode, 1N4004 power diode, red LED, three 1 k Ω resistors, breadboard, wire strippers, hookup wire.

Prelab Work: Please complete the requested formula derivation and also the simulated test data analysis required on p. 3 *before* coming to the laboratory. (See Appendix A for a review of using Microsoft Excel to plot data and fit the plot to a straight line.)

1. The pn junction diode as a "unidirectional flow valve"

Connect a small-signal 1N4148 diode in series with a 1 k Ω resistor and a 5 V dc power supply, as shown in Fig. 1. Begin by connecting the "bar" end of the diode package to the (-) terminal of the 5 V supply. Measure the voltage across the diode (V_d) and the voltage across the resistor (V_r), the sum of these two readings better equal 5.0 V. Indicate whether the diode is "forward-biased" or "reverse-biased". Now reverse the power supply terminals and again measure V_d and V_r . Repeat for the 1N4004 power diode and a red LED:

1N4148 small signal diode with "bar" end connected to (-) terminal of 5 V supply:

$V_d =$ _____ $V_r =$ _____ Fwd or Reverse Bias _____

1N4148 small signal diode with bar end connected to (+) terminal of 5 V supply.

$V_d =$ _____ $V_r =$ _____ Fwd or Reverse Bias _____

1N4004 power diode with bar end connected to (-) terminal of 5 V supply:

$V_d =$ _____ $V_r =$ _____ Fwd or Reverse Bias _____

1N4004 power diode with bar end connected to (+) terminal of 5 V supply.

$V_d =$ _____ $V_r =$ _____ Fwd or Reverse Bias _____

Red LED with short lead connected to (-) terminal of 5 V supply.

$V_d =$ _____ $V_r =$ _____ Fwd or Reverse Bias _____

Red LED with short lead connected to (+) terminal of 5 V supply.


$V_d =$ _____ $V_r =$ _____ Fwd or Reverse Bias _____

In the space below, sketch each of these diodes, and below each sketch, draw the correct corresponding diode symbol. Does the "bar" on the diode package match with the bar (cathode terminal) in the diode symbol? Which lead of the LED, long lead or short lead (with the flattened rim), corresponds to the cathode terminal in the diode symbol?

2. Diode Model Parameter Determination (Finding n and I_s)

We shall use a 1 k Ω resistor as a "current sensing" element, which is connected in series with a 1N4148 small-signal diode (connected so the diode will be forward-biased) and your variable dc bench power supply, as shown in Figure 1. Record the DVM voltage measurements across the diode, and also across the current sensing resistor (V_d and V_r). Use the Microsoft Excel spreadsheet program to make a table of your results. Start by entering side-by-side columns for V_d and V_r . Then, from the V_r column, calculate additional columns that display I_d (in Amperes) and also the natural log of I_d , $\ln(I_d)$. Now vary your dc supply voltage so that you obtain data points corresponding to $V_r = 20$ V, 10 V, 5V, 2.5 V, 1.25 V, 0.625 V, 0.3125 V (or as close as you can come to these values.) Please remember that V_r is the voltage across the 1 k Ω resistor, **not** the dc power supply voltage, which must be set slightly higher than V_r to overcome the diode junction drop.

Figure 1. Diode I-V Curve Measurement Circuit

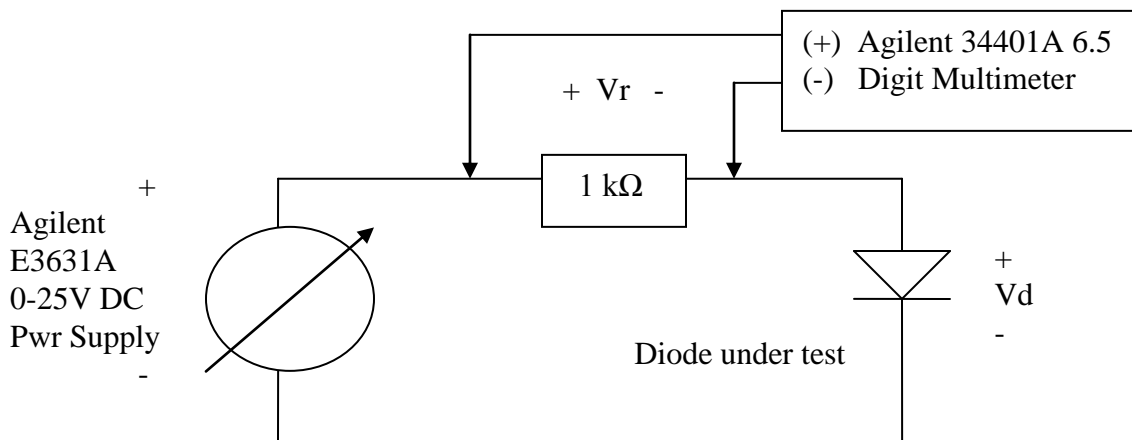

Repeat these measurements using a 1N4004 power diode and a Red LED. Attach this table (including you measurements for each of these three diodes) **as "Exhibit A"**. From your recorded data, list the observed "diode forward voltage drop" at a forward diode current of 10 mA for each of these three common types of diodes?

Small Signal Diode Forward Voltage Drop at 10 mA = _____ Volts

Power Diode Forward Voltage Drop at 10 mA = _____ Volts

Red LED Forward Voltage Drop at 10 mA = _____ Volts

For your small-signal diode data, use Microsoft Excel (see Appendix A) to plot V_d vs. I_d and also plot V_d vs. $\ln(I_d)$. Attach these two plots as "**Exhibit B**". Which of these two plots appears to be more "linear"? _____

In the space below, start with the ideal diode equation

$$I_d = I_s[\exp(V_d/(n \cdot V_t)) - 1], \quad \text{where } V_t = k \cdot T / q$$

throw out the "-1" (go to the forward-bias approximation), and derive formulas for finding n and I_s from the slope (m) and y intercept (b) of the linear least squares curve fit (linear regression) of the V_d vs. $\ln(I_d)$ plot, which is of the form $V_d = m \cdot \ln(I_d) + b$. You may assume that the thermal energy per coulomb of charge is given by $V_t = kT / q = 0.026$ Volts, since our laboratory is at "room temperature". You should be able to show that

$$I_s = \exp(-b / m) \text{ and } n = m / V_t$$

Derivation of expressions for I_s and n in terms of linear regression parameters m and b

First use the Microsoft Excel spreadsheet to perform a linear least squares regression analysis on the following PSPICE simulated data. Follow the instructions in Appendix A.

V_r	$V_d(\text{D1N4148})$	$V_d(\text{D1N4002})$
20 V	0.765 V	0.727 V
10 V	0.723 V	0.691 V
5 V	0.685 V	0.656 V
2.5 V	0.650 V	0.620 V
1.25 V	0.615 V	0.584 V
0.625 V	0.582 V	0.549 V
0.3125 V	0.549 V	0.513 V

Use the Microsoft Excel spreadsheet to perform a linear least squares regression analysis on this simulated V_d vs. $\ln(I_d)$ data for the two diodes indicated, which were taken from the PSPICE "Eval" library. Attach your computer-generated EXCEL spreadsheet, as well as each of the two linear regression plots, as *Exhibit C*. Fill in your regression results, and also calculate the corresponding n and I_s values for each of the diodes right on the spreadsheet. You **MUST SHOW** that your answers come out to $n = 1.981$ and $I_s = 7.809 \times 10^{-9}$ A, with $R^2 = 0.998$ for the

D1N4148 simulated diode, and $n = 1.977$ and $I_s = 1.439 \times 10^{-8}$ A with $R^2 = 1.00$ for the D1N4002 simulated power diode. If you cannot get your spreadsheet to give the correct answers with these simulated data, please get help! **No credit will be given for this entire laboratory if this check data cannot be properly analyzed in Exhibit C!**

Once you have gotten the correct answers for the simulated data, repeat your analysis with the live data that you have collected for the three “real” diodes you recorded in Part A, be sure to include your R^2 value, whose closeness to 1 indicates how reliably your measurements were. Include your spreadsheet as **Exhibit D**.


1N4148 $m =$ _____ $b =$ _____ $n =$ _____ $I_s =$ _____ A $R^2 =$ _____

1N4004 $m =$ _____ $b =$ _____ $n =$ _____ $I_s =$ _____ A $R^2 =$ _____

Red LED $m =$ _____ $b =$ _____ $n =$ _____ $I_s =$ _____ A $R^2 =$ _____

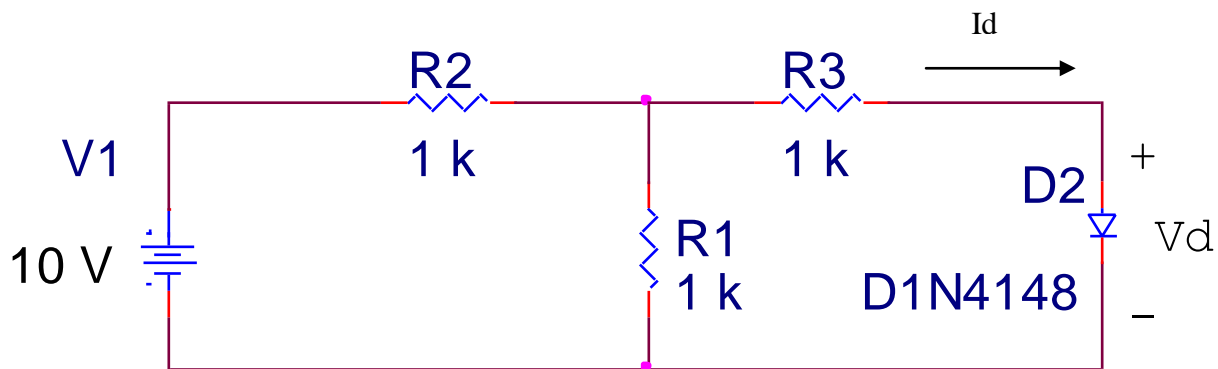3. Application of Diode Model to Solve for V_d and I_d

Use the n and I_s values obtained above for your 1N4148 diode to (numerically) solve (using MAPLE or MathCad) for the diode current I_d and the diode voltage V_d when it is placed in the circuit drawn below. Start by finding the Thevenin Equivalent of what is seen looking out from the diode terminals. Include your MAPLE or MathCad work as “**Exhibit E**”.



Finally, build this circuit and compare the measured I_d and V_d values (I_d can be found by measuring the voltage across resistor R3) with the predicted ones using the diode model. Fill in the summary table below:

Measured Values	Predicted Values	% Error (Pred – Meas) / Pred
$I_d =$ _____	_____	_____
$V_d =$ _____	_____	_____

Now assume that the forward-biased diode has a constant 0.7 V forward voltage drop, and therefore it simply acts like a 0.7 V battery. Now re-calculate I_d and compared with the predicted value for I_d above. Calculate the % error incurred by adopting this MUCH SIMPLER diode model.

Method 1	Method 2	
Pred I_d (from above)	Pred I_d using simplified	% Error
Using diode equation	Constant 0.7 V model	$(\text{Meth2}-\text{Meth1})/\text{Meth1}$
$I_d =$ _____	$I_d =$ _____	_____

4. Using an LED as a “reciprocal” transducer

In Part 1 you should have already observed that the LED lights when it is forward biased. In this case, current (or voltage) is the stimulus or input variable, and light is the result, or output variable. Likewise, it turns out that, like most transducers, the LED can be used in the reciprocal sense; that is, light can be used as the stimulus (or input), and then voltage will be generated across the LED as the result, or output variable. Investigate this phenomenon using your bench dc voltmeter and fill in the blanks below:

NO light (LED well covered by fingers): V_d (anode w.r.t. cathode) = _____ V

Moderate light (LED aimed toward room lights): V_d (anode w.r.t. cathode) = _____ V

Bright light (overhead projector?): V_d (anode w.r.t. cathode) = _____ V

Appendix A. Plotting Data and Least-Squares Curve Fitting with Excel 2007

- 1) Bring up Microsoft Excel (**Start – All Programs – Microsoft Office - Microsoft Office Excel 2007**). Enter the V_r values (20 V, 10 V, 5 V, 2.5 V, 1.25 V, 0.625 V, 0.3125 V) in the first column of the spreadsheet. Label the top of each column, as shown in the example spreadsheet below. From the V_r values, calculate the diode current values in Amperes (I_d) in the 2nd column. Do this by clicking on the first row of the I_d column, and enter the equation

$$=A2/1000$$

where A2 identifies the location of the top entry in the V_r column, and this value is divided by the value of the 1000 ohm resistor. You may then copy this entry into the remaining positions of the I_d column. Next, calculate the corresponding $\ln(I_d)$ values in the 3rd column. Do this by typing the following equation into the first row of the $\ln(I_d)$ column:

$$=\ln(B2)$$

where B2 is the location of the top entry in the I_d column. You may then copy this entry into the remaining positions of the $\ln(I_d)$ column. Finally, enter the diode voltage (V_d) data in the 4th column.

- 2) By holding down the left mouse button and dragging it downward, select the $\ln(I_d)$ column. Next, hold down the Ctrl key and select the V_d column. **Note that the leftmost column selected will go onto the horizontal axis of the plot. Therefore, it is important to place the V_d column to the right of the $\ln(I_d)$ column, so that the $\ln(I_d)$ data goes on the horizontal axis and the V_d data goes on the vertical axis.**
- 3) Now click on the **Insert** tab and select **Scatter**. Then select the scatter plot icon with the smooth lines drawn through the points. The desired plot should appear with $\ln(I_d)$ on the horizontal axis and V_d on the vertical axis, as desired.
- 4) To add an appropriate plot title and both horizontal and vertical axis titles, click anywhere inside the chart (to select it), and then click on the **Layout** tab at the top of the screen. Select **Chart Title** and enter it (in this case “ **V_d vs. $\ln(I_d)$ Plot for 1N4148 Diode**”). In similar fashion click on the **Layout** tab once again, but this time select **Axis Titles**. Label the vertical axis “ **V_d in volts**” and label the horizontal axis “ **$\ln(I_d)$, where I_d is in Amperes**”. Note that we cannot ascribe any units to the natural log of I_d , $\ln(I_d)$. However we might as well point out that I_d is in Amperes.
- 5) The resulting scatter plot can be sized in the usual way by applying the mouse to the chart borders. Likewise, the chart can be dragged out to any desired position on the spreadsheet. Likewise the axis labels and chart label can be dragged to any desired position within the chart area.
- 6) To add least-squares linear curve fit (regression) trend line, **LEFT CLICK** on the data line in the plot so that the points on the line are highlighted. Then left click on the **Layout** tab at the top of the page and select “**Trendline**”. Click on the “**More Trendline Options**” at the bottom of the list. A “**Trendline Options**” box should appear. In the “**Trend/Regression Type**” box, click on “**Linear**”. Now click the “**Options**” tab. Check the box labeled “**Display Equation on Chart**”. This equation is of the form $y = mx + b$, where “ y ” is the dependent variable on the vertical (in this case V_d), and “ x ” is the independent variable on the

horizontal axis (in this case $\ln(I_d)$). Likewise, m is the slope of the line and b is the y-intercept.

- 7) Also check the box labeled “**Display R^2 value on chart**”. R is called the “linear correlation coefficient”, which varies between (0, 1). The closer to 1 it is, the better the linear curve fit is, and hence the more closely your data falls along a straight line. Thus the closer the R^2 value is to one, the “better” your data is! Hit the **close** button. The linear curve fit equation, as well as the linear correlation coefficient can now be “dragged and dropped” wherever you would like them to be placed on the chart.

Your spreadsheet should now look like the one shown below:

Vr	Id(1N4148)	ln(Id)	Vd(1N4148)
20	0.02	3.91202	0.765
10	0.01	4.60517	0.723
5	0.005	5.29832	0.685
2.5	0.0025	5.99146	0.65
1.25	0.00125	6.68461	0.615
0.625	0.000625	7.37776	0.582
0.3125	0.0003125	8.07091	0.549

