


Quiz 11

ECE331 Class Quiz #11 3 points maximum (Lecture 11 Microcontroller Interfacing)


Name: _____ CM Box: _____

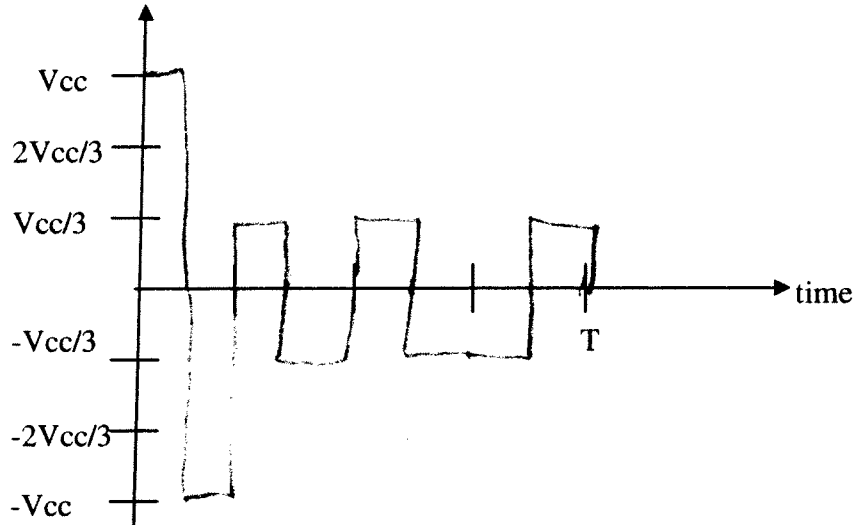- 1) (1 pt) Recall that in Lecture Slide #12, for the case of 1:4 multiplexing discussed in class, the front plane voltage waveform “(f)” corresponds to Segment 1, 2, and 3 ON and Segment 4 off. Let us call this waveform “FPi(f)”
- a) Sketch 1 period (from $t = 0..T$) of the voltage waveform that exists across Segment 1. This is the segment that is driven by this FPi(f) waveform and the Backplane 1 waveform. Next, sketch 1 period of the voltage waveform that exists across Segment 4.



$V_{seg1} = (BP1 - FPi(f))$, the voltage across Segment 1 of FPi (f)



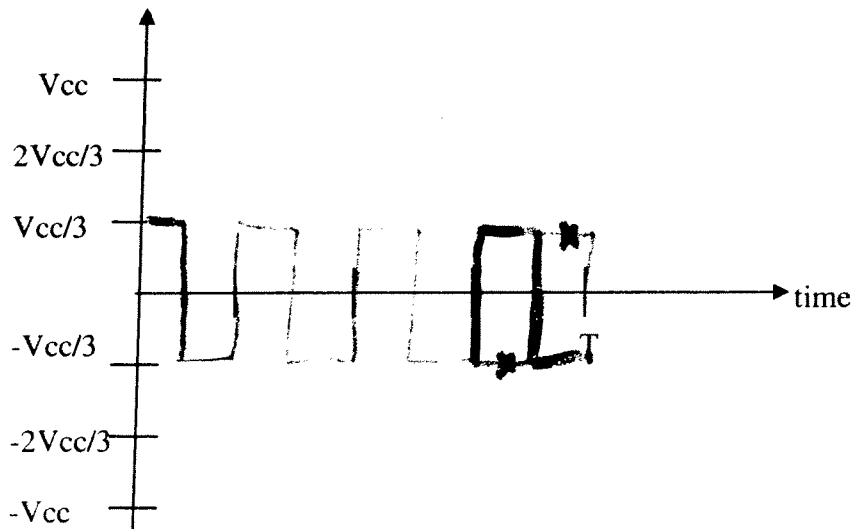$V_{seg4} = (BP4 - Fpi(f))$, the voltage across Segment 4 of FPi (f)



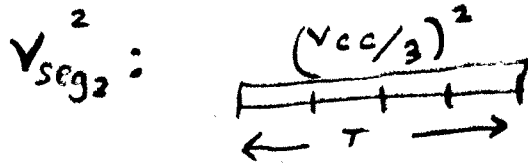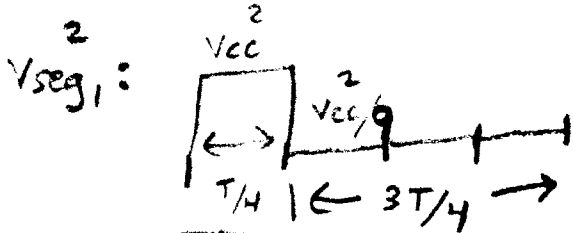- b) Find the RMS voltage of the Segment 1 and Segment 4 waveforms obtained in Part (a), assuming that $V_{cc} = 5.0$ Volts. Show your calculations clearly in the space below.



$$V_{seg1, RMS} = \sqrt{\frac{1}{T} \int_0^T V_{seg1}^2 dt} = \sqrt{\frac{1}{T} \left[V_{cc}^2 \cdot \frac{T}{4} + \frac{V_{cc}^2}{9} \cdot \frac{3T}{4} \right]} = \sqrt{V_{cc}^2 \left[\frac{1}{4} + \frac{3}{36} \right]} = \sqrt{\frac{V_{cc}^2}{3}}$$

$$= \sqrt{\frac{5^2}{3}} = \sqrt{\frac{25}{3}} = 2.886 V$$

$$V_{seg2, RMS} = \sqrt{\frac{1}{T} \left[T \cdot \frac{V_{cc}^2}{9} \right]} = \sqrt{\frac{V_{cc}^2}{3}} = \frac{V_{cc}}{3} = \frac{5}{3} = 1.667 V$$

$$V_{seg1} = \underline{2.886} \text{ V, rms}$$

$$V_{seg4} = \underline{1.667} \text{ V, rms}$$

- c) From the LCD contrast plot presented on an earlier slide, an LCD segment is ON (dark) if its periodic segment voltage is greater than 2.8 V, rms. Likewise a segment is OFF (light) if periodic segment voltage is less than 1.7 V, rms.

- d) Indicate the state of Segment 1 and Segment 4 (ON or OFF) based upon your answers to Parts (b) and (c) above.

Segment 1 state ON (dark)
Segment 4 state OFF

- e) An LCD display has 416 segments. How many connections need be made to the LCD display if no multiplexing (1:1 multiplexing is used)? 417

$$416 + 1 = 417$$

How many connections need be made to the LCD display if 1:4 multiplexing is used?

$$4 + \frac{416}{4} = 4 + 104 = 108$$

$$\underline{108}$$

How many connections need be made to the LCD display if 1:6 multiplexing is used?



$$6 + \frac{416}{6} = 6 + 69.33 = 76$$

$$\underline{76}$$


round up
to 70

2) (1 pts) Now consider a 1:6 multiplexed display (with 6 backplane signals). The backplane voltage waveforms will still take on the same 4 discrete voltage values as before, and they follow in the same pattern as before.

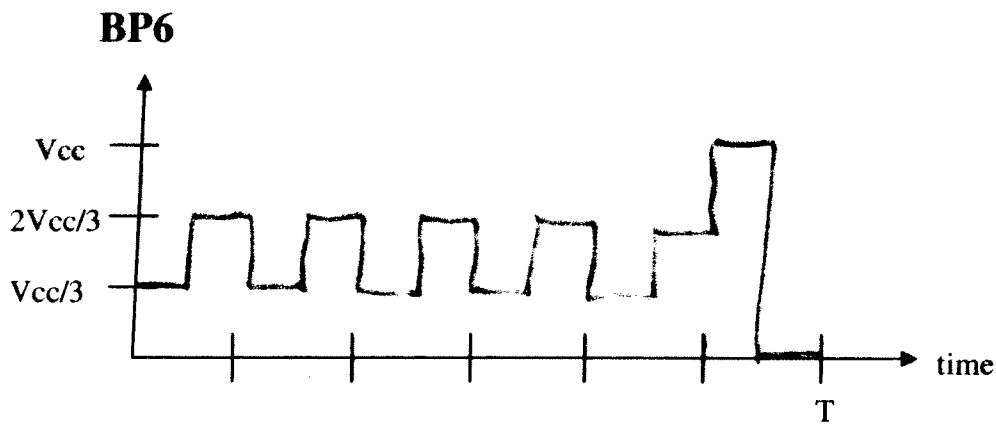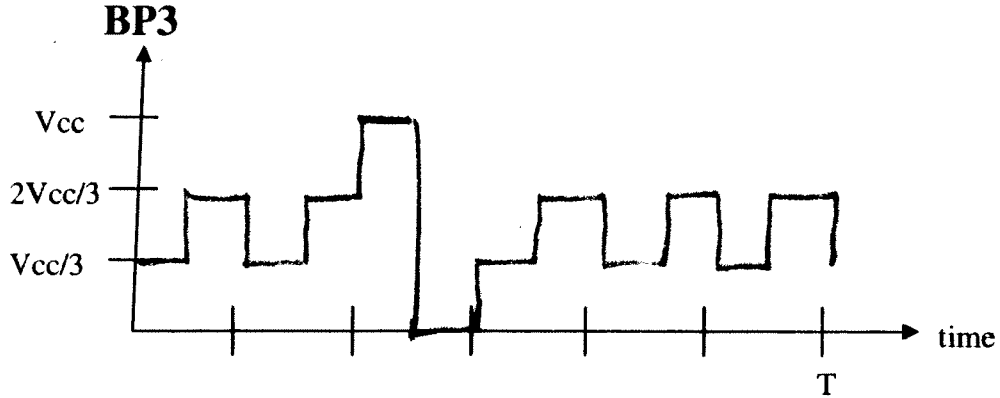a) Sketch one period (from $t = 0..T$) of the BP3 signal and the BP6 backplane voltage waveform below. Also sketch one period of the F_{Pi} signal that turns ON the segments over BP1, BP3, and BP5 and turns OFF the segments over BP2, BP4, and BP6.




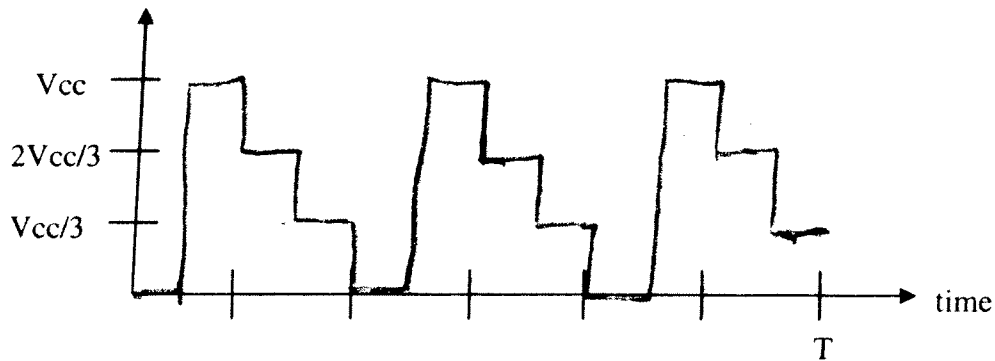F_{Pi} (This waveform should turn ON Segments 1,3,5 and turn OFF Segments 2,4,6)




b) Sketch one period of the electrode voltage across segments 3 and 6.

(BP3 – Fpi) Segment 3 periodic voltage waveform

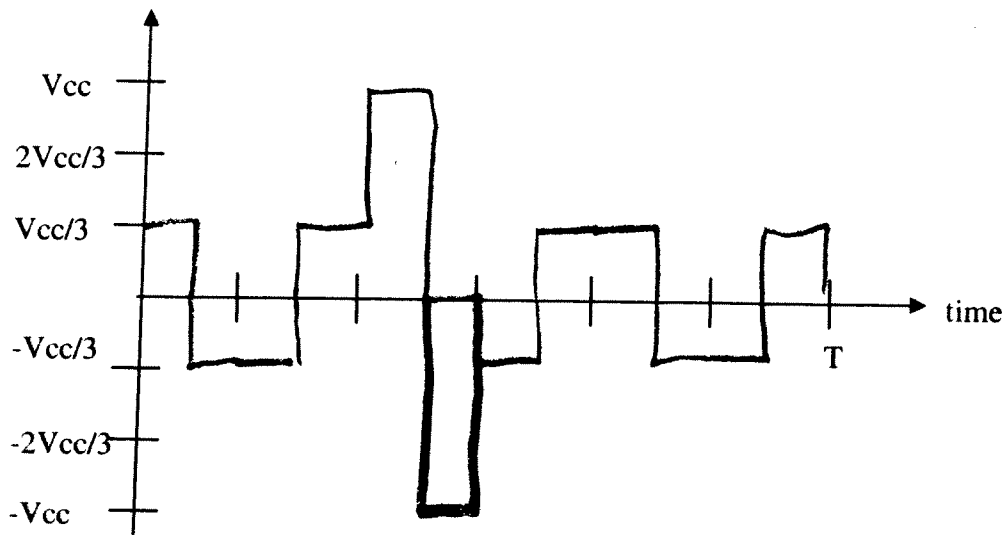

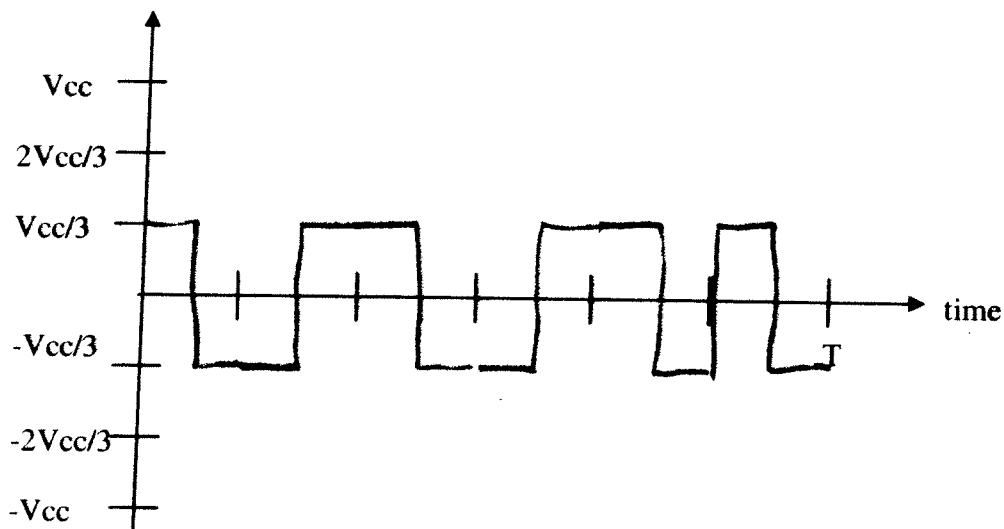(BP6 – Fpi) Segment 6 periodic voltage waveform



c) Calculate the RMS values of these two segment waveforms in the space below.

$$V_{\text{Seg3}}^{\text{RMS}} = \sqrt{\frac{1}{T} \left[\frac{V_{\text{cc}}^2}{9} \left(\frac{5T}{6} \right) + V_{\text{cc}}^2 \left(\frac{T}{6} \right) \right]} = V_{\text{cc}} \sqrt{0.2592} = 2.546V$$

$$V_{\text{Seg6}}^{\text{RMS}} = \sqrt{\frac{1}{T} \left[\frac{V_{\text{cc}}^2}{9} (T) \right]} = \frac{5}{3} = 1.667V$$

$$V_{\text{rms_Seg3}} = 2.546 \text{ V,rms}$$

$$V_{\text{rms_Seg6}} = 1.667 \text{ V,rms}$$

d) Though the number of wires are fewer for 1:6 multiplexing (as compared to 1:4 multiplexing), explain why the contrast (darkness) of the turned ON segment is lower.

darkness lower since $2.546V < 2.886V$
 (contrast down on "contrast spec.", 2/3 to 2)