

Interfacing EM Relays, Solenoids, and DC Motors

- Interface circuit must provide sufficient current and voltage to activate the device.
- In off state, input current should be zero.
- Due to inductive nature of the coil, huge back electromotive force (EMF) when coil current is turned off.
- Due to high speed transistor switch, there is a large *di/dt* when the coil is deactivated (activation also but smaller).
- Voltages can range from 50 to 200V.
- To protect the driver electronics, a snubber diode is added to suppress the back EMF.

Isolated Interfaces

6N139

Vdd

800Ω

7405

Chris J. Myers (Lecture 15: Relays and Motors) ECE/CS 5780/6780: Embedded System Desig

Vdd

Computer

╧

Vpp


 $1k\Omega$

Vpp

Coil


IRF540

Relay and Motor Interfaces

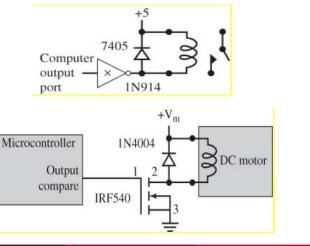


Chris J. Myers (Lecture 15: Relays and Motors) ECE/CS 5780/6780: Embedded System D

H-Bridge

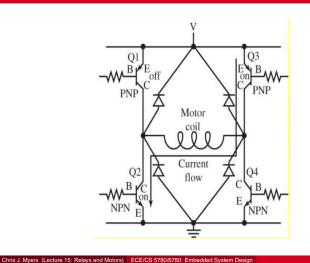

Isolated H-Bridge with Direction Control

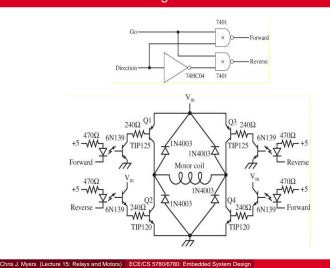



• Very popular due to inherent digital interface.

- Easy to control both position and velocity in an open-loop fashion.
- Though more expensive then ordinary DC motors, system cost is reduced as they require no feedback sensors.

Stepper Motors

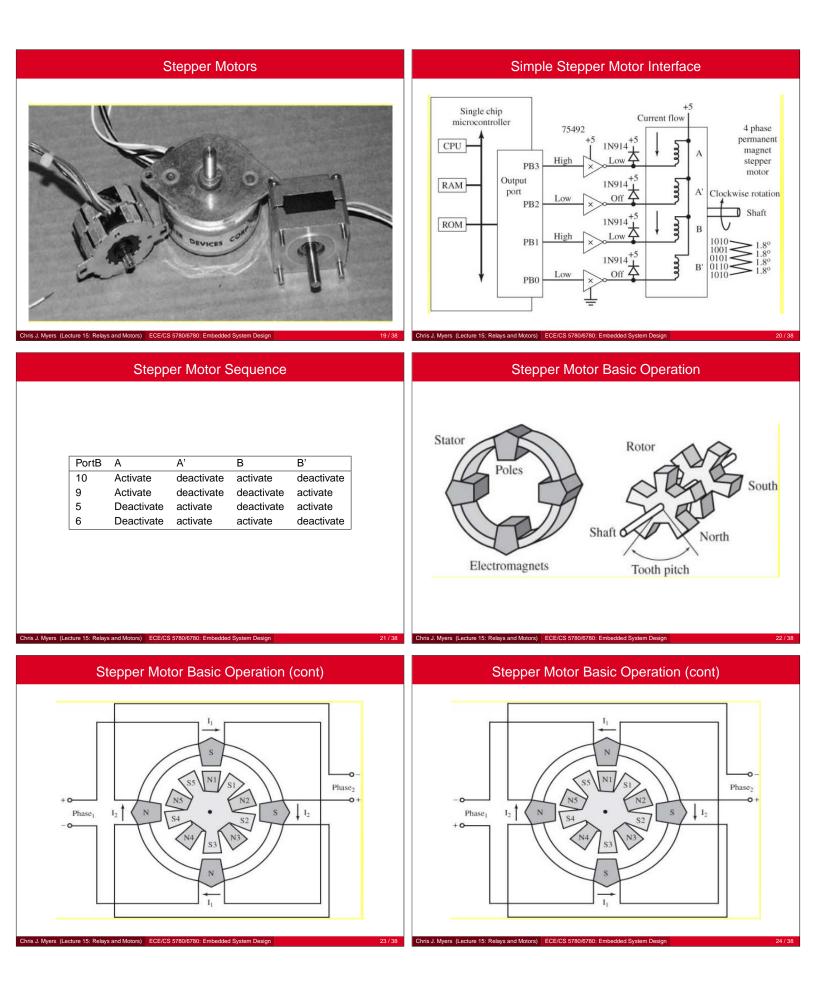
- Used in disk drives and printers.
- Can also be used as shaft encoders to measure both position and speed.



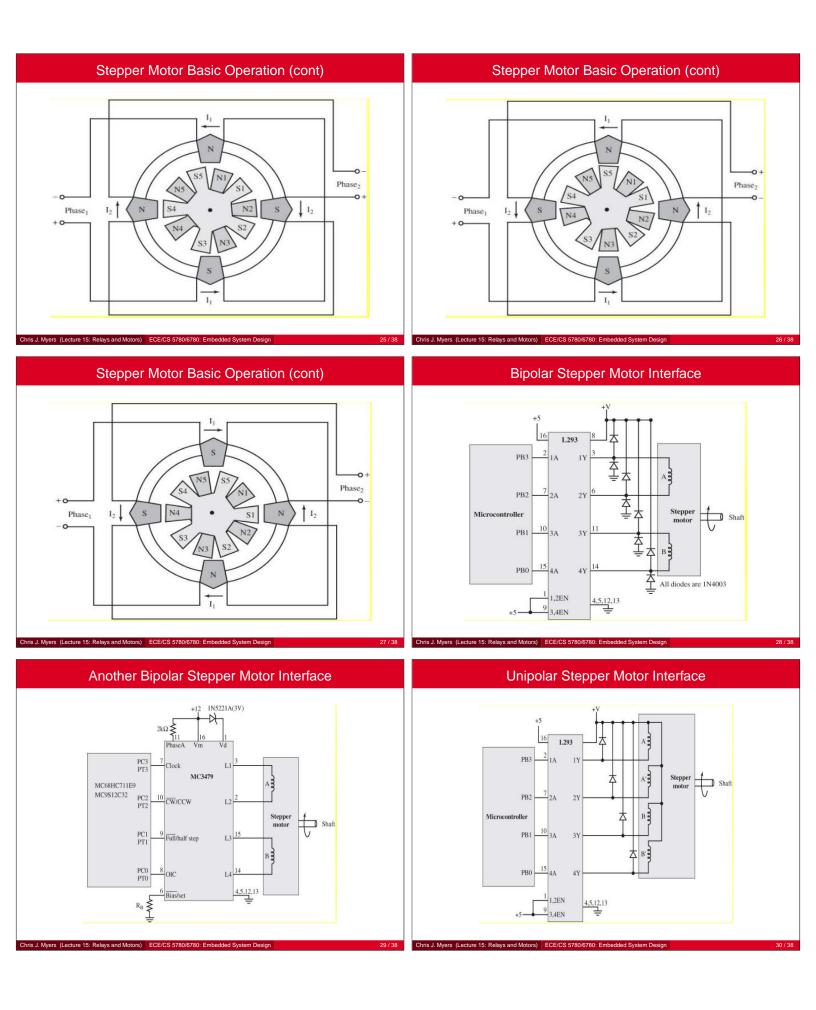

Slip

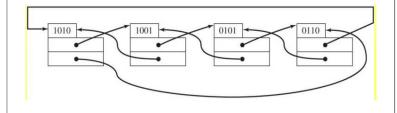- A *slip* is when computer issues a sequence change, but the motor does not move.
- Occurs if load on shaft exceeds available torque of motor.
- Can also occur if computer changes output too fast.
- If initial shaft angle known and motor never slips, computer can control shaft angle and speed without position sensor.



Chris J. Myers (Lecture 15: Relays and Motors) ECE/CS 5780/6780: Embedded System Design 31 / 38	Chris J. Myers (Lecture 15: Relays and Motors) ECE/CS 5780/6780: Embedded System Design 32 / 38
Data Structures to Control Stepper Motor	Ritual to Control Stepper Motor
<pre>const struct State{ unsigned char Out;</pre>	<pre>void Init(void){ Pos = 0; Pt = &fsm[0]; DDRB = 0xFF; }</pre>
Helper Functions to Control Stepper Motor	High-Level Control of Stepper Motor
<pre>void CW(void){ Pt = Pt->Next[clockwise]; // circular PORTB = Pt->Out; // step motor if(Pos==199){ // shaft angle Pos = 0; // reset }else{ Pos++;} // CW void CCW(void){ Pt = Pt->Next[counterclockwise]; PORTB = Pt->Out; // step motor if(Pos==0){ // shaft angle Pos = 199; // reset }else{ Pos;} // CCW</pre>	<pre>void Seek(unsigned char desired){ short CWsteps; if((CWsteps=desired-Pos)<0){ CWsteps+=200; } // CW steps is 0 to 199 if(CWsteps>100){ while(desired!=Pos){ CCW(); } } else{ while(desired!=Pos){ CW(); } } } Ctnist.Wyers (Lecture 15. Relays and Moters) ECE/CS 57806780: Embedded System Design 36/38 </pre>

