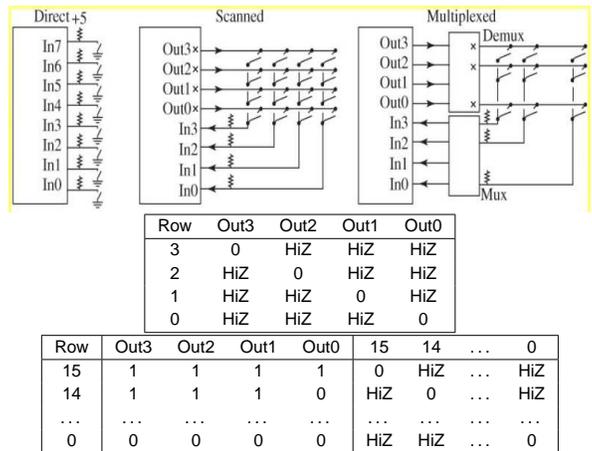


# ECE/CS 5780/6780: Embedded System Design


Chris J. Myers

Lecture 16: Keyboards and Displays


## Basic Approaches to Interfacing Multiple Keys




## Sixteen-Key Electronic Piano

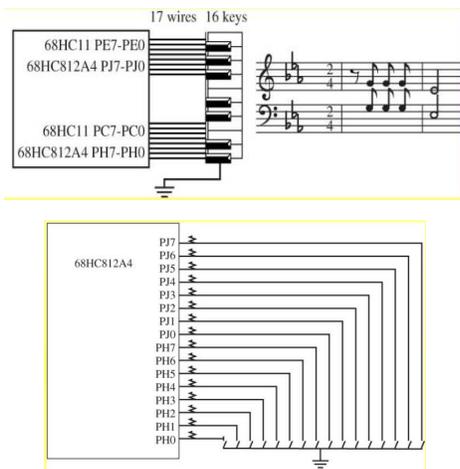

## Hardware for Generating Interrupts

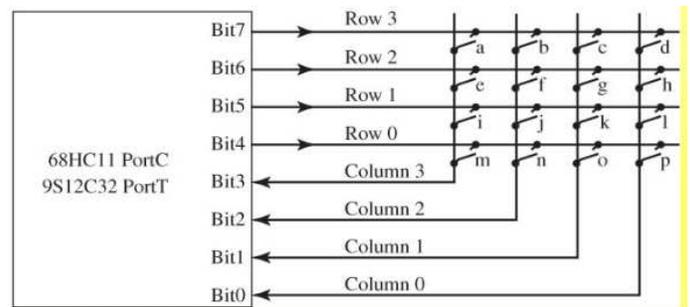
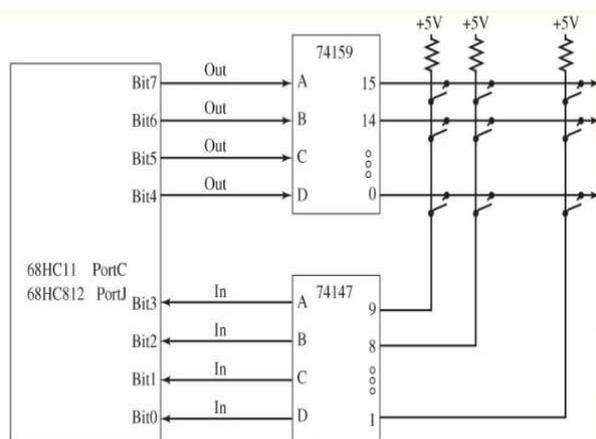
## Multiplexed/Demultiplexed Scanned Keyboard



## Software for Multiplexed Keyboard

```

unsigned char Key;           // current pattern
unsigned char PreviousKey;  // 10 ms ago
#define period 20000        // 10 ms
unsigned char KeyScan(void){
    unsigned char key,row;
    key=0;                  // means no key pressed
    for(row=0;row<16;row++){
        PORTJ=row<<4;      // Select row
        if((PORTJ&0x0F)!=0x0F){
            key=PORTJ^0x0F;
        }
    }
    return(key);
}
    
```

## Software for Multiplexed Keyboard (cont)

```
void Ritual(void){
    asm(" sei");           // make atomic
    DDRJ=0xF0;
    PreviousKey=Key=KeyScan(); // read
    TMSK1|=0x20;          // Arm OC5
    TIOS|=OC5;            // enable OC5
    TSCR|=0x80;           // enable
    TMSK2=0x32;          // 500 ns clock
    TC5=TCNT+wait;
    TFLG1=0x20;          // clear OC5F
    asm(" cli"); }


```

## Software for Multiplexed Keyboard (cont)


```
#pragma interrupt_handler TOC5handler()
void TOC5handler(void){
    unsigned char NewKey;
    NewKey=KeyScan(); // Current pattern
    if(NewKey!=PreviousKey) Key=NewKey;
    PreviousKey=NewKey;
    TOC5=TOC5+period;
    TFLG1=0x20; } // ack OC5F

```


## Interfacing Multiple LEDs

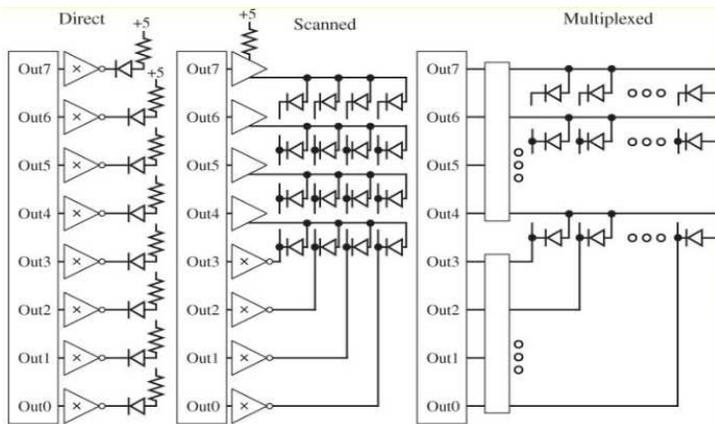

## Single LED Interface

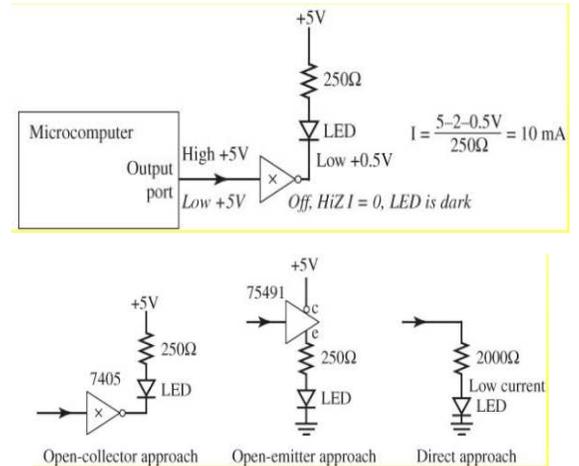

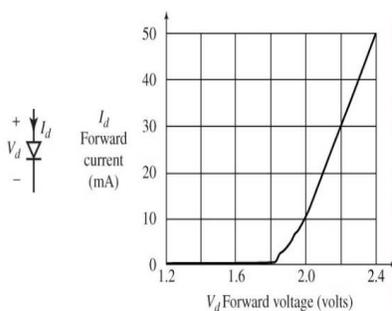
## Typical Voltage/Current Response of a LED




Parameter	red	green	yellow	orange	units
Max power	55	75	60	75	mW
Peak current	160	100	80	100	mA
Max current	25	25	20	25	mA


## Calculating the Resistor Value

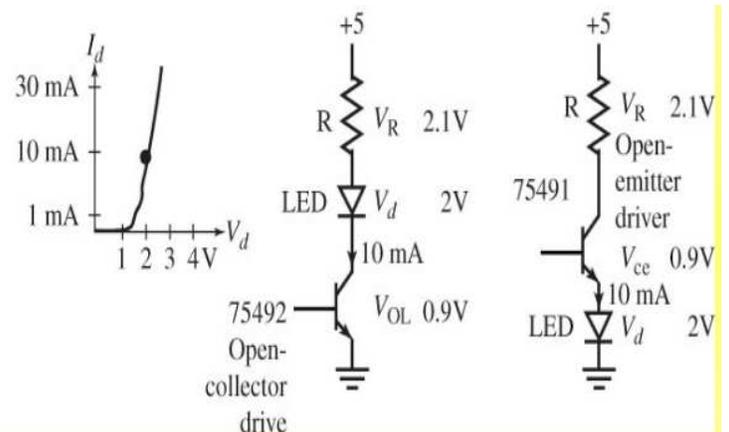


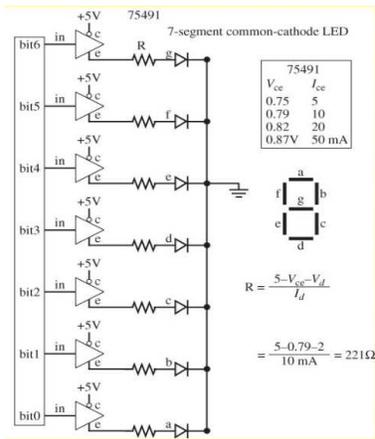
## Seven-Segment LED Interfaces (Common-Cathode)



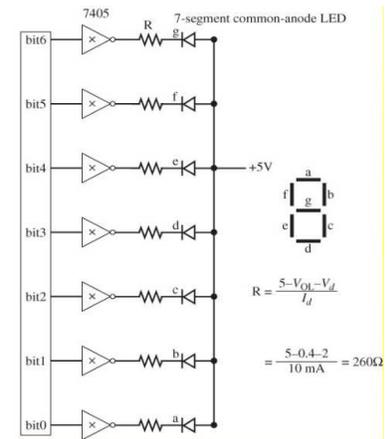
## Seven-Segment LED Interfaces (Common-Anode)



## Scanned Seven-Segment LED Interface

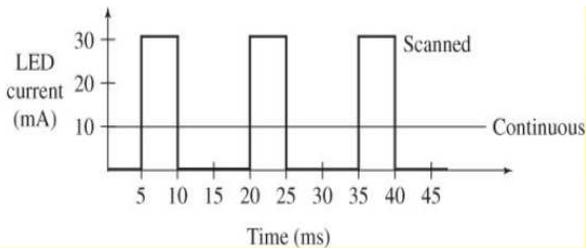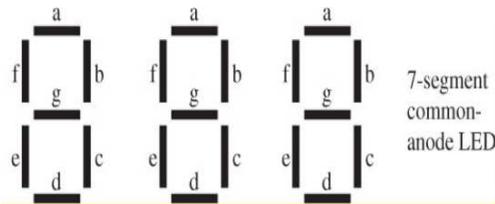

## Circuit Used to Scan a LED Interface

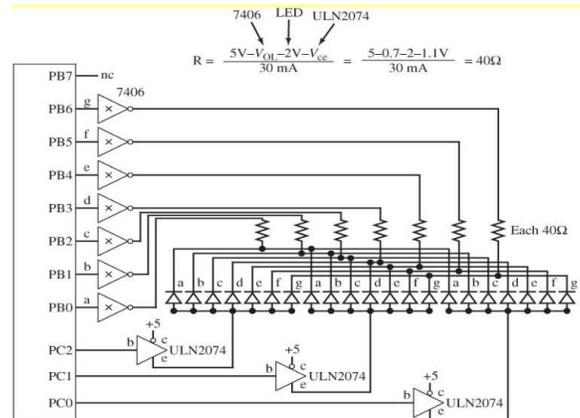

For MC9S12C32, replace PB with PT and PC with PM.


## Software for Scanned LED Display

```
// PT7-PT0 output, 7 bit pattern
// PM2-PM0 output, selects LED digit
unsigned char code[3]; // binary codes
static unsigned char select[3]={4,2,1};
unsigned short index; // 0,1,2
void LED_Init(void) {
asm sei // make atomic
index = 0;
DDRT = 0xFF; // outputs 7 segment code
DDRM |= 0x03; // outputs select LED
TIE |= 0x20; // Arm OC5
TIOS |= 0x20; // enable OC5
TSCR1 = 0x80; // enable
TSCR2 = 0x01; // 500 ns clock
TC5 = TCNT+10000;
asm cli }
```

## Software for Scanned LED Display

```
void interrupt 13 TC5handler(void){
TFLG1 = 0x20; // Acknowledge
TC5 = TC5+10000; // every 5 ms
PTM = select[index]; // which LED?
PTT = code[index]; // enable
if(++index==3) index=0;
asm(" cli"); }
```

## Scanned LED Interface Using Decoder

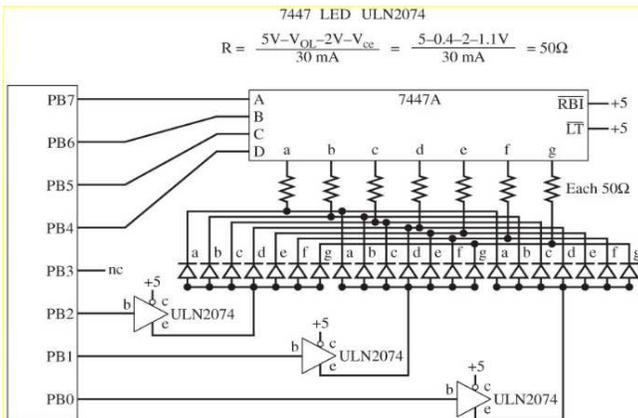

For MC9S12C32, replace PB with PT.

## Software for Multiplexed LED Display

```
unsigned short Global; // 12-bit packed BCD
const struct LED
{ unsigned char enable; // select
  unsigned char shift; // bits to shift
  const struct LED *Next; }; // Link
typedef const struct LED LEDType;
typedef LEDType * LEDPtr;
LEDType LEDTab[3]={
{ 0x04, 8, &LEDTAB[1] }, // Most sig
{ 0x02, 4, &LEDTAB[2] },
{ 0x01, 0, &LEDTAB[0] }}; // least sig
LEDPtr Pt; // Points to current digit
```

## Software for Multiplexed LED Display (cont)

```
void LED_Init(void) {
asm sei // make atomic
DDRT = 0xFF; // outputs to LED's
Global = 0;
Pt=&LEDTAB[0];
TIE |= 0x20; // Arm OC5
TIOS |= 0x20; // enable OC5
TSCR1 = 0x80; // enable
TSCR2 = 0x01; // 500 ns clock
TC5 = TCNT+10000;
asm cli }
```


## Software for Multiplexed LED Display (cont)

```
void interrupt 13 TC5handler(void){
TFLG1 = 0x20; // Acknowledge
TC5 = TC5+10000; // every 5 ms
PTT = (Pt->enable)
+(Global>>(pt->shift))<<4;
Pt = Pt->Next; }
```


## Extensions to Multiple Digits

- Two issues to consider as number of digits is increased:
  - Scan frequency - for display to "look" continuous, each digit must be updated faster than 60 Hz.
    - interrupt rate = 60 Hz × #digits
  - Duty cycle - this decreases as digits added, so must increase instantaneous current.
    - instantaneous current = desired current × #digits
- Ratio of maximum instantaneous current to desired LED current determines maximum number of digits.
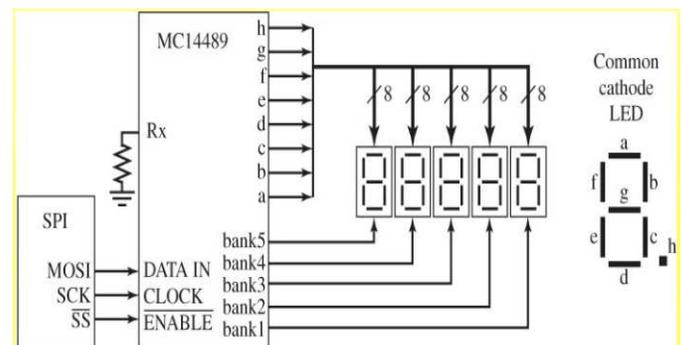
## Integrated IC Interface for LED Digits


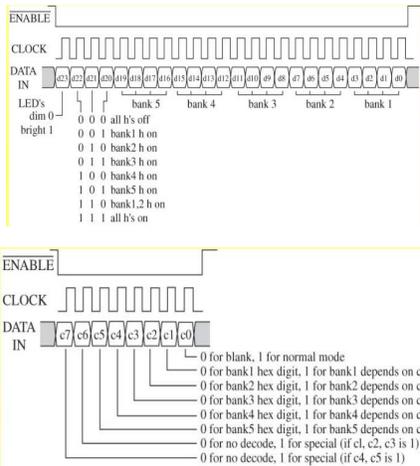
## Data Timing of Integrated LED Controller



## Software for Integrated LED Display

```
// PM4/MOSI = MC14489 DATA IN
// PM5/SCLK = MC14489 CLOCK IN
// PM3 (simple output) = MC14489 ENABLE
void LED_Init(void) {
    DDRM |= 0x38; // outputs to MC14489
    SPICR1 = 0x50;
    SPICR2 = 0x00; // regular drive
    SPIBR = 0x01; // 1MHz SCLK
    PTM |= 0x08; // ENABLE=1
    PTM &=~0x08; // ENABLE=0
    SPIDR= 0x01; // hex format
    while((SPISR&0x80)==0){};
    PTM |=0x08; // ENABLE=1
}
```


## Software for Integrated LED Display

```
void LED_out(unsigned char data[3]){
    unsigned char dummy;
    PTM &=~0x08; // ENABLE=0
    while((SPISR&SPTEF)==0); // wait for transmit empty
    SPIDR = data[2]; // send MSbyte
    dummy = SPIDR; // clear SPIF
    while((SPISR&SPTEF)==0); // wait for transmit empty
    SPIDR = data[1]; // send middle byte
    dummy = SPIDR; // clear SPIF
    while((SPISR&SPTEF)==0); // wait for transmit empty
    SPIDR = data[0]; // send LSbyte
    dummy = SPIDR; // clear SPIF
    Timer_Wait(10); // wait for SPI output completion
    PTM |=0x08; // ENABLE=1
}
```


## LCD Fundamentals

- LCD display consume less power than LED displays.
- LCDs are more flexible in sizes and shapes, allowing for combination of numbers, letters, words, and graphics.
- Uses liquid-crystal material that behaves as a capacitor.
- While LED converts electric power to emitted optical power, LCD uses AC voltage to change light reflectivity.
- Light energy is supplied by room or separate back light.
- Display controlled by altering reflectivity of each segment.
- Disadvantage is that they have slow response time, but typically fast enough for human perception.

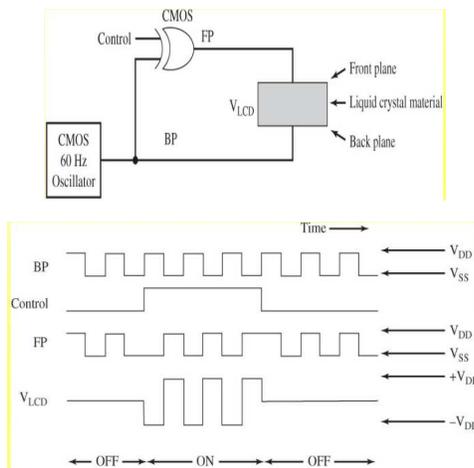
## Basic Idea of a Liquid Crystal Interface




## Direct Interface of a LCD

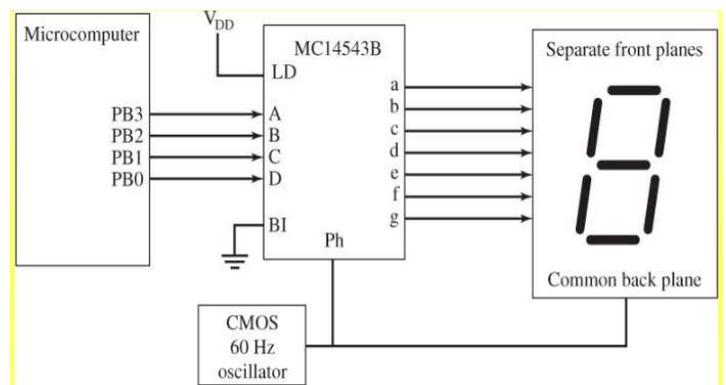

## Latched Interface of a LCD

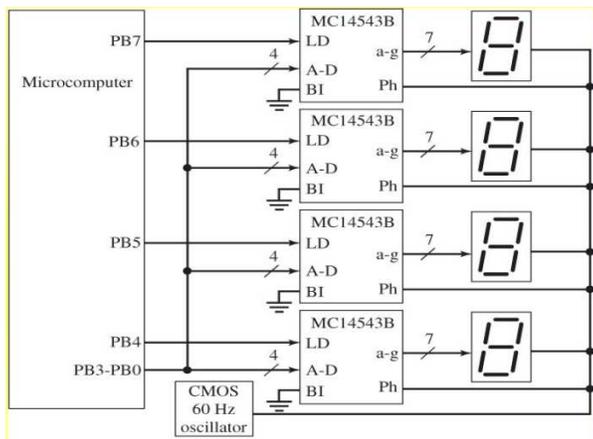

## Artwork for 8-Segment LCD Digits

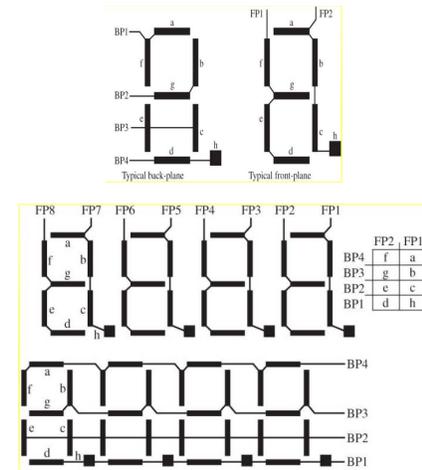

## Interface of a 48-Segment LCD Display

