

Introduction to Analog Interfacing


ECE/CS 5780/6780: Embedded System Design

Chris J. Myers

Lecture 17: Operational Amplifiers

- Most embedded systems include components that measure and/or control real-world parameters.
- These include position, speed, temperature, etc.
- Usually exist in a continuous, or analog, form.
- Often need to amplify, filter, and convert these signals to digital form.
- This chapter develops analog circuit building blocks for data acquisition and control systems.

Ideal Op Amps

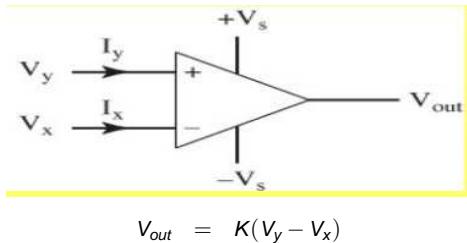


- Voltage ranges are bounded by the supply voltages, $\pm V_s$.
- Input currents, I_x and I_y , are zero.
- Negative feedback drives V_x to equal V_y .
- Positive feedback or no feedback drives V_{out} to equal $-V_s$ or $+V_s$.

Various Op Amps


Op amp	Description	Open loop gain	$\pm V_s$	$\pm I_s$
OPA4227	High Precision	160 dB	± 5 to ± 15 V	± 3.8 mA
OPA4132	High-Speed FET	130 dB	± 2.5 to ± 18 V	± 4.8 mA
TLC2274	Rail-to-Rail	104 dB	0 to 5 or ± 5 V	3 mA

Input Impedance

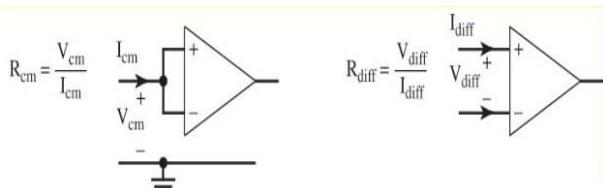


Op amp	R_{cm}	R_{diff}
OPA4227	1 G Ω	10 M Ω
OPA4132	10^{13} Ω	10^{13} Ω
TLC2274	10^{12} Ω	10^{12} Ω

Output Impedance

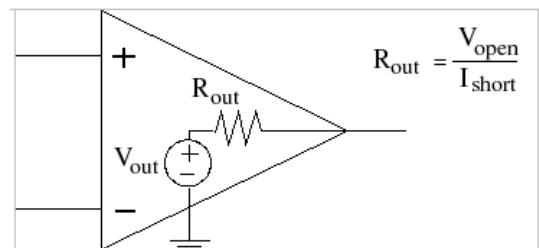


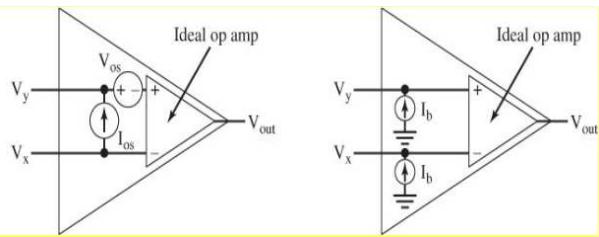Offset Voltage, Offset Current, and Bias Current




Op amp	V_{os}	I_{os}	I_b
OPA4227	0.075 mV	10 nA	10 nA
OPA4132	0.5 mV	50 pA	50 pA
TLC2274	3 mV	100 pA	100 pA

Noise Density

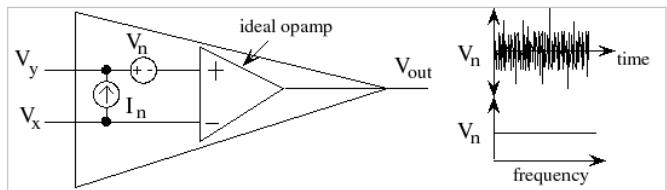


Op amp	e_n
OPA4227	3 nV/ $\sqrt{\text{Hz}}$
OPA4132	23 nV/ $\sqrt{\text{Hz}}$
TLC2274	50 nV/ $\sqrt{\text{Hz}}$

Transient Response

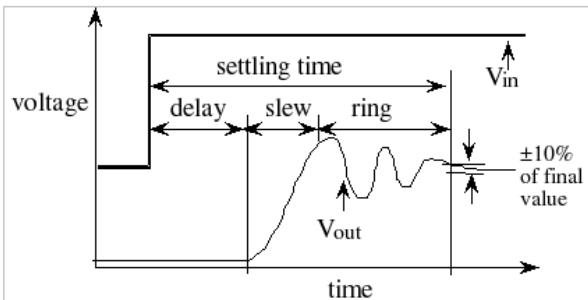

Op amp	dV/dt , Slew rate
OPA4227	2.3 V/ μs
OPA4132	20 V/ μs
TLC2274	3.6 V/ μs

Frequency Response

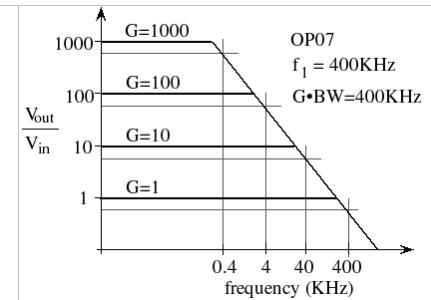

Op amp	f_1
OPA4227	8 MHz
OPA4132	8 kHz
TLC2274	2.18 MHz

Power Gain (A_{db})


- Combines voltage gain, input impedance, and output impedance.

$$P_{in} = \frac{V_{in}^2}{R_{in}}$$

$$P_{out} = \frac{V_{out}^2}{R_{out}}$$


$$A_{db} = 10 \log_{10} \frac{P_{out}}{P_{in}} = 20 \log_{10} \frac{V_{out}}{V_{in}} + 10 \log_{10} \frac{R_{in}}{R_{out}}$$

Threshold Detector

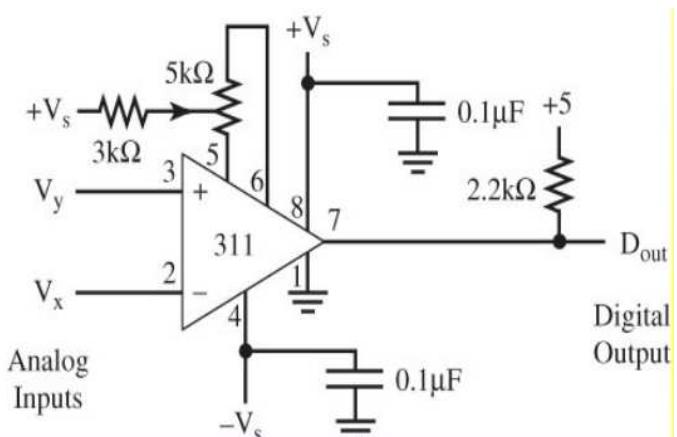

Simple Rules for Linear Op Amp Circuits

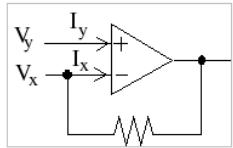
- Choose quality components.
- Negative feedback required to create linear mode circuit.



- Assume no current flows into the op amp inputs.
- Assume negative feedback equalizes input voltages.
- Choose resistor values in the $1\text{k}\Omega$ to $1\text{M}\Omega$ range.
- BW depends on the gain and the op amp performance.


Simple Rules for Linear Op Amp Circuits (cont)

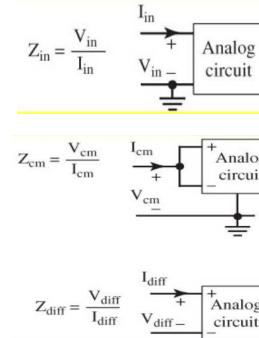- Equalize the effective resistance to ground at the two op amp inputs.
- Input impedance is input voltage / input current.




Simple Rules for Linear Op Amp Circuits (cont)

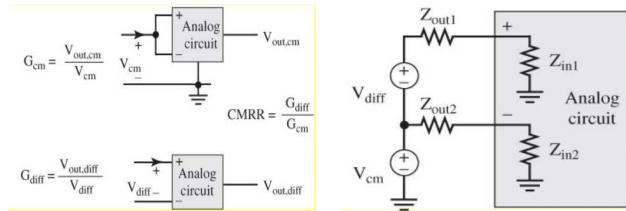
- Match input impedances to improve common-mode rejection ratio (CMRR).




Inverting Amplifier

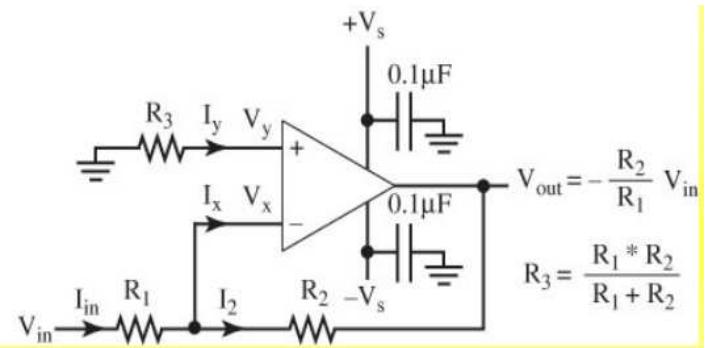

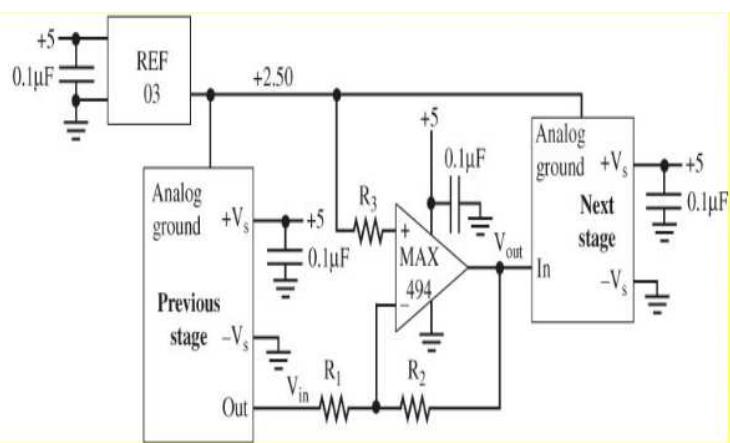Inverting Amplifier with -2.5V to 2.5V Range




Noninverting Amplifier

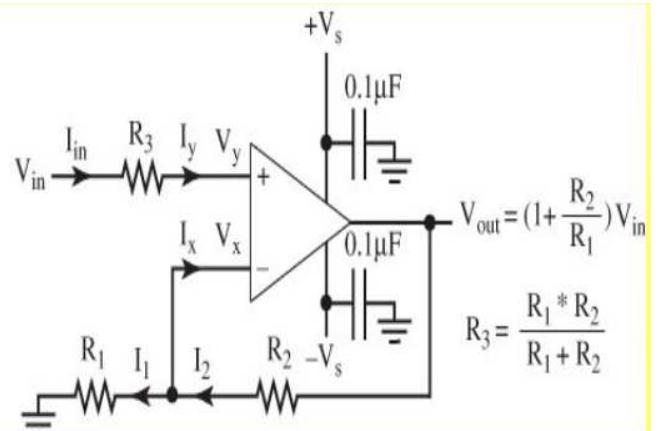

Model for Linear Circuit Design
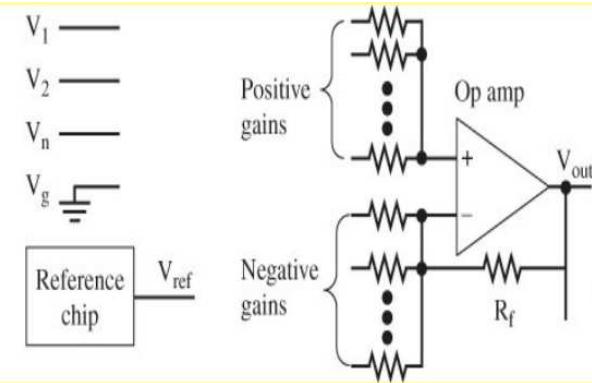
$$V_{out} = A_1 V_1 + A_2 V_2 + \dots + A_n V_n + B$$



Linear Circuit Design

$$V_{out} = 5V_1 - 3V_2 + 2V_3 - 10$$

- Choose a reference voltage from available reference voltage chips.

$$V_{ref} = 5V$$

- Rewrite the design equation in terms of the reference voltage, V_{ref} .

$$V_{out} = 5V_1 - 3V_2 + 2V_3 - 2V_{ref}$$

- Add a ground input to the equation such that the sum of the gains is 1.

$$V_{out} = 5V_1 - 3V_2 + 2V_3 - 2V_{ref} - V_g$$


- Choose a feedback resistor, R_f , in range of $10\text{ k}\Omega$ to $1\text{ M}\Omega$.

$$R_f = 150\text{ k}\Omega \quad R_1 = 30\text{ k}\Omega \quad R_2 = 50\text{ k}\Omega$$


$$R_3 = 75\text{ k}\Omega \quad R_{ref} = 75\text{ k}\Omega \quad R_g = 150\text{ k}\Omega$$

- Build the circuit: connect positive gain inputs to positive terminal and negative gain inputs to the negative terminal.


Linear Op Amp Circuit

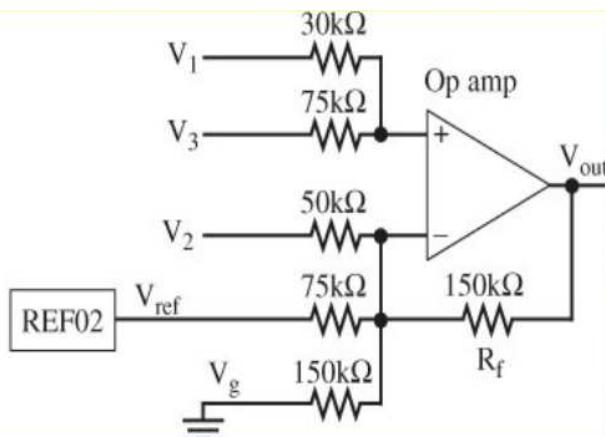


Instrumentation Amplifier

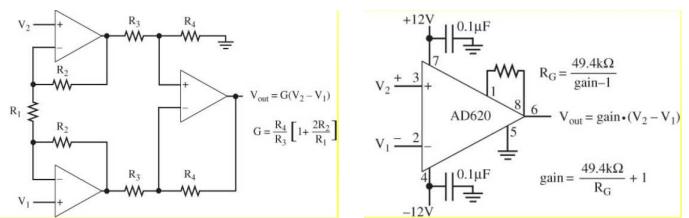


Current-to-Voltage Circuit

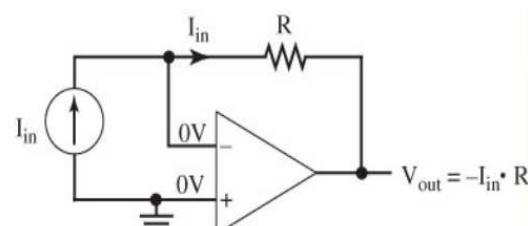


Voltage-to-Current Circuit

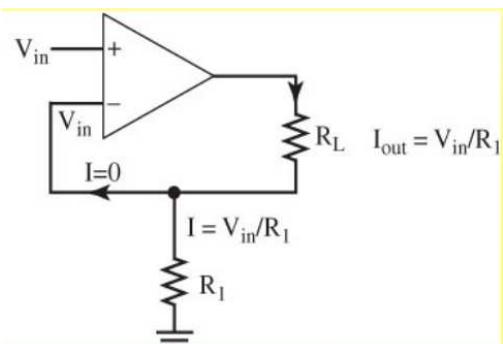


Integrator Circuit

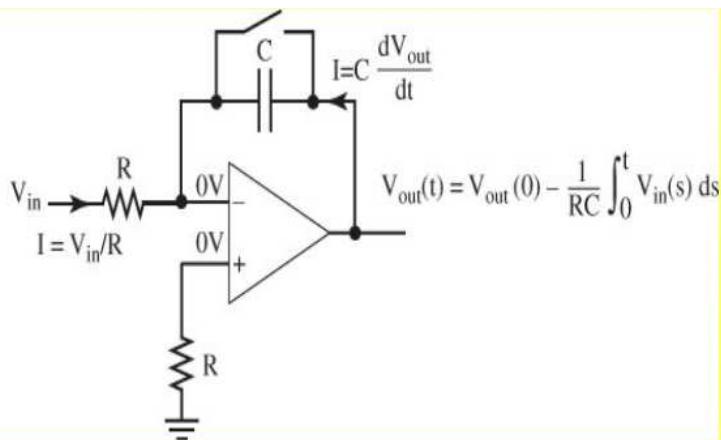


Derivative Circuit

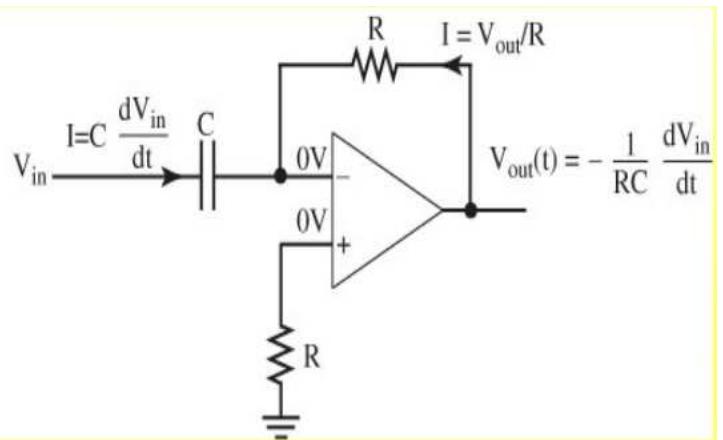

Hysteresis

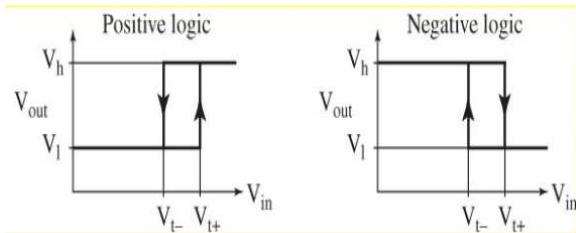

Voltage Comparators with Hysteresis

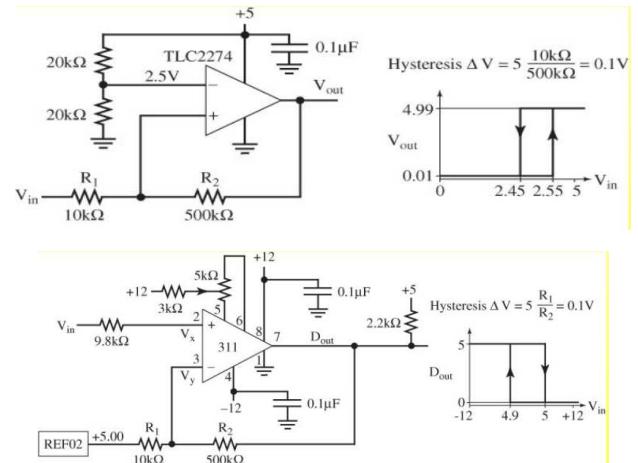

Analog Isolation

