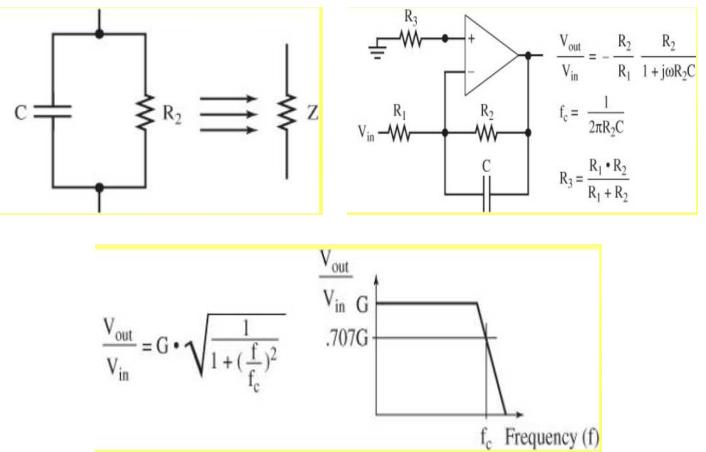


## ECE/CS 5780/6780: Embedded System Design


Chris J. Myers

Lecture 18: Analog Filters and DACs

## Simple Active Filter



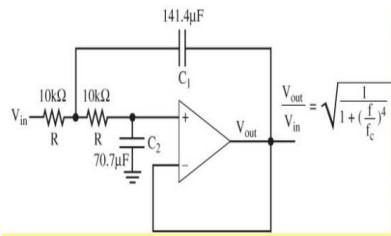
## Two-Pole Butterworth Low-Pass Analog Filter




- ① Select the cutoff frequency  $f_c$ .
- ② Divide the two capacitors by  $2\pi f_c$ .
- ③ Select standard capacitors with same order of magnitude.
- ④ Adjust resistors to maintain  $f_c$  (i.e.,  $R = 10k\Omega \cdot x$ ).


## Bandpass Filters

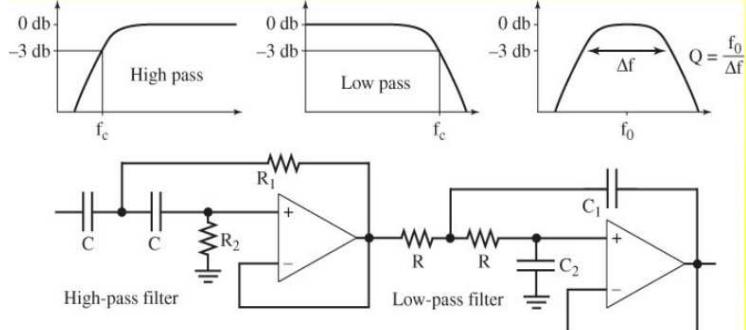

## Band-Reject Filters

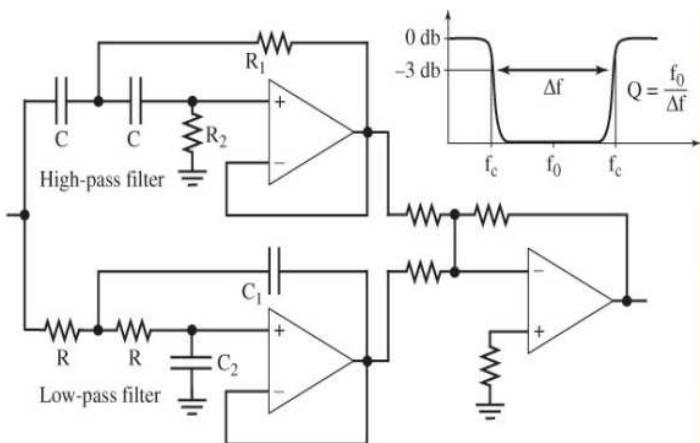


## Multiple Feedback Bandpass Filter

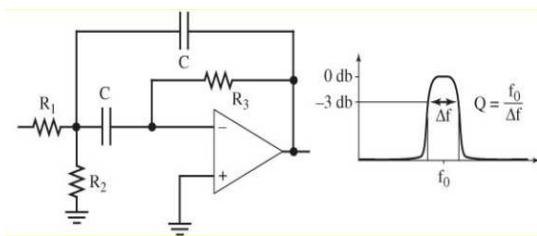

- ① Select a convenient capacitance value for the two capacitors.
- ② Calculate the three resistor values for  $x = 1/(2\pi f_0 C)$ .
- ③ Resistors should be in the 5kΩ to 5MΩ range. If not, repeat with different capacitance value.

## Digital-to-Analog Converters

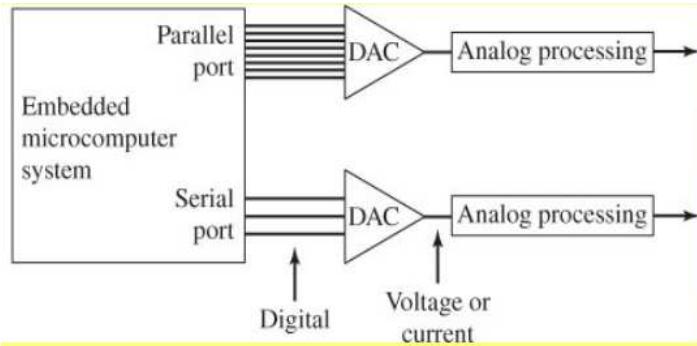

## DAC Parameters

- **Precision** is number of distinguishable DAC outputs.
- **Range** is maximum and minimum DAC output.
- **Resolution** is smallest distinguishable change in output.


$$\text{Range (volts)} = \text{Precision (alternatives)} \cdot \text{Resolution (volts)}$$

- **Accuracy** is (actual-ideal)/ideal.
- Two common encoding schemes:


$$V_{out} = V_{fs} \left( \frac{b_7}{2} + \frac{b_6}{4} + \frac{b_5}{8} + \frac{b_4}{16} + \frac{b_3}{32} + \frac{b_2}{64} + \frac{b_1}{128} + \frac{b_0}{256} \right) + V_{os}$$

$$V_{out} = V_{fs} \left( -\frac{b_7}{2} + \frac{b_6}{4} + \frac{b_5}{8} + \frac{b_4}{16} + \frac{b_3}{32} + \frac{b_2}{64} + \frac{b_1}{128} + \frac{b_0}{256} \right) + V_{os}$$

## Three-Bit DAC Examples

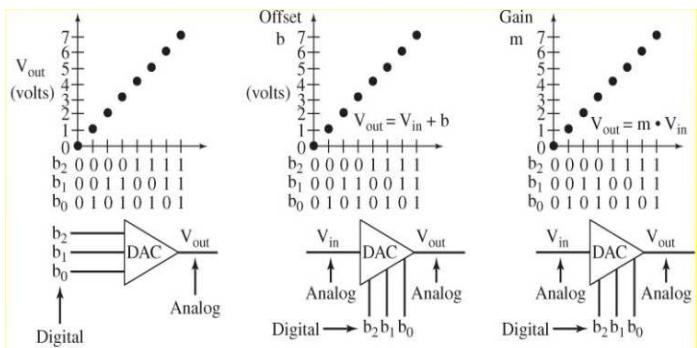



## DAC Performance Measures

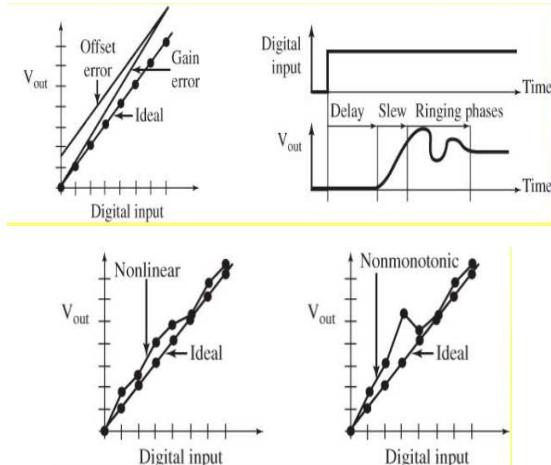

## DAC Errors: Sources and Solutions


Errors can be due to	Solutions
Incorrect resistor values	Precision resistors w/low tolerances
Drift in resistor values	Precision resistors w/good temperature coefficients
White noise	Reduce BW w/low pass filter, reduce temperature
Op amp errors	Use more expensive devices w/low noise and low drift
Interference from external fields	Shielding, ground planes

## DAC Using a Summing Amplifier

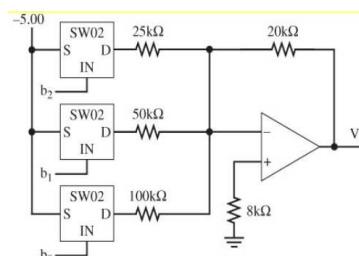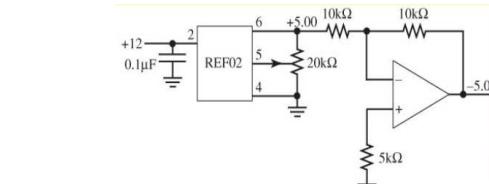


$b_2$	$b_1$	$b_0$	$V_{out}$
0	0	1	+1
0	1	0	+2
1	0	0	+4


### Three-Bit DAC with an R-2R Ladder

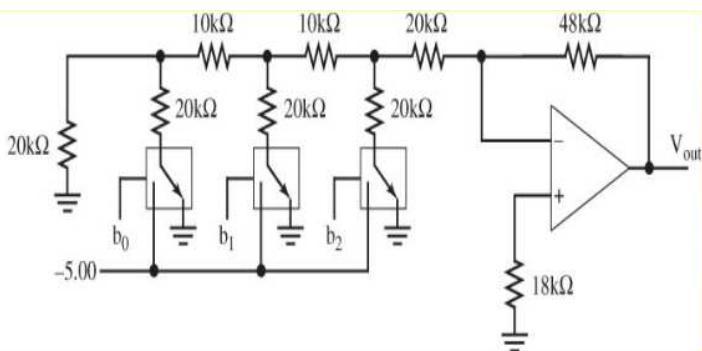


### Three-Bit DAC with an R-2R Ladder

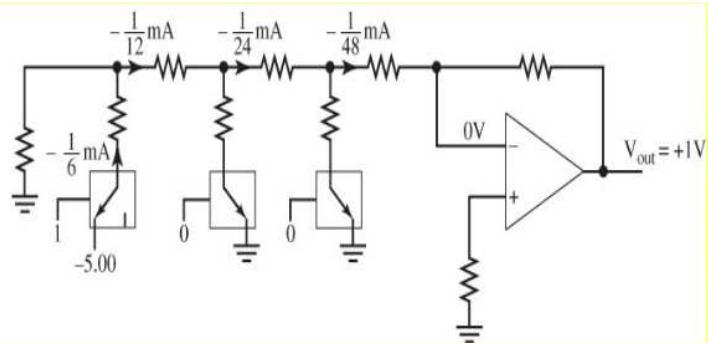


### Three-Bit DAC with an R-2R Ladder

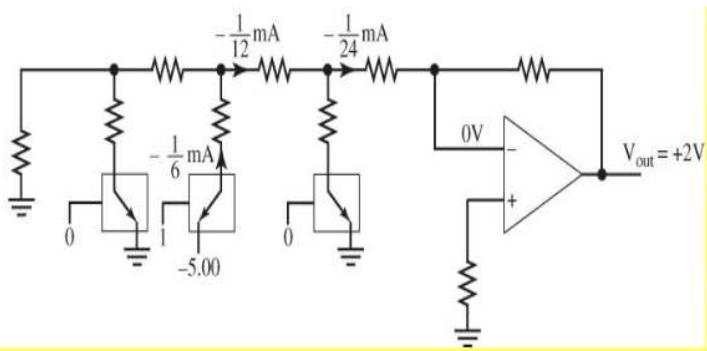


### Three-Bit DAC with an R-2R Ladder

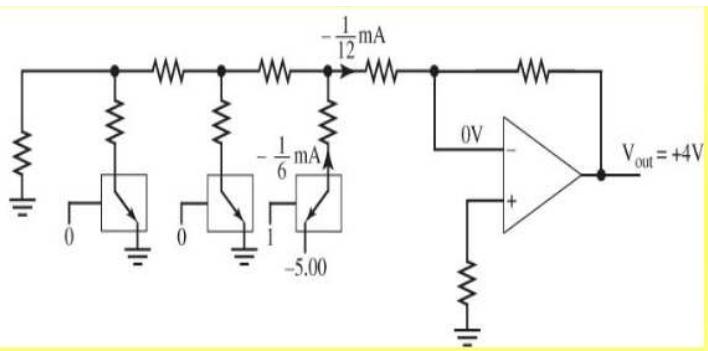
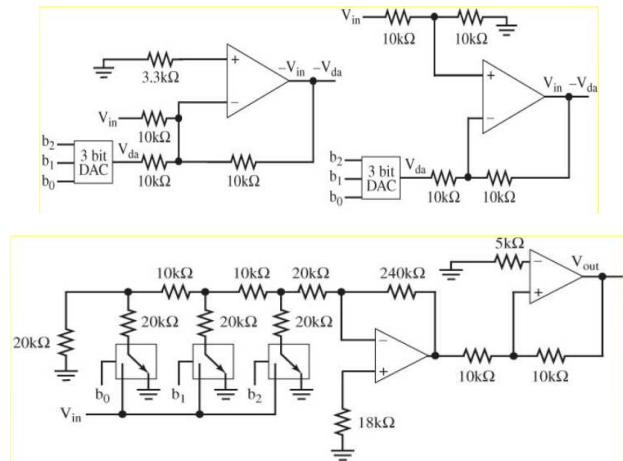
### Variable-Offset and Gain Using 3-bit DACs




### Twelve-Bit DAC with a DAC8043

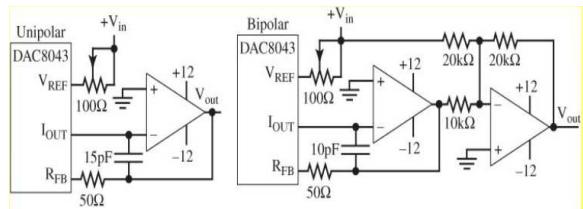

Digital Input	Unipolar $V_{out}$	Bipolar $V_{out}$	Unipolar gain	Bipolar gain
1111,1111,1111	-4.999	4.998	- $\frac{4095}{2^{12}}$	+ $\frac{2047}{2^{12}}$
1000,0000,0001	-2.501	0.002	- $\frac{2049}{2^{12}}$	+ $\frac{1}{2^{12}}$
1000,0000,0000	-2.500	0.000	- $\frac{2048}{2^{12}}$	+ $\frac{0}{2^{12}}$
0111,1111,1111	-2.499	-0.002	- $\frac{2047}{2^{12}}$	+ $\frac{-2048}{2^{12}}$
0000,0000,0001	-0.001	-4.998	- $\frac{1}{2^{12}}$	- $\frac{2047}{2^{12}}$
0000,0000,0000	0.000	-5.000	- $\frac{0}{2^{12}}$	- $\frac{2048}{2^{12}}$

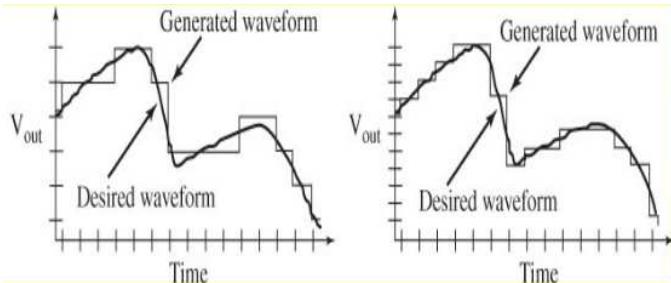
## DAC Selection: Precision, Range, and Resolution

- Affect quality of signal that can be generated.
- More bits means finer control over the waveform.
- Can be hard to specify a priori.



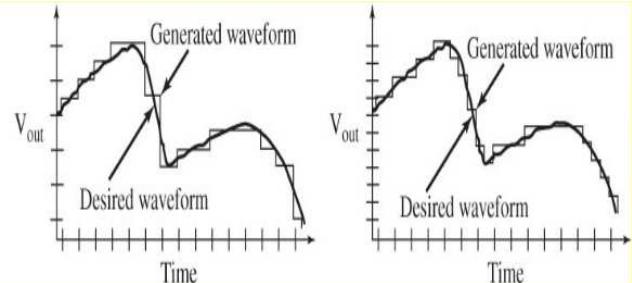
## DAC Selection: Channels, Configuration, and Speed

- Usually more efficient to implement multiple *channels* using a signal DAC.
- *Configuration*: can have voltage or current outputs, internal or external references, etc.
- *Speed* specified in many ways: *settling time*, *maximum output rate*, *gain/BW product*, etc.



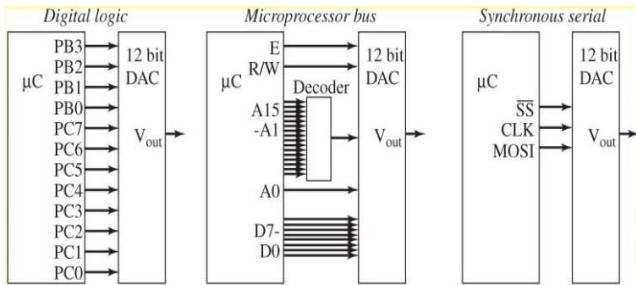
## DAC Selection: Power and Interface

- Three power issues: type of power required, amount of power required, and need for low-power sleep mode.
- Three approaches for interfacing exist:




## DAC Selection: Package and Cost

- Variety of packages exist:

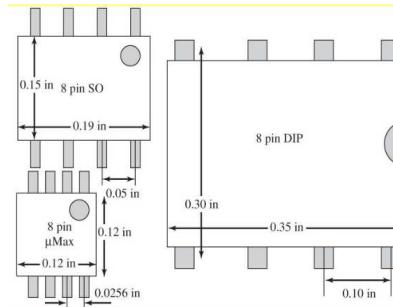

- Cost includes direct cost of components, power supply requirements, manufacturing costs, labor in calibration, and software development costs.

## DAC Waveform Generation

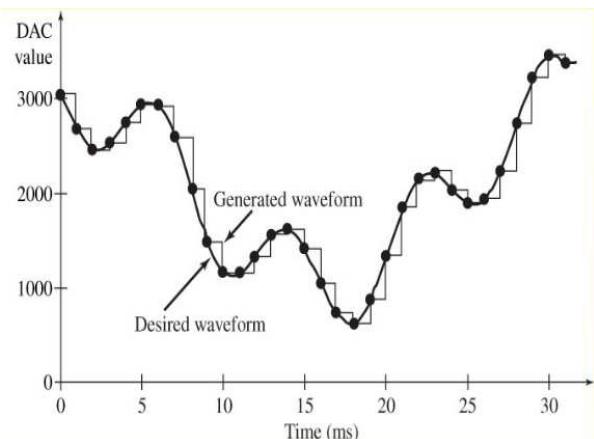


## Periodic Interrupt Used to Generate Waveform

```
unsigned short wave(unsigned short t){
    float result,time;
    time = 2*pi*((float)t)/1000.0;
    // integer t in msec into floating point time in seconds
    result = 2048.0+1000.0*cos(31.25*time)-500.0*sin(125.0*time);
    return (unsigned short) result;
}
#define RATE 2000
#define OC5 0x20
unsigned short Time; // Inc every 1ms
void interrupt 13 TOC5handler(void){
    TFLG1 = OC5; // ack C5F
    TC5 = TC5+RATE; // Executed every 1 ms
    Time++;
    DACout(wave(Time));
}
```

## Periodic Interrupt Used to Generate Waveform

```
unsigned short I; // incremented every 1ms
const unsigned short wave[32] = {
    3048, 2675, 2472, 2526, 2755, 2957, 2931, 2597,
    2048, 1499, 1165, 1139, 1341, 1570, 1624, 1421,
    1048, 714, 624, 863, 1341, 1846, 2165, 2206, 2048,
    1890, 1931, 2250, 2755, 3233, 3472, 3382};
#define RATE 2000
#define OC5 0x20
void interrupt 13 TOC5handler(void){
    TFLG1 = OC5; // ack C5F
    TC5 = TC5+RATE; // Executed every 1 ms
    if((++I)==32) I = 0;
    DACout(wave[I]);
}
```
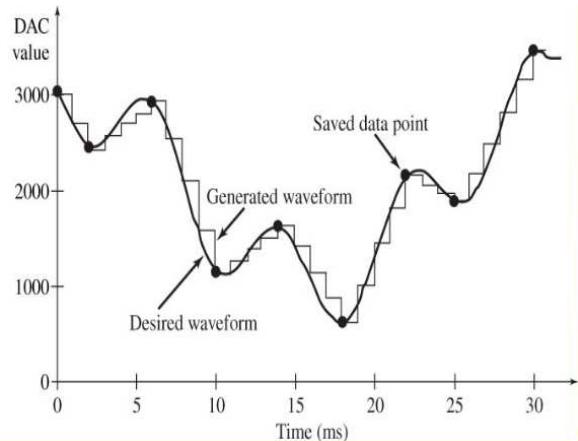
## Generated Waveform Using Linear Interpolation




## Periodic Interrupt Used to Generate Waveform

```
short I; // incremented every 1ms
short J; // index into these two tables
const short t[10] = {0, 2, 6, 10, 14, 18, 22, 25, 30, 32};
const short wave[10] = {3048, 2472, 2931, 1165, 1624,
                      624, 2165, 1890, 3472, 3048};
```

## Periodic Interrupt Used to Generate Waveform

```
#define RATE 2000
#define OC5 0x20
void interrupt 13 TOC5handler(void){
    TFLG1 = OC5; // ack C5F
    TC5 = TC5+RATE; // Executed every 1 ms
    if((++I)==32) {I=0; J=0;}
    if(I==t[J]){
        DACout(wave[J]);
    } else if (I==t[J+1]){
        J++;
        DACout(wave[J]);
    } else {
        DACout(wave[J]+((wave[J+1]-wave[J])
                         *(I-t[J]))/(t[J+1]-t[J])));
    }
}
```

## Generated Waveform Using Uneven-Time

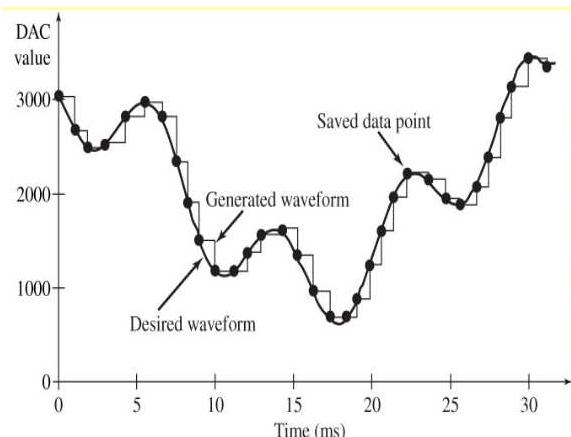

## Periodic Interrupt Used to Generate an Analog Waveform

```
unsigned short I; // incremented every sample
const unsigned short wave[32] = {
    3048, 2675, 2472, 2526, 2817, 2981, 2800, 2337, 1901, 1499, 1165,
    1341, 1570, 1597, 1337, 952, 662, 654, 863, 1210, 1605, 1950,
    2202, 2141, 1955, 1876, 2057, 2366, 2755, 3129, 3442, 3382};
const unsigned short dt[32] = { // 500 ns cycles
    2000, 2000, 2000, 2500, 2000, 2000, 1500, 2000, 4000,
    2000, 2500, 2000, 2000, 2000, 1500, 1500, 1500, 2000,
    2500, 2000, 2000, 1500, 1500, 1500, 2000, 2500, 2000};
#define OC5 0x20
void interrupt 13 TOC5handler(void){
    TFLG1 = OC5; // ack C5F
    if((++I)==32) I=0;
    TC5 = TC5+dt[I]; // variable rate
    DACout(wave[I]);
}
```