# ECE/CS 5780/6780: Embedded System Design

#### Chris J. Myers

Lecture 19: Analog-to-Digital Conversion

Chris J. Myers (Lecture 19: ADCs

ECE/CS 5780/6780: Embedded System Design

1 / 34

## **ADC Parameters**

- Precision is number of distinguishable ADC inputs.
- Range is maximum and minimum ADC inputs.
- Resolution is change in input that causes digital output to change by 1.

Range (volts) = Precision (alternatives) · Resolution (volts)

- Accuracy usually given for entire instrument (including transducer, analog circuit, ADC, and software).
- ADC is monotonic if it has no missing codes.
- ADC is *linear* if resolution is constant through the range.
- ADC speed is time to convert.

hris J. Myers (Lecture 19: ADCs)

E/CS 5780/6780: Embedded System Design

# Common Encoding Schemes

Unipolar codes	Straight binary	Complementary binary		
+5.00	1111,1111	0000,0000		
+2.50	1000,0000	0111,1111		
+0.02	0000,0001	1111,1110		
+0.00	0000,0000	1111,1111		


Bipolar codes	Offset binary	2s Complement binary		
+5.00	1111,1111	0111,1111		
+2.50	1100,0000	0100,0000		
+0.04	1000,0000	0000,0001		
+0.00	1000,0000	0000,0000		
-2.50	0100,0000	1100,0000		
-5.00	0000,0000	1000,0000		

Chris J. Myers (Lecture 19: ADC:

ECE/CS 5780/6780: Embedded System Design

2/34

# Two-Bit Flash ADC

 


V <sub>in</sub>	Х3	X2	X1	Z1	Z0
2.5 > V <sub>in</sub>	0	0	0	0	0
$5.0 > V_{in} \ge 2.5$	0	0	1	0	1
$7.5 > V_{in} \ge 5.0$	0	1	1	1	0
$V_{in} \geq 7.5$	1	1	1	1	1

Chris J. Myers (Lecture 19: ADCs)

ECE/CS 5780/6780: Embedded System Design


4/3

#### Successive Approximation ADC

 

ECE/CS 5780/6780: Embedded System Desi

### Sixteen-Bit Dual Slope ADC

 


Chris J. Myers (Lecture 19: ADCs)

E/CS 5780/6780: Embedded System Design

6/34
 
#### Waveforms During Dual Slope ADC Conversion



#### $V_{out}(t_0) = 0$

$$t_{ref} = t_1 - t_0 = 65,535 \mu s$$

$$V_{out}(t_1) = V_{out}(t_0) - \frac{1}{RC} \int_{t_0}^{t_1} V_{in}(s) ds = -\frac{1}{RC} V_{in}t_{ref}$$

$$V_{out}(t_2) = 0$$

$$t_{in} = t_2 - t_1$$

$$V_{out}(t_2) = V_{out}(t_1) - \frac{1}{RC} \int_{t_1}^{t_2} V_{ref}(s) ds = V_{out}(t_1) - \frac{1}{RC} V_{ref}t_{in} = 0$$

**Dual Slope ADC Conversion: Theory** 

$$0 = -\frac{1}{PC}V_{in}t_{ref} - \frac{1}{PC}V_{ref}t_{in}$$


$$0 = V_{in}t_{ref} + V_{ref}t_{in}$$

$$0 = -\frac{1}{RC} V_{in} t_{ref} - \frac{1}{RC} V_{ref} t_{in}$$

$$0 = V_{in} t_{ref} + V_{ref} t_{in}$$

$$V_{in} = -V_{ref} \frac{t_{in}}{t_{ref}} = 10 V \frac{t_{in}}{65,535 \mu s}$$

# Sigma Delta ADC

 


# Software Implementation of Sigma Delta ADC


unsigned char DOUT; // 8-bit sample unsigned char SUM; // number of times Z=0 and V0=1 unsigned char CNT; // 8-bit counter void interrupt 13 TOC5handler(void){ TFLG1 = OC5;// ack C5F TC5 = TC5+rate; // interrupt 256 times faster // check input if(Z()) // too high, set D/A output, V0=0 DACout(0); else { DACout(1); // too low, set D/A output, V0=+5v SUM++; if(++CNT==0){ // end of 256 loops? DOUT = SUM; // new sample SUM = 0;// get ready for the next }}

ECE/CS 5780/6780: Embedded System Design

#### **ADC Interface**

 

Sample and Hold

 



- Should use polystyrene capacitor because of its high insulation resistance and low dielectric absorption.
- A larger value of C decreases (improves) droop rate. If droop current is  $I_{DR}$ , then droop rate is:


$$\frac{dV_{out}}{dt} = \frac{I_{DR}}{C}$$

A smaller C decreases (improves) acquisition time.

 
Chris J. Myers (Lecture 19: ADCs) ECE/CS 5780/6780: Embedded System Design



 

 

 Chris J. Myers (Lecture 19: ADCs) ECE/CS 5780/6780: Embedded System De:




ECE/CS 5780/6780: Embedded System De

#### ADC Interrupt Software Without S/H One channel One channel Two channels (Interrupt) (Interrupt) (Interrupt) Wait for Mux to settle Read ADC result Start ADC Start ADC Start ADC Save result ADC ADC ADC done? done? done? Yes Yes Yes Start ADC Read ADC result Read ADC result Read ADC result (RTI) Save result Save result Save result (RTI) Set Mux to channel 2 Set Mux to channel

(RTI)

ADC Interrupt Software With S/H One channel Two channels Interrupt Wait for S/H and Mux to settle Interrupt Set S/H to hold Set S/H to hold Set S/H to hold Start ADC Start ADC Start ADC No ADC ADC ADC done? Yes done? Yes Yes Read ADC result 1 Read ADC result 2 Save result 2 Save result Save result 1 Set S/H to sample Set S/H to sample Set S/H to sample RTI Set Mux to channel 2 Set Mux to channel 1 (RTI)
 
#### Power and Grounding for the ADC System



#### Internal ADCs

- 6812 has built-in ADCs with following features:
  - Eight-channel operation.
  - 8-bit or 10-bit resolution.
  - Successive approximation conversion technique.
  - Clock and charge pump to create higher voltages.
  - Two operation modes: single sequence of conversions then stop, and continuous conversion.
  - Supports multiple conversion of single channel, and one conversion each for group of channels.
  - ullet External  $V_{RH},\ V_{RL}$  analog high/low references.

Chris J. Myers (Lecture 19: ADCs)


ECE/CS 5780/6780: Embedded System Design

22 / 34

#### 6812 ADC System: Conversions

- When ADC is triggered, it performs 1 to 8 conversions.
- Number of conversions is selected by the value written into the S8C, S4C, S2C, and S1C bits of ATDCTL3 (values of 0, 8-15 are all 8).
- The channel used is selected by the CC, CB, CA bits of ATDCTL5.
- All conversions can be on one channel or on multiple channels if MULT in ATDCTL5 is set (channel sequence determined by S8C, S4C, S2C, S1C).
- ATDSTAT0 register:
  - SCF flag in ATDSTAT0 is set to 1 when conversion is complete.
  - CC2, CC1, and CC0 bits are a counter to show conversion progress.
- ATDSTAT1 register contains CCFn flag bits for each conversion.
 
#### Input Protection for CMOS Analog Inputs



# 6812 ADC System: Setup

- 8 pins of Port AD can be individually configured as analog or digital inputs using the ATDDIEN register (1 for digital, 0 for analog).
- If pin is digital, DDRAD register is used to set pins direction.
- Can use 8-bit or 10-bit resolution which is selected by setting the SRES8 bit (1=8-bit) in the ADTCTL4 register
- ATDCTL2 register:
  - ADC system is enabled by setting ADPU to 1.
  - Interrupts are enabled by setting ASCIE to 1.
  - ASCIF flag is set 1 when conversion sequence is complete, if ASCIE is 1.

Chris J. Myers (Lecture 19: ADCs

FCF/CS 5780/6780: Embedded System Design

23 / 34

#### 6812 ADC System: Triggers

- Conversion can be triggered in three ways:
  - Writing to ATDCTL5 and when done SCF bit in ATDSTAT0 is set.
  - Trigger continuously if SCAN in ATDCTL5 is set.
  - Using an external trigger connected to PAD7.
- External trigger enabled when ETRIGE bit in ATDCTL2 is set.

ETRIGLE	ETRIGP	External trigger mode
0	0	Falling edge of PAD7
0	1	Rising edge of PAD7
1	0	Convert while PAD7 is low
1	1	Convert while PAD7 is high

Chris J. Myers (Lecture 19: ADCs) ECE/CS 5780/6780: Embedded System Desi

24 / 34

s J. Myers (Lecture 19: ADCs) ECE/CS 5780/6780: Embedded Syste

25 / 34

#### 6812 ADC System: Sample Period

- Determined by ATDCTL4 register and E clock.
- Sample done in two phases:
  - Phase one transfers sample to ADC's storage node.
  - Phase two attaches external analog signal to the storage node.

SMP1	SMP0	First sample	Second sample	Total
0	0	2 ADC clocks	2 ADC clocks	4 ADC clocks
0	1	2 ADC clocks	4 ADC clocks	6 ADC clocks
1	0	2 ADC clocks	8 ADC clocks	10 ADC clocks
1	1	2 ADC clocks	16 ADC clocks	18 ADC clocks

• If m is 5-bit number formed by PRS4-0 and  $f_E$  is E clock frequency:

ATD clock frequency 
$$= \frac{1}{2} \frac{f_E}{(m+1)}$$

Chris J. Myers (Lecture 19: ADCs

ECE/CS 5780/6780: Embedded System Desig

26 / 34

# 6812 ADC System: Binary Formats


- Results returned in the 16-bit ATDDR0 to ATDDR7 registers.
- 10-bit results can unsigned or signed (DSGN=1 in ATDCTL5).
- Results can be left or right justified (DJM=1 in ATDCTL5).

	Input (V)	8-bit(u)	10-bit(ur)	10-bit (ul)	10-bit (sr)	10-bit (sl)
	0.000	\$00	\$0000	\$0000	\$FE00	\$8000
	0.005	\$00	\$0001	\$0040	\$FE01	\$8040
	0.020	\$01	\$0004	\$0100	\$FE04	\$8100
	2.500	\$80	\$0200	\$8000	\$0000	\$0000
	3.750	\$C0	\$0300	\$C000	\$0100	\$4000
	5.000	\$FF	\$03FF	\$FFC0	\$01FF	\$7FC0

Chris J. Myers (Lecture 19: ADCs)

E/CS 5780/6780: Embedded System Design

# **ADC Example**

 

Chris J. Myers (Lecture 19: ADC

FCF/CS 5780/6780: Embedded System Desig

28 / 34

#### **ADC Software**

```
void ADC_Init(void){
  ATDCTL2 = 0x80; // enable ADC
  ATDCTL3 = 0x08;
  ATDCTL4 = 0x05; // 10-bit, divide by 12
}
unsigned short ADC_In(unsigned short chan){
  ATDCTL5 = (unsigned char)chan; // start sequence while((ATDSTAT1&0x01)==0){}; // wait for CCF0 return ATDDR0;
}
```


Chris J. Myers (Lecture 19: ADCs)

CE/CS 5780/6780: Embedded System Design

Computing a Derivative

30 / 34

#### Multiple-Access Circular Queue

 



Chris J. Myers (Lecture 19: ADCs) ECE/CS 5780/67

ECE/CS 5780/6780: Embedded System Design

Simple approach:

$$d(n) = \frac{x(n) - x(n-1)}{\Delta t}$$

Approach that is more robust to noise:

$$d(n) = \frac{x(n) - 3x(n-1) - 3x(n-2) - x(n-3)}{\Delta t}$$

Chris J. Myers (Lecture 19: ADCs)

C/CS 5780/6780: Embedded System Design

32 / 34

# Software for First Derivative Using a MACQ

```
#define RATE 2000
#define OC5 0x20
unsigned short x[4]; // MACQ (mV)
unsigned short d; // derivative (V/s)
void interrupt 13 TOC5handler(void){
 TC5 = TC5+RATE;  // Executed every 1 ms
 TFLG1 = 0x20;
                    // ack OC5F
                 // shift MACQ data
// units of mV
 x[3] = x[2];
 x[2] = x[1];
 x[1] = x[0];
 x[0] = ADC_In(0x85); // current data, from Channel 5
 d = x[0]+3*x[1]-3*x[2]-x[3]; // mV/ms
```

Chris J. Myers (Lecture 19: ADCs) ECE/CS 5780/6780: Embedded System Design