

ECE/CS 5780/6780: Embedded System Design


Chris J. Myers

Lecture 20: Memory Interfacing


Introduction

- Most embedded systems use only the memory built-in to the microcontroller.
- Memory interfacing and bus timing is important to understanding internal microcontroller architecture.
- Sometimes internal memory insufficient, and external memory needed.
- Sometimes external devices are interfaced using memory-mapped I/O.


Memory-Mapped I/O

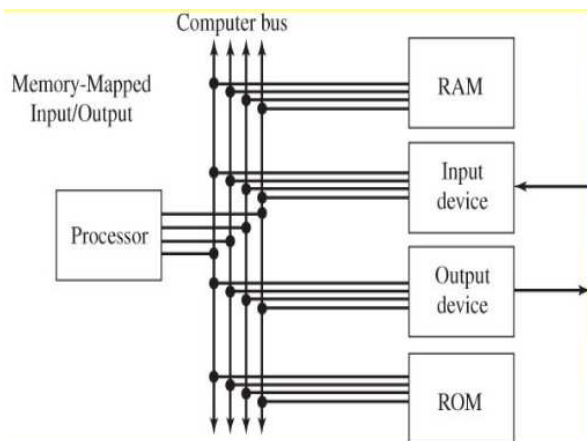

Isolated I/O

 


Expanded Mode

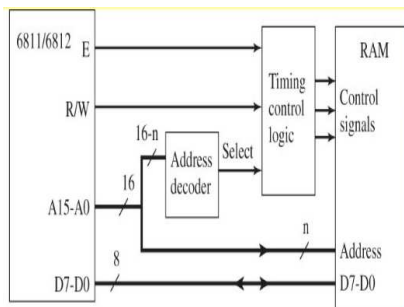

Select	R/W	Function
0	0	Off
0	1	Off
1	0	Write
1	1	Read

Multiplexed Address and Data Lines

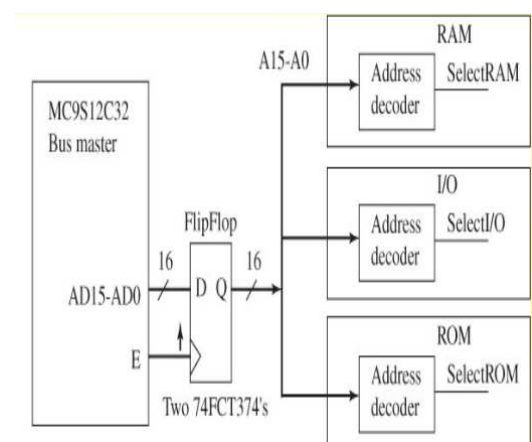


Full-Address Decoding

- Slave selected only when slave's address is on the bus.
- Design using the following steps:
 - 1 Write specified address using 0,1,X:


0100, 00XX, XXXX, XXXX for 1K RAM at \$4000-\$43FF
 - 2 Write equation using all 0s and 1s:

$$select = \overline{A15} \cdot A14 \cdot \overline{A13} \cdot \overline{A12} \cdot \overline{A11} \cdot \overline{A10}$$
 - 3 Build circuit using gates.

 Address Decoder for 1K RAM at \$4000-\$43FF



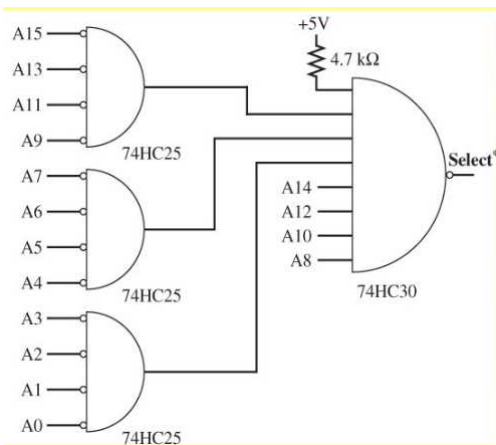An Address Decoder for I/O Device at \$5500




Minimal-Cost Address Decoding

- Use don't cares for unspecified addresses to simplify.
- Example:

4K RAM	\$0000 to \$0FFF	0000, XXXX, XXXX, XXXX
Input	\$5000	0101, 0000, 0000, 0000
Output	\$5001	0101, 0000, 0000, 0001
16K ROM	\$C000 to \$FFFF	11XX, XXXX, XXXX, XXXX

RAM			ROM			Input			Output		
A15	A14	A0	A15	A14	A0	A15	A14	A0	A15	A14	A0
0	0	1	0	0	0	0	0	0	0	0	0
0	1	0	0	1	0	0	1	0	0	1	0
1	1	0	1	1	1	1	1	0	1	1	0
1	0	X	1	0	X	1	0	X	1	0	X

An Address Decoder

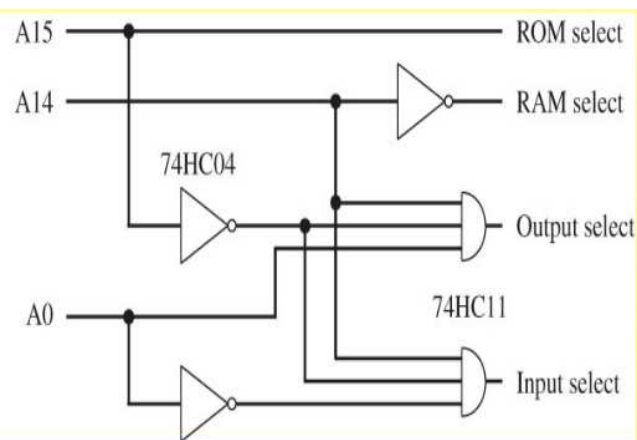



Karnaugh Maps

Cheaper			Safer			Expandable		
A15	A14	A0	A15	A14	A0	A15	A14	A0
0	0	RAM	0	0	RAM	0	0	RAM
0	1	In	0	1	Out	0	1	In
1	1	ROM	1	1	ROM	1	1	ROM
1	0	X	1	0	X	1	0	X

Special Cases


- Size of the memory is not a power of 2.
 - 20K RAM with address range \$0000 to \$4FFF
 - 00XX, XXXX, XXXX, XXXX Range \$0000 to \$3FFF
 - 0100, XXXX, XXXX, XXXX Range \$4000 to \$4FFF
- Start address divided by memory size not an integer.
 - 32K RAM with address range \$2000 to \$9FFF
 - 001X, XXXX, XXXX, XXXX Range \$2000 to \$3FFF
 - 01XX, XXXX, XXXX, XXXX Range \$4000 to \$7FFF
 - 100X, XXXX, XXXX, XXXX Range \$8000 to \$9FFF

Programmable Address Decoder

  



In	M _n	A _n	V _n	Out
0	X	X	X	0
1	0	X	X	1
1	1	0	0	1
1	1	1	0	0
1	1	0	1	0
1	1	1	1	1

Timing Intervals

 

$$\begin{aligned}
 (\uparrow Y, \downarrow Y) &= (\downarrow A, \uparrow A) + 10 \\
 (\uparrow Y, \downarrow Y) &= (\downarrow A, \uparrow A) + [5, 15] \\
 (\uparrow Y, \downarrow Y) &= (\downarrow A + [8, 15], \uparrow A + [5, 12])
 \end{aligned}$$

Available and Required Time Intervals

 
 


$$\begin{aligned}
 DA &= (\downarrow G^* + [10, 20], \uparrow G^* + [0, 15]) \\
 DA &= (\downarrow G^* + 20, \uparrow G^*) \text{ worst-case} \\
 DR &= (\uparrow Clk - 30, \uparrow Clk + 5)
 \end{aligned}$$


Timing Diagrams

Symbol	Input	Output
	The input must be valid	The output will be valid
	If the input were to fall	Then the output will fall
	If the input were to rise	Then the output will rise
	Don't care, it will work regardless	Don't know, the output value is indeterminate
	Nonsense	High impedance, tristate, HiZ, Not driven, floating


Example Timing Diagrams

  


Read Cycle Circuit

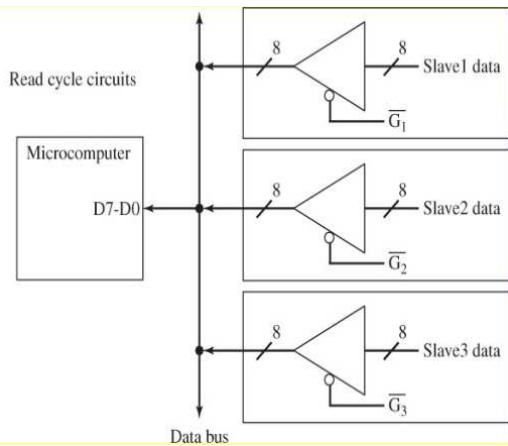


Write Cycle Circuit

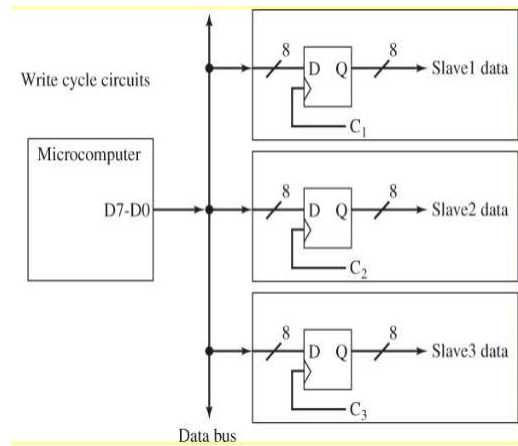


Synchronous Bus Timing

 

 
Partially Asynchronous Bus Timing (6809/680x0/x86)




Fully Asynchronous Read Cycle

 


Fully Asynchronous Write Cycle

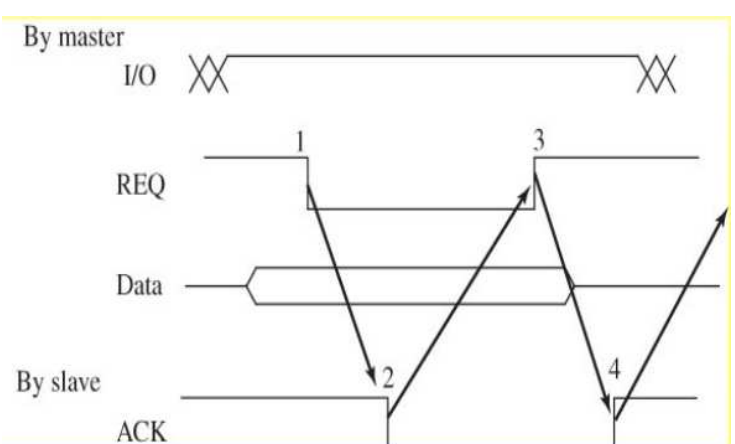

Four Types of Control Signals

 

MC9S12C32

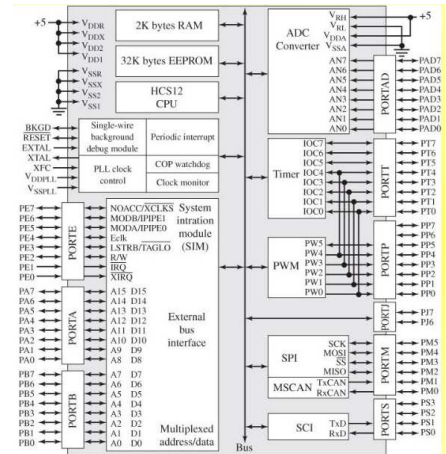


MC9S12C32 Modes of Operation

BKGD	MODB	MODA	Description	Port A	Port B	MODx write
0	0	0	Special Single chip	In/Out	In/Out	Write anytime, not peripheral
0	0	1	Emulation Exp. narrow	A15-A8/ D7-D0	A7-A0	Cannot change
0	1	0	Special test Exp. narrow	A15-A8/ D15-D8	D7-D0	Write anytime, not peripheral
0	1	1	Emulation Exp. wide	A15-A8/ D15-D8	D7-D0	Cannot change
1	0	0	Normal Single chip	In/Out	In/Out	Write once, Norm exp N/W
1	0	1	Normal Exp. narrow	A15-A8/ D7-D0	A7-A0	Cannot change
1	1	0	Peripheral	—	—	Cannot change
1	1	1	Normal Exp. wide	A15-A8/ D15-D8	A7-A0 D7-D0	Cannot change


MC9S12C32 Modes of Operation

BKGD	MODB	MODA	Description	Port A	Port B	MODx write
1	0	0	Normal Single chip	In/Out	In/Out	Write once, Norm exp N/W
1	0	1	Normal Exp. narrow	A15-A8/ D7-D0	A7-A0	Cannot change
1	1	1	Normal Exp. wide	A15-A8/ D15-D8	A7-A0 D7-D0	Cannot change


MC9S12C32 Clock Circuit

 


MC9S12C32 Expanded Mode Bus Timing

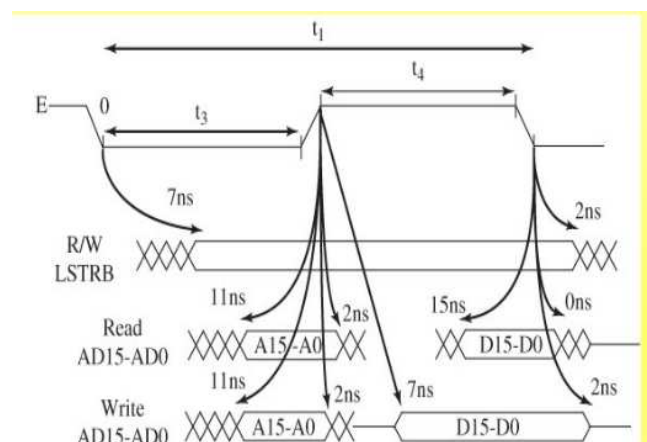


Address Latch for MC9S12C32

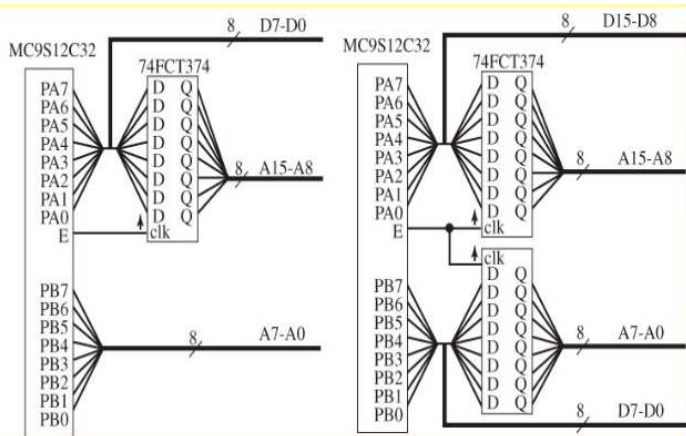


General Approach to Memory Interfacing

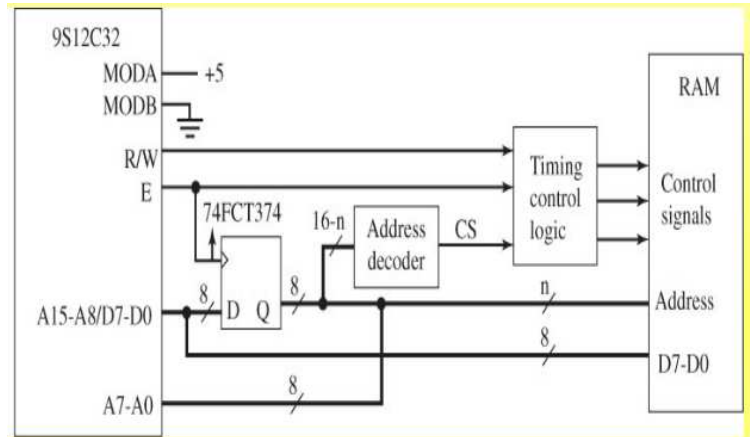


Wide Expanded Mode

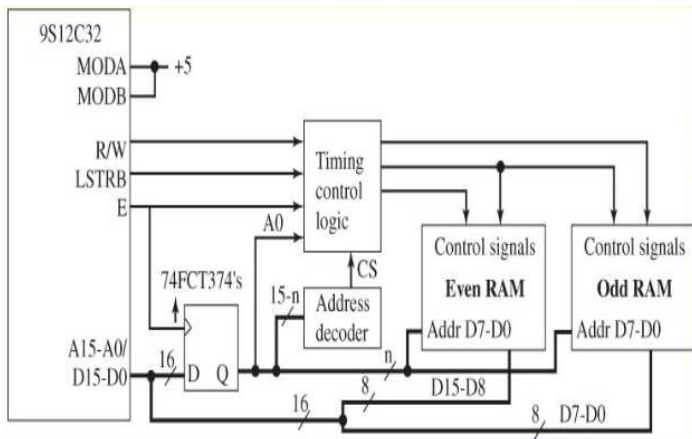

8K RAM Read Timing

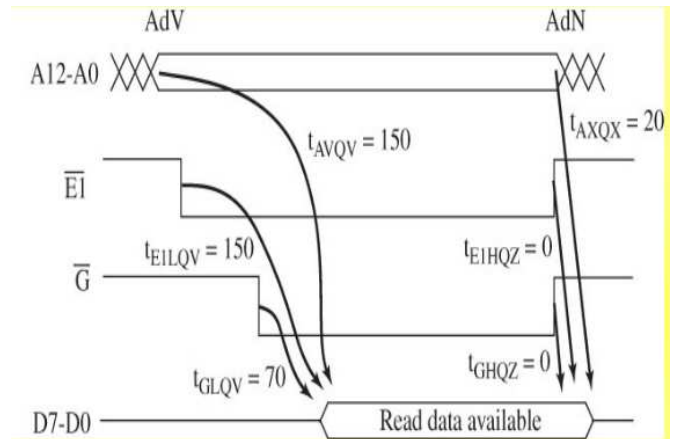

8K RAM Write Timing

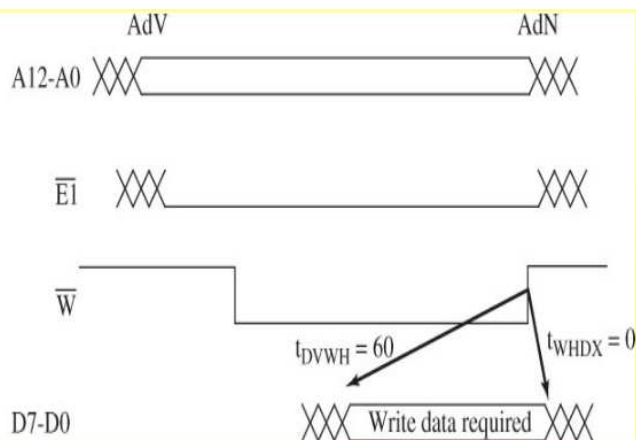

8K RAM Write Timing

