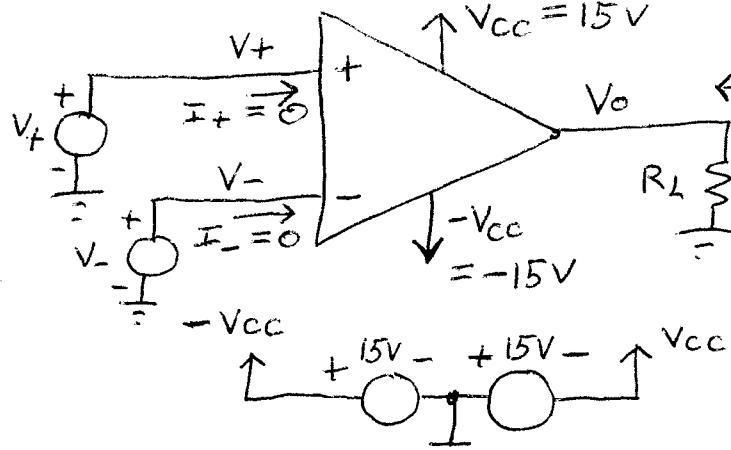


Operational Amplifier (OPAMP)

⇒ "High Gain Differential Voltage Amplifier"




"Typical" Op Amps have protective current limiting circuitry that limits I_o to:
 $-25\text{mA} < I_o < +25\text{mA}$

$$V_o = \begin{cases} -V_{cc} & \text{for } A(V_+ - V_-) \leq -V_{cc} \\ A(V_+ - V_-) & \text{for } -V_{cc} < A(V_+ - V_-) < +V_{cc} \\ +V_{cc} & \text{for } A(V_+ - V_-) \geq +V_{cc} \end{cases}$$

As long as I_o is within $(-25\text{mA}, +25\text{mA})$ current range, V_o is independent of I_o , and hence V_o is independent of the load resistance R_L .

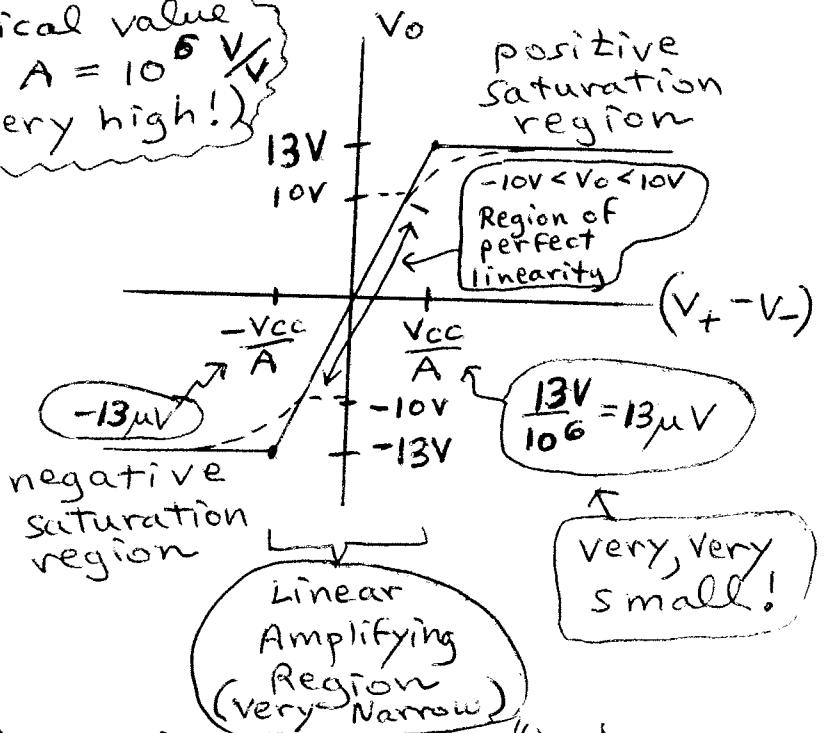
Typical value of $A = 10^6 \text{ V/V}$ (very high!)



Rule #1 of OPAMP: ("Virtual Voltage Rule") When OP AMP is operating in its linear amplifying range, $V_+ \approx V_-$, since $(V_+ - V_-)$ must lie between $+15\mu\text{V}$ and $-15\mu\text{V}$.

Rule #2 of OPAMP: No current flows into the (+) input or the (-) input of the OPAMP ($I_+ = 0, I_- = 0$)

Inverting Amplifier Configuration

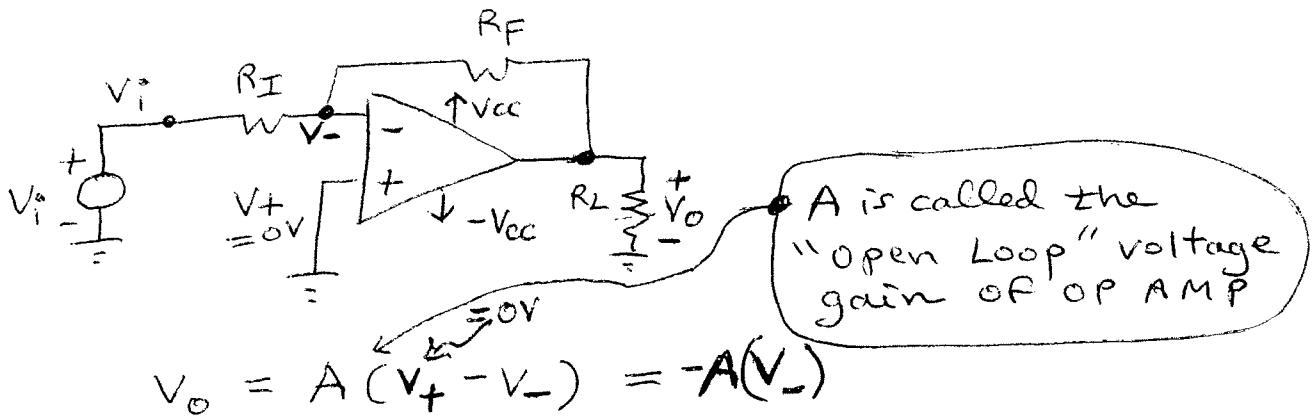

Since no current flows into (-) input of OP AMP, by linear superposition we see

$$V_- = V_i \underbrace{\frac{R_F}{R_F + R_I}}_{\substack{\text{Contribution} \\ \text{to } V_- \text{ due to} \\ V_i \text{ acting alone}}} + V_o \underbrace{\frac{R_I}{R_F + R_I}}_{\substack{\text{Contribution} \\ \text{to } V_- \text{ due to} \\ V_o \text{ acting alone}}}$$

$$V_o = -A V_i \left(\frac{R_F}{R_F + R_I} \right) - A V_o \left(\frac{R_I}{R_F + R_I} \right)$$

"Closed Loop Voltage Gain"

$$V_o \left[1 + A \left(\frac{R_I}{R_F + R_I} \right) \right] = V_i \left(-A \left(\frac{R_F}{R_F + R_I} \right) \right)$$

$$A_v \triangleq \frac{V_o}{V_i} = \frac{\left(\frac{-A R_F}{R_F + R_I} \right)}{1 + A \left(\frac{R_I}{R_F + R_I} \right)} = \frac{\left(\frac{-A R_F}{R_F + R_I} \right)}{\left(\frac{R_F + R_I + A R_I}{R_F + R_I} \right)}$$


$$A_v = \frac{-R_F}{\left(\frac{R_F + R_I}{A} \right) + R_I} \quad \text{Assuming} \quad \frac{R_F + R_I}{A} \ll R_I$$

OR Assuming $\frac{R_F + R_I}{R_I} \ll A$, $\left(\text{This assumption is usually true, since } A \approx 10^6! \right)$

$$\Rightarrow \boxed{A_v = -\frac{R_F}{R_I}}$$

Note that the closed-loop voltage gain is independent of "A" as long as A is LARGE

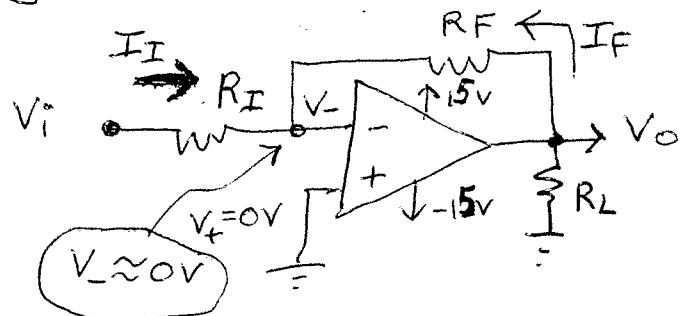The "Inverting Amplifier Configuration" closed-loop Voltage Gain is more easily calculated using the two "rules of the OP AMP":



By Rule #1 (Virtual Voltage Rule) V_- is "virtually at ground" since $V_+ \approx$ at ground.

$$\text{Thus } I_I = \frac{V_i - 0}{R_I} = \frac{V_i}{R_I}$$

But because Rule #2 says that no current can flow into the (+) terminal of the OP AMP,

$$\text{KCL} \Rightarrow I_F = -I_I = -\frac{V_i}{R_I}$$


$$\text{Thus } V_o = I_F R_F + \underbrace{V_-}_{=0V} = I_F R_F = -\frac{V_i}{R_I} R_F$$

$$\therefore \boxed{A_v \triangleq \frac{V_o}{V_i} = -\frac{R_F}{R_I}}$$

Valid while OP AMP is in its linear amplifying region while $-13V < V_o < 13V$

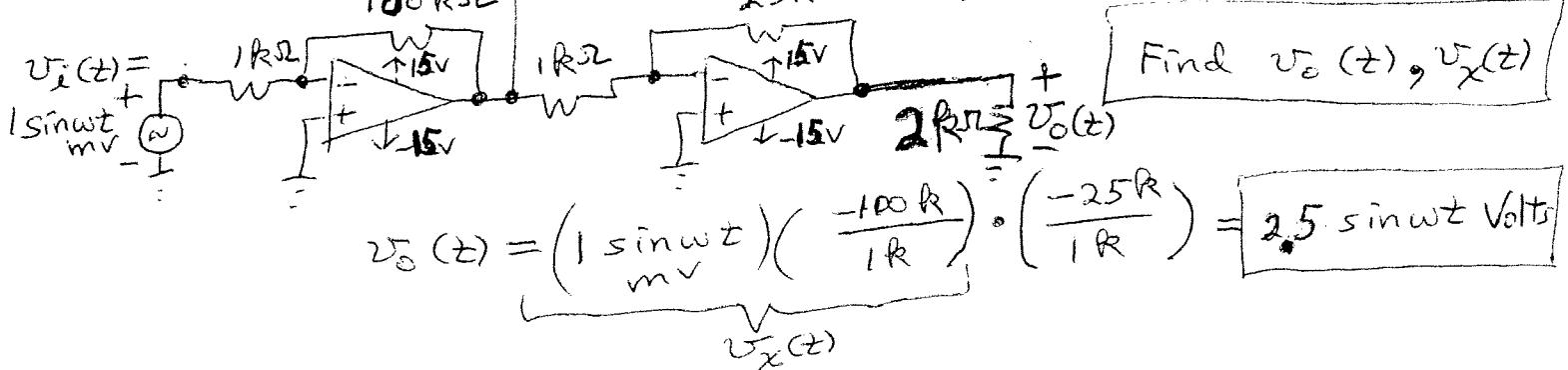Example #1

$$V_x(t) = \frac{1}{100k\Omega} \rightarrow V_x(t) = (1 \sin \omega t) \left(\frac{-100k}{1k} \right) = -0.1 \sin \omega t \text{ Volts}$$




Example #2

Now what would happen if $v_i(t)$ amplitude in EX#1 were increased to

$$v_i(t) = 10 \sin \omega t \text{ mV} ?$$

$$v_x(t) = (10 \sin \omega t) \left(\frac{-100k}{1k} \right) = -10 \sin \omega t \text{ Volts}$$

$$v_y(t) = v_x(t) \left(\frac{-25k}{1k} \right) = \begin{cases} +13V, & \text{when } 2500v_i(t) > 13V \\ +25 \sin \omega t \text{ Volts}, & |2500v_i(t)| < 13V \\ -13V, & \text{when } 2500v_i(t) < -13V \end{cases}$$

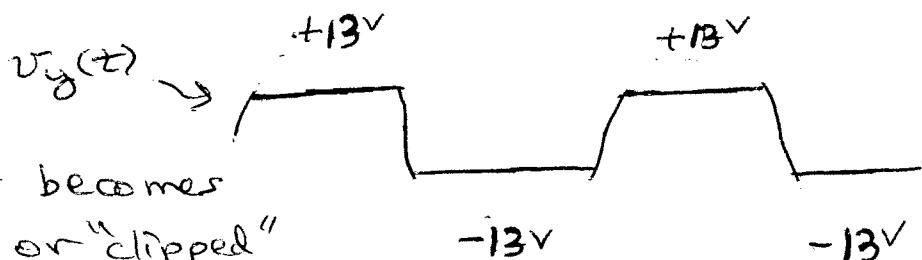

Note:


$v_y(t)$ output becomes distorted, or "clipped"

because v_i amplitude has been raised to a level that requires

$v_y(t)$ to rise above the $+13V$ limit $= V_{cc} - 2V$

Voltage and below the $-13V$ limit $= -V_{cc} + 2V$

Non-Inverting OP AMP Configuration

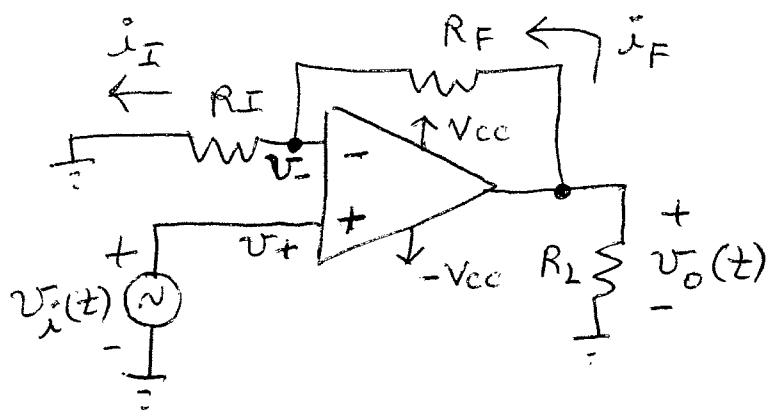

Find the closed-loop voltage gain $A_v \triangleq \frac{v_o}{v_i}$


$$v_f = v_i \Rightarrow v_- \approx v_i \quad (\text{Rule #1 OP AMP})$$

$$\therefore i_I = \frac{v_-}{R_I} = \frac{v_i}{R_I}$$

$$i_F = i_I \quad (\text{Rule #2 OP AMP}) \Rightarrow v_o = i_F R_F + v_-$$

$$\therefore v_o = \frac{v_i}{R_I} R_F + v_i \Rightarrow A_v \triangleq \frac{v_o}{v_i} = \frac{R_F + R_I}{R_I}$$

Example #1

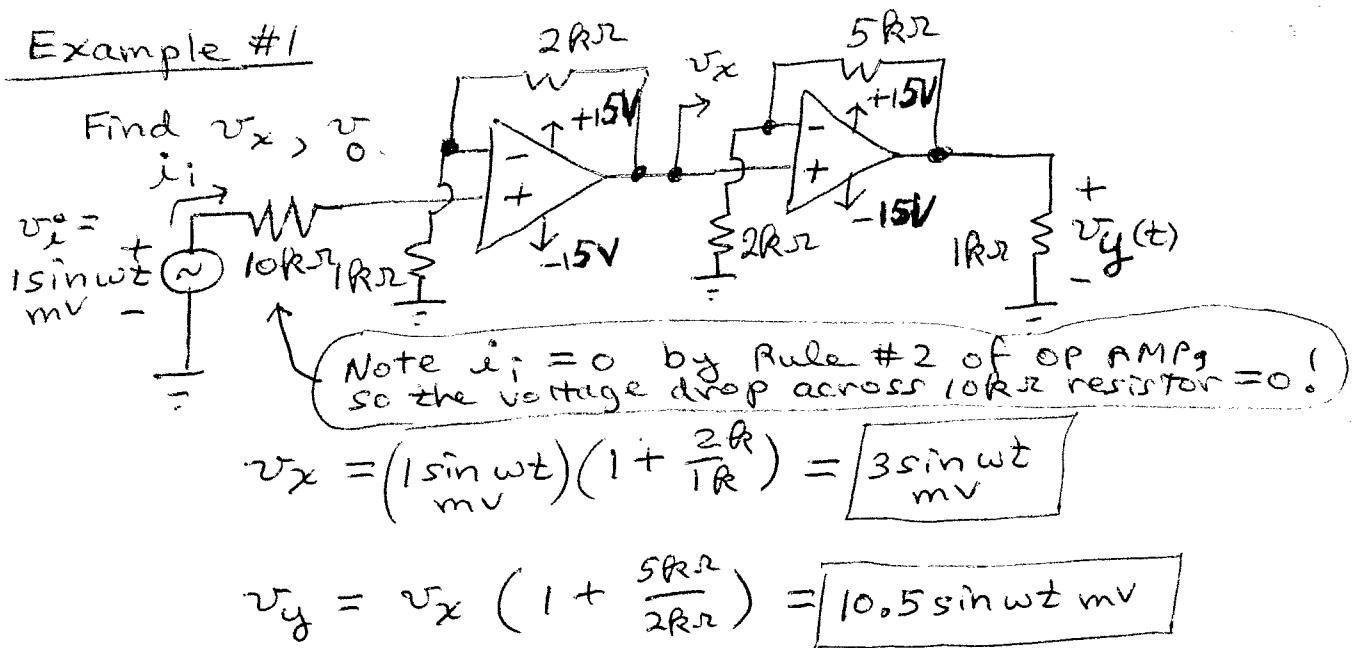

Example #2

Repeat Ex #1 if v_i were changed to $v_i = 3 \text{ V}$ (dc)

$$v_x = (3 \text{ V}) \left(1 + \frac{2k}{1k}\right) = \boxed{9 \text{ V}}$$


$$v_y = (3 \text{ V}) \left(1 + \frac{2k}{1k}\right) \left(1 + \frac{5k}{2k}\right) = 31.5 \text{ V} > 13 \text{ V}$$

$\underbrace{v_x = 9 \text{ V}}_{\rightarrow v_y = +13 \text{ V}}$

$$\Rightarrow v_y = \boxed{+13 \text{ V}}$$

positive saturation

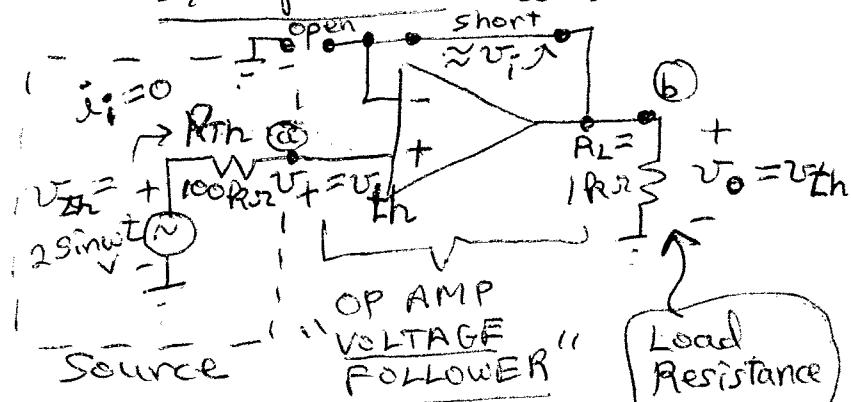Example #3 Consider Non-Inverting OP AMP with



$R_F = \infty \Omega$ (short circuit)
 $R_I = \infty \Omega$ (open circuit)


$$\Rightarrow A_v \triangleq \frac{v_o}{v_i} = \left(1 + \frac{\infty}{\infty}\right) = 1.0$$

This is called the
"Voltage follower"
configuration,

$$\text{where } v_o = v_{Th} = 2 \sin \omega t \text{ V}$$

Load
Resistance

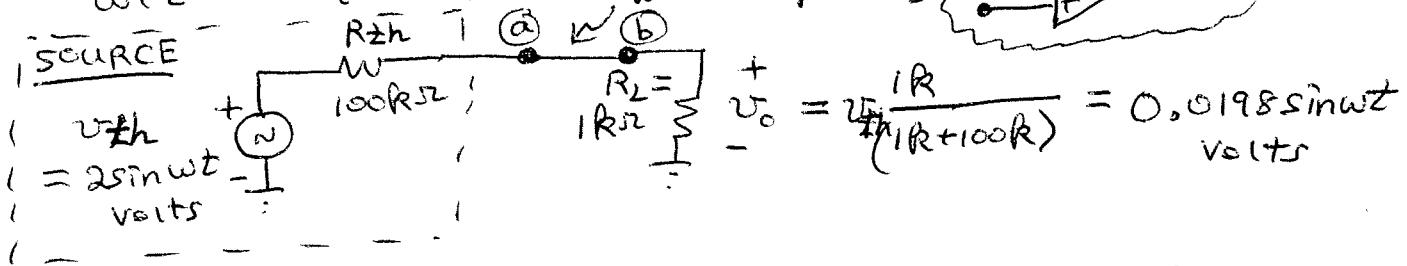
To appreciate the usefulness of the "opamp follower circuit with a voltage gain of 1.0 over a "wire", let us replace the OPAMP with a wire:



with the op amp voltage follower removed, far less signal gets delivered to the load due to the presence of the $100k\Omega$ resistor. We say that the op amp follower circuit eliminates the effects of "Loading" a source with a high Thevenin resistance when it is connected across a relatively low load resistance " R_L ".

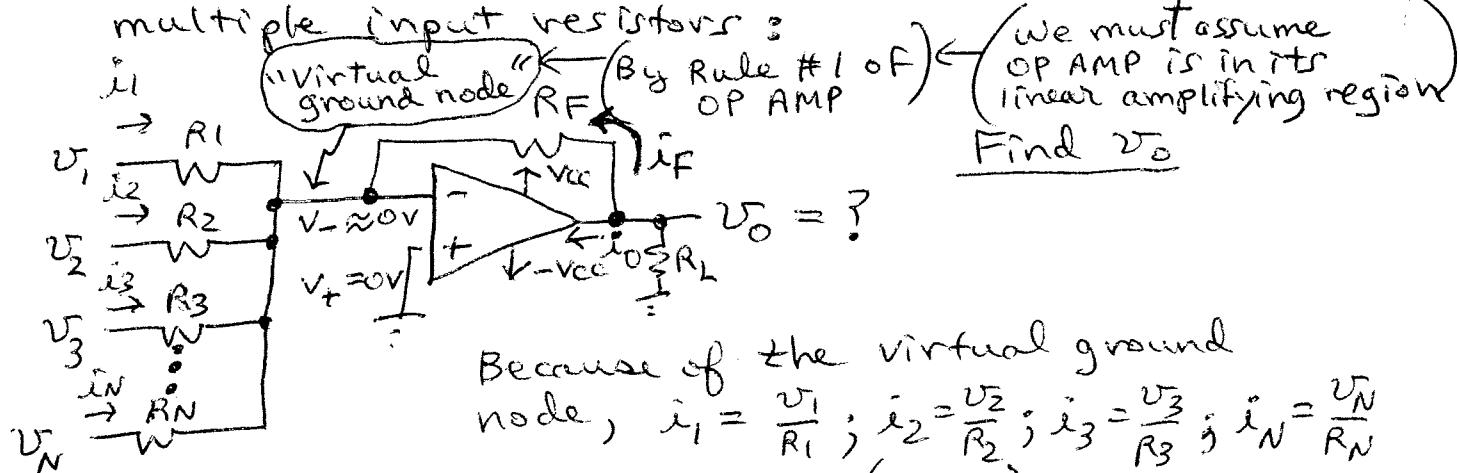Example #4 Inverting, Weighted Summing Circuit

Consider an inverting OP AMP configuration with multiple input resistors:



Because of the virtual ground node, $i_1 = \frac{v_1}{R_1}; i_2 = \frac{v_2}{R_2}; i_3 = \frac{v_3}{R_3}; \dots; i_N = \frac{v_N}{R_N}$


∴ By Rule #2 of OP AMP ($i_- = 0$)

$$KCL \Rightarrow i_F = -(i_1 + i_2 + i_3 + \dots + i_N)$$

$$\therefore v_o = i_F R_F = -\frac{R_F}{R_1} v_1 - \frac{R_F}{R_2} v_2 - \frac{R_F}{R_3} v_3 - \dots - \frac{R_F}{R_N} v_N$$


(valid as long as $|v_o| < V_{CC}/2$ and $|i_o| < 25mA$)

Difference Amplifier Circuit

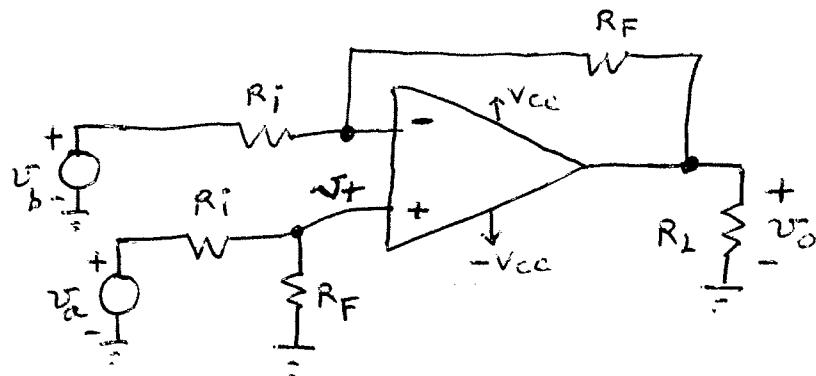

Use Linear Superposition to find v_o

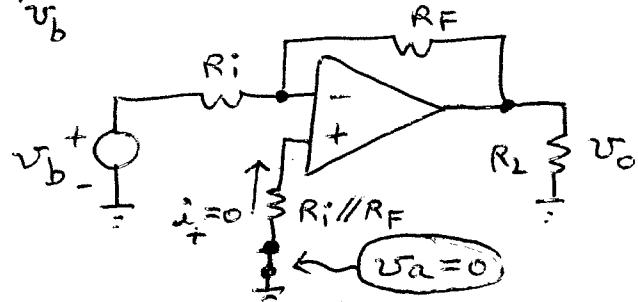[a] $(v_o)_{v_b} = ?$ Set $v_a = 0V$ (replace it by a short circuit)




The $R_i//R_F$ resistance may be replaced by a short circuit, since there is no voltage dropped across $R_i//R_F$, since $i_+ = 0$ (Rule #2 of OP AMP). Thus we have the "inverting OP AMP configuration"

and

$$(v_o)_{v_b} = v_b \left(\frac{-R_F}{R_i} \right)$$

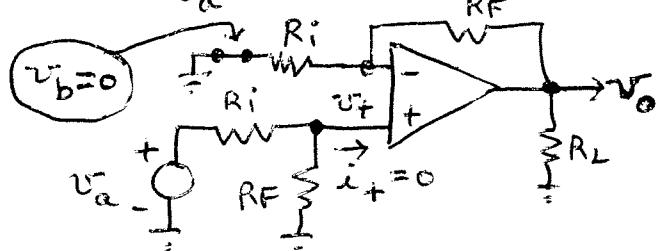[b] $(v_o)_{v_a} = ?$ Set $v_b = 0V$ (replace by a short circuit)



Because $i_+ = 0$, we may use a voltage divider eqn to find v_+ , then from v_+ to v_o , we have a "non-inverting OP AMP config."

$$v_o = \underbrace{v_a \left(\frac{R_F}{R_F + R_i} \right)}_{v_+} \cdot \left(1 + \frac{R_F}{R_i} \right) = v_a \left(\frac{R_F}{R_i} \right)$$

Thus the complete output voltage is given by

$$v_o = (v_o)_{va} + (v_o)_{vb} = \frac{R_f}{R_I} (v_a - v_b)$$

Let us define the differential voltage and the common-mode voltage as

$$v_{dm} \triangleq v_a - v_b \quad (\text{differential voltage})$$


$$v_{cm} \triangleq \frac{v_a + v_b}{2} \quad (\text{common-mode voltage})$$

Solving for v_a and v_b \Rightarrow

$$v_a = v_{cm} + \frac{1}{2} v_{dm}$$

$$v_b = v_{cm} - \frac{1}{2} v_{dm}$$

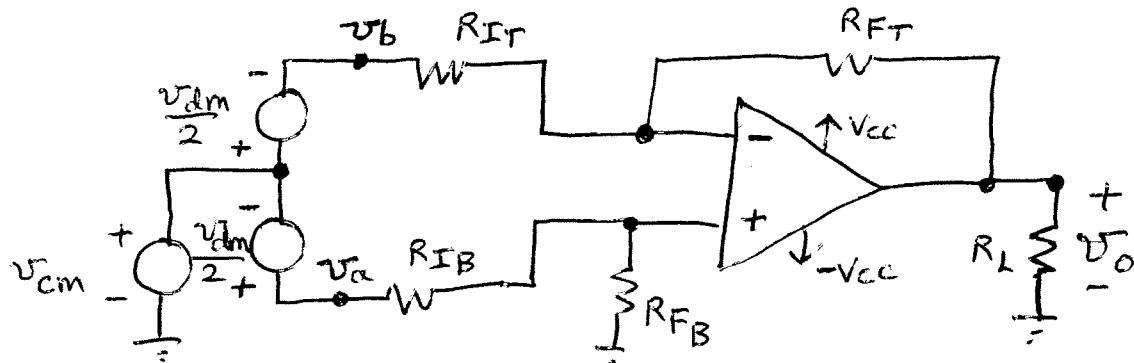Our difference amplifier may be drawn in terms of v_{dm} and v_{cm} sources instead of v_a and v_b :



Also note that the R_f & R_I resistors have been differentiated using the subscripts T (top) and B (bottom).

$$v_o = \left(v_{cm} - \frac{v_{dm}}{2}\right) \left(-\frac{R_{FT}}{R_{IT}}\right) + \left(v_{cm} + \frac{v_{dm}}{2}\right) \left(\frac{R_{FB}}{R_{FB} + R_{IB}}\right) \left(\frac{R_{FT} + R_{IT}}{R_{IT}}\right)$$

$$v_o = v_{cm} \left[\left(\frac{R_{FB}}{R_{FB} + R_{IB}} \right) \left(\frac{R_{FT} + R_{IT}}{R_{IT}} \right) - \frac{R_{FT}}{R_{IT}} \right] + v_{dm} \left[\left(\frac{R_{FB}}{R_{FB} + R_{IB}} \right) \left(\frac{R_{FT} + R_{IT}}{2R_{IT}} \right) + \frac{R_{FT}}{2R_{IT}} \right]$$

$= Av_{cm}$ (we desire this z_0 to be as close to 0 as possible!)

Av_{dm} (Typ. $\gg 1$)

If the R_I 's and R_F 's are perfectly matched

$$R_{IT} = R_{IB} = R_I; \quad R_{FT} = R_{FB} = R_F$$

then

$$v_o = v_{cm} (0) + v_{dm} \left(\frac{RF}{RI} \right)$$

$$= \frac{1}{2} (v_a + v_b)$$

$$= (v_a - v_b)$$

But if the R_I 's and R_F 's are not perfectly matched
(which is always the case in the real world)


$Av_{cm} \ll 1 \rightarrow Av_{dm}$ is usually $\gg 1$

A "Figure of merit" for a difference amplifier

$$CMRR \triangleq \left| \frac{Av_{dm}}{Av_{cm}} \right| \quad (\text{should be very large!})$$

The higher the CMRR, the better the difference amplifier is at rejecting common-mode noise.

"noise" in a circuit:

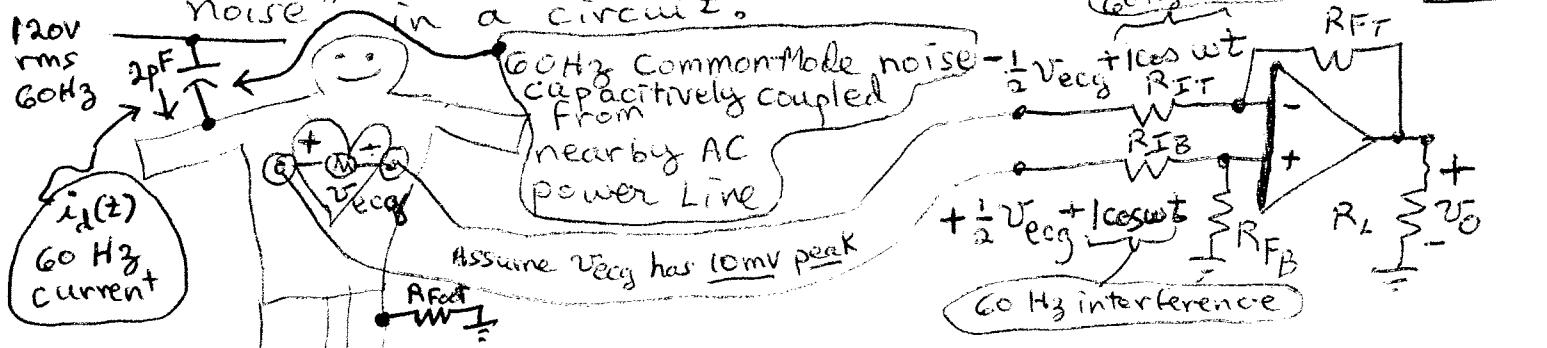

Ex #1 (Ideal Case)

Let $R_{F_T} = R_{F_B} = 100 \text{ k}\Omega$ and $R_{I_T} = R_{I_B} = 1 \text{ k}\Omega$

Then $A_{Vcm} = 0 \rightarrow A_{Vdm} = \frac{100\text{k}}{1\text{k}} = 100 \Rightarrow CMRR = \frac{100}{0}$

$$\therefore v_o = \frac{1}{2} \left(\left[\frac{v_{eg}}{2} + \cos \omega t \right] + \left[-\frac{v_{eg}}{2} + \cos \omega t \right] \right) A_{Vcm} +$$

$$CMRR = \infty$$

$$\left\{ \left[\frac{v_{eg}}{2} + \cos \omega t \right] - \left[-\frac{v_{eg}}{2} + \cos \omega t \right] \right\} A_{Vdm}$$

$$v_o = \cos \omega t \cdot A_{Vcm} + v_{eg} \cdot A_{Vdm}$$

$$v_o = \cos \omega t \cdot (0) + v_{eg} \cdot (100) = 100 v_{eg}$$

\therefore all of the interfering 60 Hz common-mode signal is rejected by OP AMP difference amplifier, while the ECG waveform is amplified by a factor of 100!

Ex #2 (Real Case)

Assume R_F 's and R_I 's are not perfectly matched

$$\text{Let } R_{F_T} = 101 \text{ k}\Omega, R_{F_B} = 99 \text{ k}\Omega$$

$$R_{I_T} = 1.1 \text{ k}\Omega, R_{I_B} = 0.9 \text{ k}\Omega$$

Find $v_o(t)$

$$A_{Vcm} = \left[\left(\frac{R_{FB}}{R_{FB} + R_{IB}} \right) \left(\frac{R_{FT} + R_{IT}}{R_{IT}} \right) - \frac{R_{FT}}{R_{IT}} \right] = 0.163$$

$$A_{Vdm} = \frac{1}{2} \left[\left(\frac{R_{FB}}{R_{FB} + R_{IB}} \right) \left(\frac{R_{FT} + R_{IT}}{R_{IT}} \right) + \frac{R_{FT}}{R_{IT}} \right] = 91.9$$

$$\Rightarrow CMRR = \frac{91.9}{0.163} = 563.8$$

$$v_o = \underbrace{\cos \omega t (0.163)}_{\text{Noise}} + \underbrace{91.9 (v_{eg})}_{\text{Signal}}$$

(If v_{eg} has 10mV peak, it is well above noise at output!)