

Homework 5

Please turn in all verilog code and a hardcopy of your simulation results. You can demonstrate proper operation by either a printout of the “monitor” output (the table printed once the simulation has been run) or by a printout of the waveforms (the results of some problems are easier to see one way and the results of other problems are easier to see another). **Be sure to annotate your simulation results telling me how your results prove that you have met all specifications.**

The Problem:

Envision a stream of 4-bit data packets that is traveling across an asynchronous channel. The source of the information has two 1-bit communication ports, **READY** and **DONE**. This configuration is illustrated in figure 1:

 


Figure 1: Interface of Stream Source Module.

When the Stream Source Module (SSM) has a new packet of data available, it asserts the active-high **READY** port. It *continues* to assert **READY** until the **DONE** port is asserted, telling the SSM that the data has been received and that it is ok to produce a new packet of data.

Your job is design, implement, and test a Stream Receiving Buffer Module (SRBM) that

- Communicates with the SSM via **READY** and **DONE**
- Stores up to two packets of data
- Outputs a stored packet of data on an output line **OUT**
- Communicates with a third device through the ports **NEW** and **UPDATE**


The SRBM asserts **DONE** when it has successfully stored the new data packet from the SSM. It outputs the next packet in sequential order of arrival on the 4-bit output **OUT**, asserting **NEW** whenever new data is available. When the third, unknown device has

collected the data from **OUT**, it will assert **UPDATE**, signaling to the SRBM that it can output the next packet of data.

Note that at any time the SRBM could be in one of the following situations:

- Both packets are stored, waiting for the third device to signal **UPDATE**
- Both packets are empty, waiting for the SSM to signal **READY**
- One packet stored, transmitting to third device while storing a second packet from the SSM
- etc.

 
1. Draw a top-level interface diagram of the SRBM



2. Divide your SRBM into two sub-units: a data partition and a controller partition
3. Outline the responsibilities of each of your two sub-units


Control Unit	Data Unit
<ul style="list-style-type: none"> • Interact with SSM via READY and DONE • Assert DONE after DATA is loaded (implies that storage had room for the new DATA) • Interact with “third device” via NEW and UPDATE • Assert NEW when a new DATA is available on OUT • Instruct Data Unit to shift when UPDATE is asserted 	<ul style="list-style-type: none"> • Store new DATA in one of two storage units • Shift DATA out when instructed by the controller

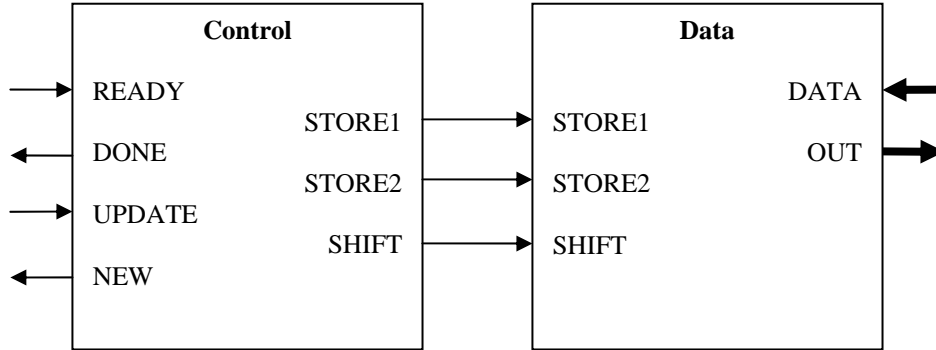4. Draw interface diagrams for each of your sub-units




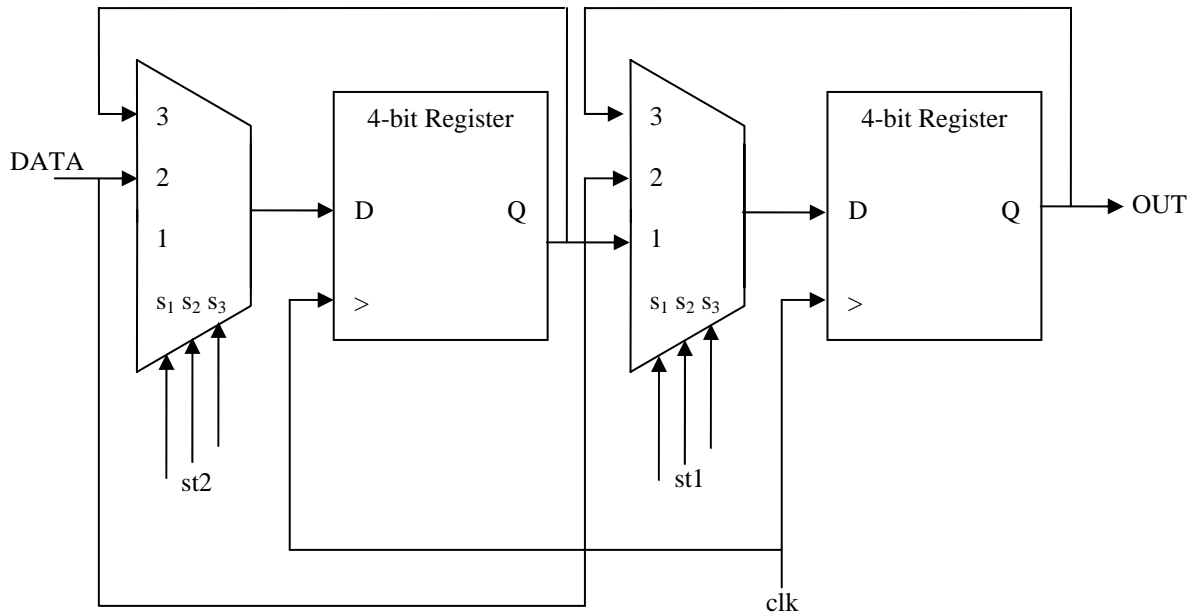5. Draw lower-middle level schematics of your sub-units. If you plan to use a finite state machine, include a block called FSM in your design – you don't have to go deeper into your schematic.

The data unit is a pair of two 4-bit registers that has shifting capability. The mux's select between feedback and data in.



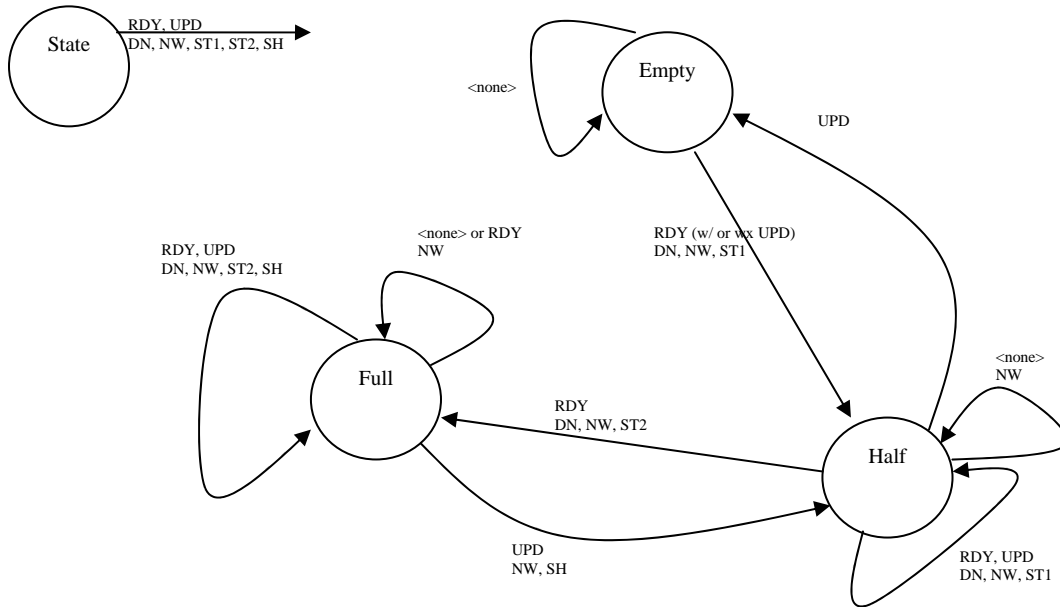The controller can be implemented with just a finite state machine. I chose a Meely machine because it has fewer states.



YOU WILL NOT RECEIVE CREDIT FOR ANY OF THE FOLLOWING PARTS IF YOU HAVE NOT FINISHED THE ABOVE PARTS

6. Implement your sub-units in Verilog. Use multi-module design whenever convenient.

srbm.v

```
module srbm( clk, reset, READY, UPDATE, DONE, NEW, DATA, OUT );

input clk, reset, READY, UPDATE;
input [3:0] DATA;

output NEW, DONE;
output [3:0] OUT;

wire [3:0] OUT;
wire STORE1, STORE2, SHIFT;

cu controller( clk, reset, READY, UPDATE, DONE, NEW, STORE1, STORE2,
SHIFT );

du datapath( clk, reset, DATA, STORE1, STORE2, SHIFT, OUT );

endmodule
```

cu.v

```
module cu( clk, reset, READY, UPDATE, DONE, NEW, STORE1, STORE2,
SHIFT );

input clk, reset, READY, UPDATE;
output DONE, NEW, STORE1, STORE2, SHIFT;

reg DONE, NEW, STORE1, STORE2, SHIFT;
reg [1:0] STATE, NEXT_STATE;

parameter EMPTY = 2'b00,
          HALF = 2'b01,
          FULL = 2'b10,
          ERROR = 2'b11;

// state register
always @ ( posedge clk, posedge reset )
  if( reset )
    STATE <= EMPTY;
  else
    STATE <= NEXT_STATE;

// next state decoder
always @ ( STATE, READY, UPDATE )
  case( STATE )
    EMPTY : if( READY )
              NEXT_STATE <= HALF;
            else
              NEXT_STATE <= EMPTY;
    HALF  : case( {READY, UPDATE} )
              2'b01 : NEXT_STATE <= EMPTY;
              2'b10 : NEXT_STATE <= FULL;
              default : NEXT_STATE <= HALF;
            endcase
    FULL  : case( {READY, UPDATE} )
              2'b01 : NEXT_STATE <= HALF;
              default : NEXT_STATE <= FULL;
            endcase
    default : NEXT_STATE <= ERROR;
  endcase

// output decoder
// (Meely, so a function of state and inputs)
always @ ( STATE, READY, UPDATE )
  case( STATE )
    EMPTY : case( {READY, UPDATE} )
              2'b10 : {DONE, NEW, STORE1, STORE2, SHIFT} = 5'b11100;
              default:{DONE, NEW, STORE1, STORE2, SHIFT} = 5'b00000;
            endcase
    HALF  : case( {READY, UPDATE} )
              2'b00 : {DONE, NEW, STORE1, STORE2, SHIFT} = 5'b01000;
              2'b01 : {DONE, NEW, STORE1, STORE2, SHIFT} = 5'b00000;
              2'b10 : {DONE, NEW, STORE1, STORE2, SHIFT} = 5'b11010;
              2'b11 : {DONE, NEW, STORE1, STORE2, SHIFT} = 5'b11100;
            endcase
  endcase
```

```
        endcase
FULL   : case( {READY, UPDATE} )
        2'b01 : {DONE, NEW, STORE1, STORE2, SHIFT} = 5'b01001;
        2'b11 : {DONE, NEW, STORE1, STORE2, SHIFT} = 5'b11011;
        default:{DONE, NEW, STORE1, STORE2, SHIFT} = 5'b01000;
        endcase
        default : {DONE, NEW, STORE1, STORE2, SHIFT} = 5'b00000;
    endcase
endmodule
```

du.v

```
module du( clk, reset, DATA, STORE1, STORE2, SHIFT, OUT );

input clk, reset, STORE1, STORE2, SHIFT;
input [3:0] DATA;

output [3:0] OUT;

reg [3:0] q2, q1, OUT, muxout1, muxout2;

always @ ( q1 )
    OUT <= q1;

// mux1
always @ ( STORE1, SHIFT, DATA, q2, q1 )
    case( {STORE1, SHIFT} )
        2'b01 : muxout1 <= q2;
        2'b10 : muxout1 <= DATA;
        default : muxout1 <= q1;
    endcase

// mux2
always @ ( STORE2, SHIFT, DATA, q2, q1 )
    casex( {STORE2, SHIFT} )
        2'b01 : muxout2 <= 4'b0000;
        2'b1x : muxout2 <= DATA;
        default : muxout2 <= q2;
    endcase

// reg1
always @ ( posedge clk, posedge reset )
    if( reset )
        q1 <= 0;
    else
        q1 <= muxout1;

// reg2
always @ ( posedge clk, posedge reset )

    if( reset )
        q2 <= 0;
    else
        q2 <= muxout2;

endmodule
```


7. Write a test-bench for your Verilog.

```
module srbm_TB;

reg clk, reset, READY, UPDATE;
wire DONE, NEW;
reg [3:0] DATA;
wire [3:0] OUT;

srbm testUnit( clk, reset, READY, UPDATE, DONE, NEW, DATA, OUT );

always #5 clk <= ~clk;

initial begin
    $shm_open( "srbm.waves" );
    $shm_probe( "AC" );

    clk = 0;
    READY = 0;
    UPDATE = 0;
    DATA = 0;
    reset = 1;

    #7          // takes it off the clock
    reset = 0;

    DATA = 5;
    READY = 1; // trace path from EMPTY to FULL through HALF

    #50
    DATA = 7; // test shifting (it should not)

    #50
    UPDATE = 1; // test shifting (it should)

    #50
    READY = 0; // should go back to empty
              // etc.

    #50
    $finish;

end

endmodule
```

8. Simulate and annotate your work.

next page

ECE 333 Winter 2004 Homework #5 Simulation

Laffien
RHIT

Notice that input changes ARE NOT ALIGNED with clock edges.

