

ECE 333

HW Set # 1

Solutions

- Given:
- Convert 23.625_{10} to binary
 - Convert 110111001.110101_2 to decimal
 - Convert $DEADBEEF_{16}$ to binary
 - Perform addition + subtraction. Are results correct?

$$\begin{array}{r} 6 \quad 0110 \\ + -3 \quad 1101 \\ \hline \end{array} \quad \begin{array}{r} -8 \quad 1000 \\ + -8 \quad 1000 \\ \hline \end{array} \quad \begin{array}{r} +3 \quad 0011 \\ - -4 \quad 1100 \\ \hline \end{array} \quad \begin{array}{r} -3 \quad 1101 \\ - -4 \quad 1100 \\ \hline \end{array}$$

Solution: 23.625

A. $23/2 = 11 \text{ r } 1$

$11/2 = 5 \text{ r } 1$

$5/2 = 2 \text{ r } 1$

$4/2 = 2 \text{ r } 0$

$2/2 = 1$

$$\boxed{10111.101_2}$$

$.625 - \frac{1}{2}(1) = .125$

$.125 - \frac{1}{4}(0) = .125$

$.125 - \frac{1}{8}(1) = 0$

B. 110111001.110101_2


$$1 \cdot 1 + 0 \cdot 2 + 0 \cdot 4 + 1 \cdot 8 + 1 \cdot 16 + 1 \cdot 32 + 0 \cdot 64 + 1 \cdot 128 + 1 \cdot 256 = 441$$

$$1 \cdot \frac{1}{2} + 1 \cdot \frac{1}{4} + 0 \cdot \frac{1}{8} + 1 \cdot \frac{1}{16} + 0 \cdot \frac{1}{32} + 1 \cdot \frac{1}{64} = .828125$$

$$\boxed{441.828125_{10}}$$

Problem 1.1 cont'd solutions

C. DEADBEEF₁₆

 

D.

$$\begin{array}{r}
 6 \quad 0110 \\
 + -3 \quad 1101 \\
 \hline
 \overset{c.o.}{\leftarrow} 110011
 \end{array}$$

carry-out is same as carry-in to last bit
Correct

$$\begin{array}{r}
 \overset{\leftarrow \text{carry-in}}{1} \\
 -8 \quad 1000 \\
 + -8 \quad 1000 \\
 \hline
 110000
 \end{array}$$

carry-out is 1, carry-in to last bit is 0, overflow (-16 cannot be shown with 4-bits).
incorrect

$$\begin{array}{r}
 3 \quad 0011 \\
 - -4 \quad 1100 \\
 \hline
 01011
 \end{array}
 \xrightarrow{\text{2's comp.}}
 \begin{array}{r}
 0011 \\
 + 0100 \\
 \hline
 01011
 \end{array}$$




carry-out is 0, same as carry-in to last bit
correct

$$\begin{array}{r}
 -3 \quad 1101 \\
 - -4 \quad 1100 \\
 \hline
 11001
 \end{array}$$


carry-out is 1, same as carry-in
correct

A. $F(A, B, C) = A'B'C + A'BC' + AB'C' + ABC$

A	B	C	F
0	0	0	0
0	0	1	1
0	1	0	1
0	1	1	0
1	0	0	1
1	0	1	0
1	1	0	0
1	1	1	1

   

 Draw the output waveform for the circuit below. The reference grid in the timing diagram is one line per 10 units. Considering 10 units=2 seconds what is the clock period of signal A (T_A), signal B (T_B) and Signal C (T_C). What is the frequency of signal A?



$$T_A = 160 \text{ units} \left(\frac{2 \text{ s}}{10 \text{ units}} \right) = \frac{32 \text{ s}}{64}$$

$$T_B = 80 \text{ units} \left(\frac{2 \text{ s}}{10 \text{ units}} \right) = \frac{16 \text{ s}}{32}$$

$$T_C = 40 \text{ units} \left(\frac{2 \text{ s}}{10 \text{ units}} \right) = \frac{8 \text{ s}}{16}$$

$$f_A = \frac{1}{T_A} = \frac{64}{32 \text{ s}} = 2 \text{ Hz}$$

$$= 0.56 \text{ Hz}$$

Problem 1,2 cont'd Solutions

B. Convert $Z(A, B, C) = A'(B+C) + B'(A+C)$ to Minterm canonical form

$$= A'B + A'C + AB' + B'C'$$

$$= A'B(C+C') + A'(B+B')C + AB'(C+C') + (A+A')B'C'$$

$$= \underset{2}{A'B C} + \underset{2}{A'B C'} + \overset{\text{Dup.}}{\cancel{A'B C}} + \underset{1}{A'B C'} + \underset{5}{A B C} + \underset{4}{A B C'} + \overset{\text{Dup.}}{\cancel{A B C}} + \overset{\text{Dup.}}{\cancel{A B C}}$$

$$\boxed{\Sigma(1, 2, 3, 4, 5)}$$


C. Write compliment of $\Sigma(0, 1, 4, 8, 13, 15)$ in maxterm form

include all elements not used in minterm form

$$\cancel{\Pi(2, 3, 5, 6, 7, 9, 10, 11, 12, 14)}$$

$$\Pi(0, 4, 8, 13, 15)$$

 A. Convert $\Sigma(0, 2, 3, 4, 6, 9, 10, 12, 14)$ to minimal and/or logic




$$A'B'D' + A'CB' + \underline{AB'C'D} + BC'D' + \underline{CD'}$$

$$CD' + CB'A' + AC'D' + BC'D' + AB'C'D$$


$$AB'C'D + A'B'C + AD + BD' + CD'$$

 B. $Z(A, B, C) = \Sigma(1, 3, 4, 6, 7)$


implement hazard-free form in NAND-NAND form



 
$$((A'C)' \cdot (B \cdot C)' \cdot (A \cdot B)' \cdot (A \cdot C)')'$$



 C. $Z = \Sigma(2, 3, 6, 7, 12, 13, 15)$ convert to NOR-NOR



 
$$((A + C)' + (A' + B)' + (A' + C' + D)')$$



20-100 30 SHEETS
 20-140 100 SHEETS
 20-141 200 SHEETS
 CAMTEC

 
A. (5 points) Implement the logic function $Z(A, B, C) = A'(B+C) + B'(A+C)$ using the 3 to 8 decoder shown below. C is the most significant selection bit of the decoder. Use additional gates if necessary.



B. Multiplexer does not have enough inputs to directly connect 1's and 0's to it's inputs. Simplify. use f, g, h as selection, and then e or e' as input.


f	g	h	e	e'
0	0	0	1	0
0	0	1	0	1
0	1	0	0	1
0	1	1	1	0
1	0	0	0	1
1	0	1	1	0
1	1	0	1	0
1	1	1	0	1

 choose e or e' where function should be 1




e	f	g	h	f
0	0	0	0	1
0	0	0	1	0
0	0	1	0	0
0	0	1	1	1
0	1	0	0	0
0	1	0	1	1
0	1	1	0	1
0	1	1	1	0
1	0	0	0	0
1	0	0	1	1
1	0	1	0	1
1	0	1	1	0
1	1	0	0	1
1	1	0	1	0
1	1	1	0	0
1	1	1	1	1

 C. (5 points) Make the necessary connections to the 74LS163 counter to operate in the free running mode (from 0 to 15 and back). The 74LS163 is a synchronous 4 bit binary counter. It has P and T inputs which enable counting when high, a clock input, a parallel load input (D-A) which is used when the LOAD input is low and a the clock The clear input loads zero into the counter and is also synchronous and active low. The RCO output goes high when the output is 15. The outputs, QD-QA, reflect the state of the counter.



 D. (5 points) Use the 74LS194 to build a basic Johnson counter. An n-bit shift register with the complement of the serial output fed back into the serial input is a counter with 2n states and is called twisted ring, Moebius or Johnson counter. The universal register 74LS94 uses a clock input, an active low clear input and two mode inputs. The modes are S1S0=00, hold, S1S0=01 shift right (toward D), S1S0=10 shift left (toward A) and S1S0=11, parallel load. R is the serial input for right shift and L is the serial input for left shift.




11-514270
20-5142 100-514270
22-5142 200-514270

CAMRY 7

Problem 5 (20 points) (5 points)

 A. (7.5 points) Analyze the following circuit. Write the excitation and output equations, fill in the transition table and draw a state diagram for the state machine shown below. You may ignore the set and reset inputs for the purpose of your state diagram.



Excitation Equations

state 1

$$Q_1 = (x \cdot Q_0)$$

state 0

$$Q_0 = (x)$$

Output Equations

$$out = (Q_0 \cdot Q_1')$$


$Q_1 = \text{state 1}$

$Q_0 = \text{state 0}$

transition table

state Q_1, Q_0	input x	Next state Q_1^*, Q_0^*
0 0	0	0 0
0 0	1	0 1
0 1	0	0 0
0 1	1	1 1
1 0	0	0 0
1 0	1	0 1
1 1	0	0 0
1 1	1	1 1


State Diagram

 

B. Design a synchronous 0-7 binary counter using JK Flip-Flops

J	K	Q_n
0	0	hold
0	1	reset
1	0	reset
1	1	change

JK Flip-Flops operate on falling edge of clock cycle so we can simply hook them up like this:

 


Problem 1.5 control

Solutions

C.

combinations of last 2 inputs:

00	state A
01	state B
10	state C
11	state D

 

100 S 15017
 22-172 100 S 15015
 22-172 100 S 15015

22-172 100 S 15015
 22-172 100 S 15015