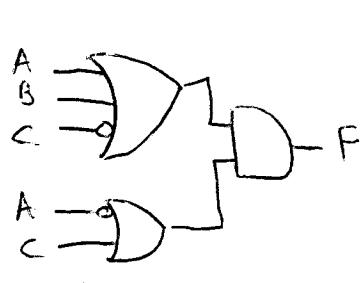



Homework 7

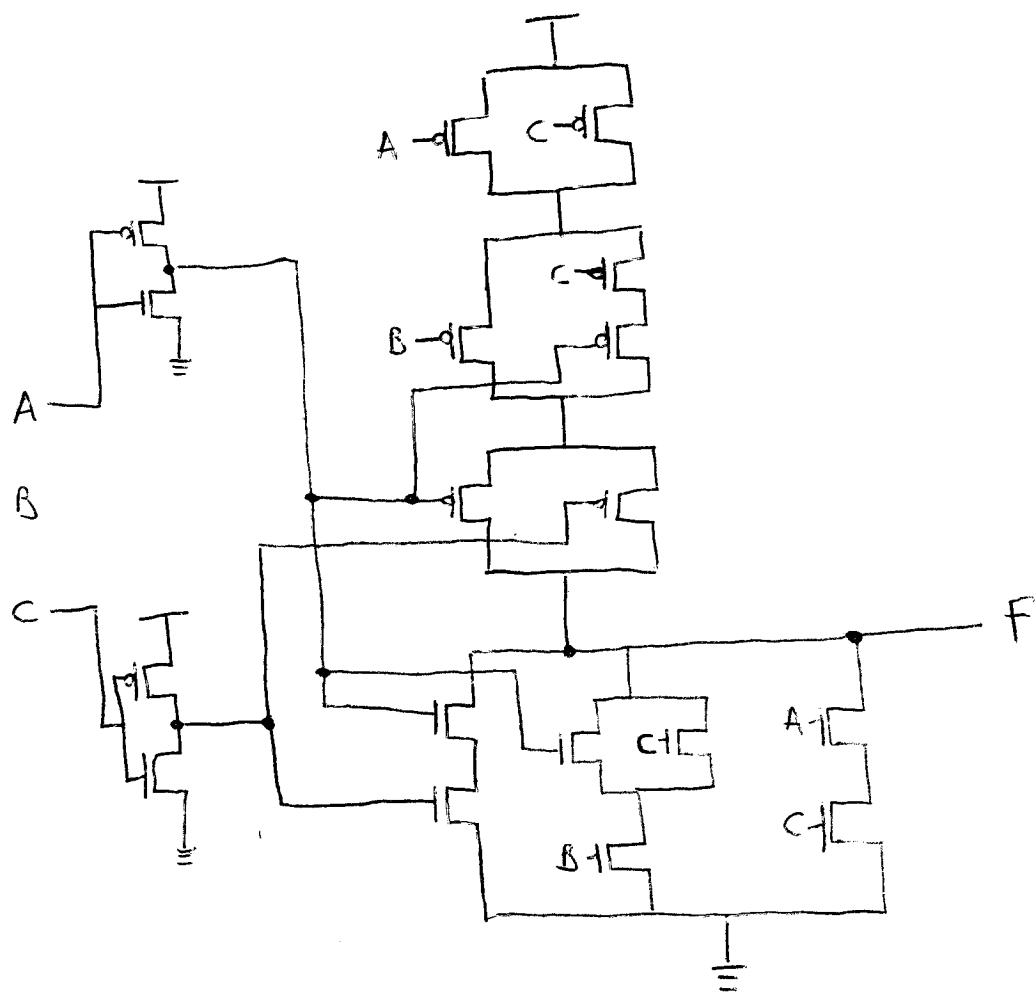(1) Implement the following Boolean expression in a CMOS circuit. Remember that a CMOS circuit contains equal numbers of p-FETs and n-FETs. Also, in this circuit you do not have access to the complements of variables – only the non-complemented variables are inputs.

$$F = (A + B + C')(A' + C)$$




$$\begin{aligned}
 &= AA' + AC + B\bar{A} + BC + \bar{C}\bar{A} + \cancel{C}\cancel{C} \\
 &= AC + \bar{A}\bar{C} + \bar{A}B + BC \\
 &= AC + \bar{A}\bar{C} + B(\bar{A} + C)
 \end{aligned}$$




(2) Consider the following circuit:

V_{dd}

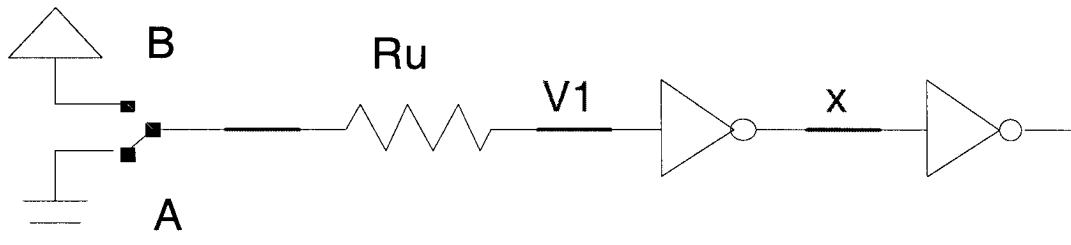

The switch changes from A to B at time $t = 0$.

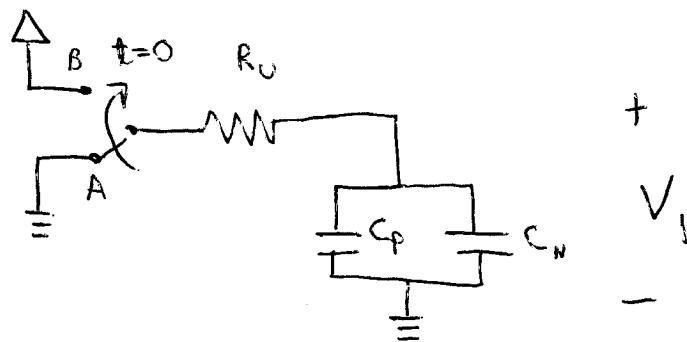
Draw a circuit diagram that illustrates the connection of the switch to the input of the first inverter. Assume that pFETs have an input capacitance of C_p and nFETs have an input capacitance of C_n .




Solve your circuit for the input voltage, V_1 , as a function of time. Use the constants V_{dd} , R_u , C_n , and C_p in your equation.

$$V_1 = V_{dd} \left(1 - e^{-\frac{t}{R_u(C_n + C_p)}} \right)$$

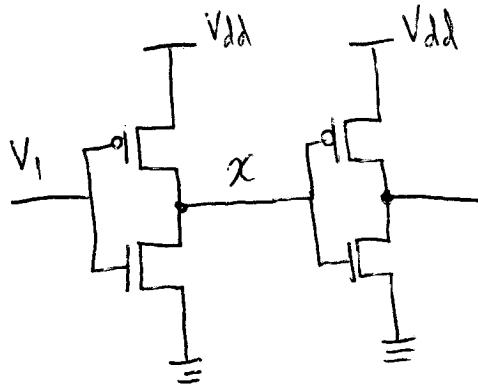Draw a circuit (transistor) level diagram for the two inverters using nFETs, pFETs, source voltage (V_{dd}), and ground.



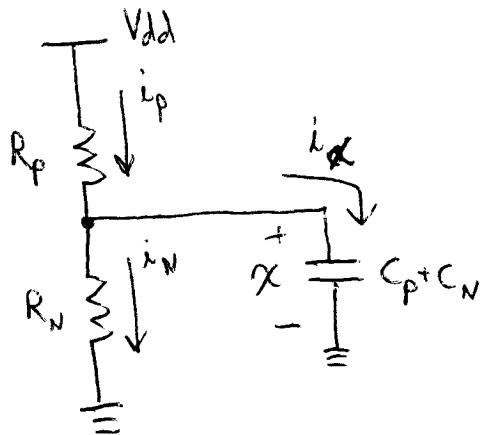Replace the pFET transistors in the first inverter with resistors with resistance R_p . Replace the nFET transistors in the first inverter with resistors with resistance R_N . Finally, replace the pFET transistors in the second inverter with capacitances C_p and the nFET transistors in the second inverter with capacitances C_N . Draw the resulting circuit below.




From your circuit, write a differential equation for x , the output voltage, as a function of V_{dd} , R_p , R_N , C_N , and C_p . **Do not solve this equation.**

$$i_p = i_x + i_N \quad i_x = (C_p + C_N) \frac{dx}{dt} \quad i_N = \frac{x}{R_N} \quad i_p = \frac{V_{dd} - x}{R_p}$$

$$\frac{V_{dd} - x}{R_p} = (C_p + C_N) \frac{dx}{dt} + \frac{x}{R_N}$$

$$(C_p + C_N) \frac{dx}{dt} + x \left(\frac{1}{R_N} + \frac{1}{R_p} \right) = \frac{V_{dd}}{R_p}$$

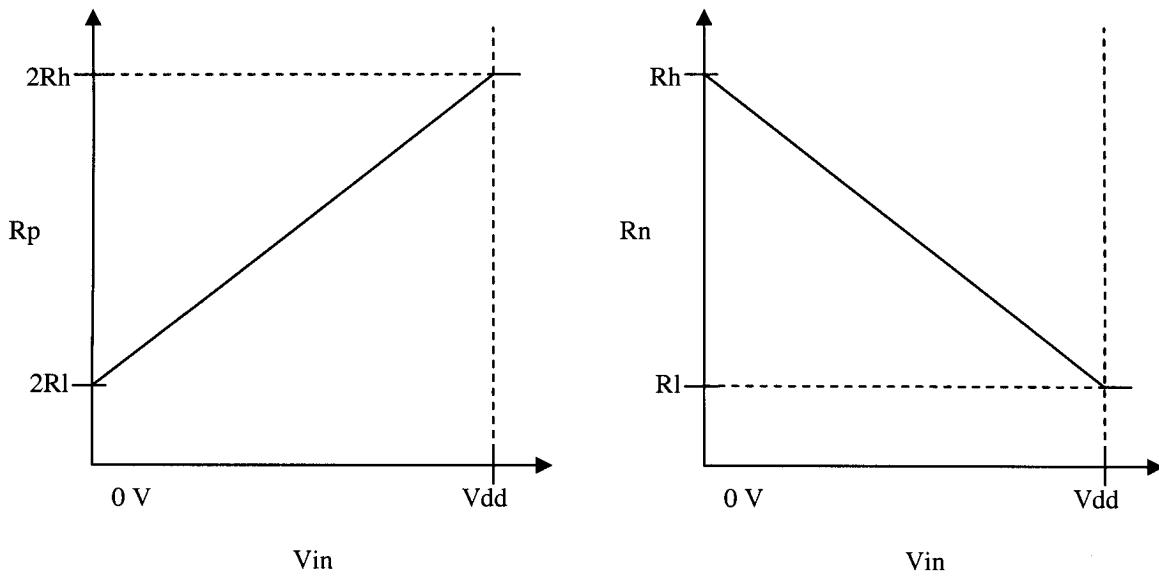Assume a linear model for the transistor resistances based on the input voltage:



Derive equations for R_p and R_n in terms of V_{in} , V_{dd} , R_h , and R_l .

$$R_p = 2R_L + \frac{2R_h - 2R_L}{V_{dd}} V_{in}$$

$$R_n = R_h + \frac{R_L - R_h}{V_{dd}} V_{in}$$

Substitute your equation for V_1 from above as the input voltage to your equations for R_p and R_n . Now you have a model of the resistance as a function of time based on the initial switching event.

$$R_p = 2R_L + 2(R_h - R_L) \left(1 - e^{-\frac{t}{R_o(C_N + C_P)}} \right)$$

$$R_n = R_h + (R_L - R_h) \left(1 - e^{-\frac{t}{R_o(C_N + C_P)}} \right)$$

Use your equations for R_p and R_n as functions of time in conjunction with your above differential equation to produce PLOTS of the output voltage x and the associated output current. Also generate a plot of instantaneous power consumption, the product of voltage and current.

For these plots use the following constants:

$V_{dd} = 5V$
 $R_h = 1 M\Omega$
 $R_l = 10 \Omega$
 $R_u = 200 \Omega$
 $C_n = C_p = 200 pF$

You do not need to solve the equations to produce these plots. Be creative and use whatever software you like.

Matlab code:

```
% ECE 333, Winter 2004
% Homework #7 Problem #2

clear all;
close all;

Vdd = 5;
Rh = 1e6;
Rl = 10;
Ru = 200;
Cn = 200e-12;
Cp = Cn;

T = 1e-6;
N = 1e4;
t = linspace( 0, T, N );

V1 = Vdd * ( 1 - exp( - t / ( Ru * ( Cn + Cp ) ) ) );

figure;
plot( t, V1 );
title( 'input voltage' );
xlabel( 'time (s)' );
ylabel( 'voltage (V)' );

Rp = 2*Rl + 2*(Rh-Rl)/Vdd*V1;
Rn = Rh + (Rl-Rh)/Vdd*V1;

figure;
plot( t, Rp, t, Rn );
title( 'effective FET resistances' );
xlabel( 'time (s)' );
```

```

ylabel( 'resistance (\omega)' );
legend( 'R_p', 'R_N' );

x = zeros( size(t) );
dx = zeros( size(t) );
x(1) = Vdd;

for m = 2:N
    dx(m) = (Vdd/Rp(m-1) - x(m-1)*(1/Rn(m-1)+1/Rp(m-1)))/(Cp+Cn)*T/N;
    x(m) = x(m-1) + dx(m);
end

figure;
plot( t, x );
title( 'output voltage, x' );
xlabel( 'time (s)' );
ylabel( 'voltage (V)' );

figure;
plot( t, -dx*(Cp+Cn)/T*N );
title( 'negative output current, C dx/dt' );
xlabel( 'time (s)' );
ylabel( 'current (A)' );

figure;
plot( t, -dx*(Cp+Cn).*x/T*N );
title( 'instantaneous power output' );
xlabel( 'time (s)' );
ylabel( 'power (W)' );

iN = x./Rn;
iP = (Vdd-x)./Rp;

figure;
plot( t, abs(iN.*x)+abs(iP.*(Vdd-x)) );
title( 'total instantaneous power consumption (source to ground)' );
xlabel( 'time (s)' );
ylabel( 'power (W)' );

```

