

- 1 Draw the output waveforms of signals in the circuit below by hand. The grid interval is 10 time units. Notice the gate delays. You may check using LogicWorks, however what you turn in must be what you did by hand before check. Include a signed statement that the work you turn in is your by hand work.

