

Rose-Hulman Institute of Technology
Electrical and Computer Engineering


EC 332 - Exam 1

Thursday, December 19th, 2002

CLOSED BOOK. Work each problem in the space provided on its sheet. Be sure the work you present is clear so I can understand what you have done. You may use one 3" by 5" card of notes. No other aids, animate or inanimate, are permitted. Please do your own work.

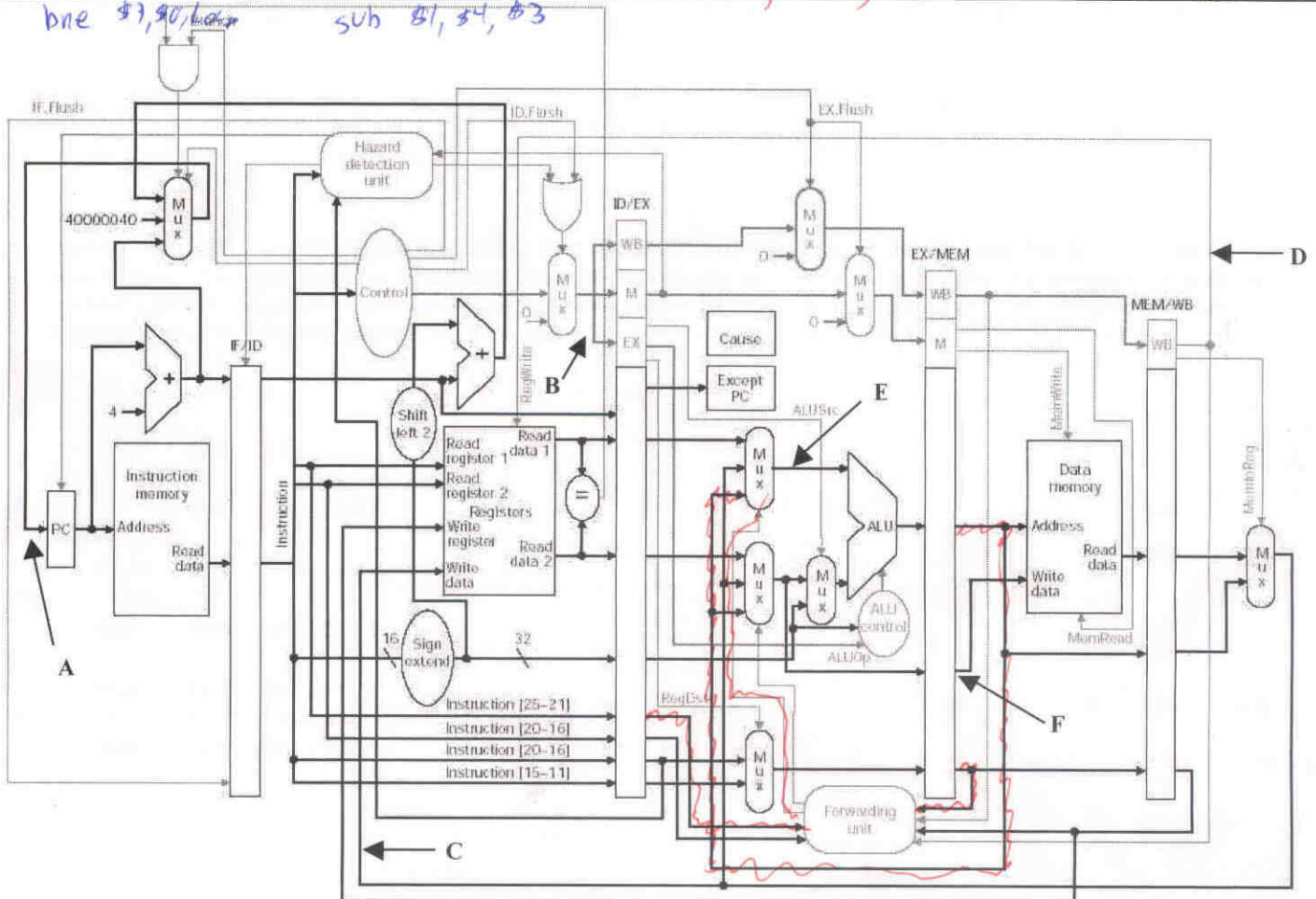Problem 1 [25 points] - The code below is to be run on the pipelined datapath shown below. Assume the datapath has hardware support for forwarding and the branch operation is performed in the Decode stage. Also, a register can be written and read during the same clock cycle.

IF: sub \$1, \$4, \$3 ID: EX: lw \$4, 10(\$2) MEM: sw \$3, 10(\$2) WB: add \$2, \$3, \$1



Show the state of the datapath for the following code sequence when the first **add** instruction is in the **WB** stage by filling the slots below with the values for the indicated lines. If you do not know the value of the signal, use the notation **\$X** to indicate the contents of register **X** and **M(\$X)** to indicate the contents of memory location **X**. Assume the "zero" input to all MUXs is the upper input. **Be sure to write the instruction above each stage.**

```

PC
A00h      li      $1, 8
A004h     li      $2, 5
A008h     li      $3, 1
A00Ch     Loop:  add  $2, $3, $1
A010h     sw      $3, 10($2)
A014h     lw      $4, 10($2)
A018h     sub     $1, $4, $3
A01Ch     bne    $3, $0, Loop
    
```

3 pts. A. A018h C 20
 B. 0 sub
 C. \$2 = 9
 D. Regwrite = 1
 E. \$2 = 9
 F. \$3 = 1
 10(\$2)


-1 if value not shown

4 pts each

Problem 3 [25 points] - Short Answer.

 a) Describe how a Combined Predictor works.

It used 2 predictors and notes which one works best.
It uses the best predictor.



b) Why does a Combined Predictor get better performance than non-combined predictors?

It can pick uses the best of the non-combined predictors.

c) Given the pipelined MIPS implementation, a friend suggest adding dynamic branch prediction to speed things up. Is this a good idea? Explain.

No. There is only 1 delay slot, so the extra hardware won't help.

d) According to Keith Diefendorff in *PC Processor Microarchitecture*, what is the biggest performance obstacle? Why?

Memory Speed.


e) For gshare, which of these stores only the global history?

- a. GR
- b. PC
- c. $GR \oplus PC$
- d. Counts table

f) For gshare, which of these stores the local history, but not the global?

- a. GR
- b. PC
- c. $GR \oplus PC$
- d. Counts table

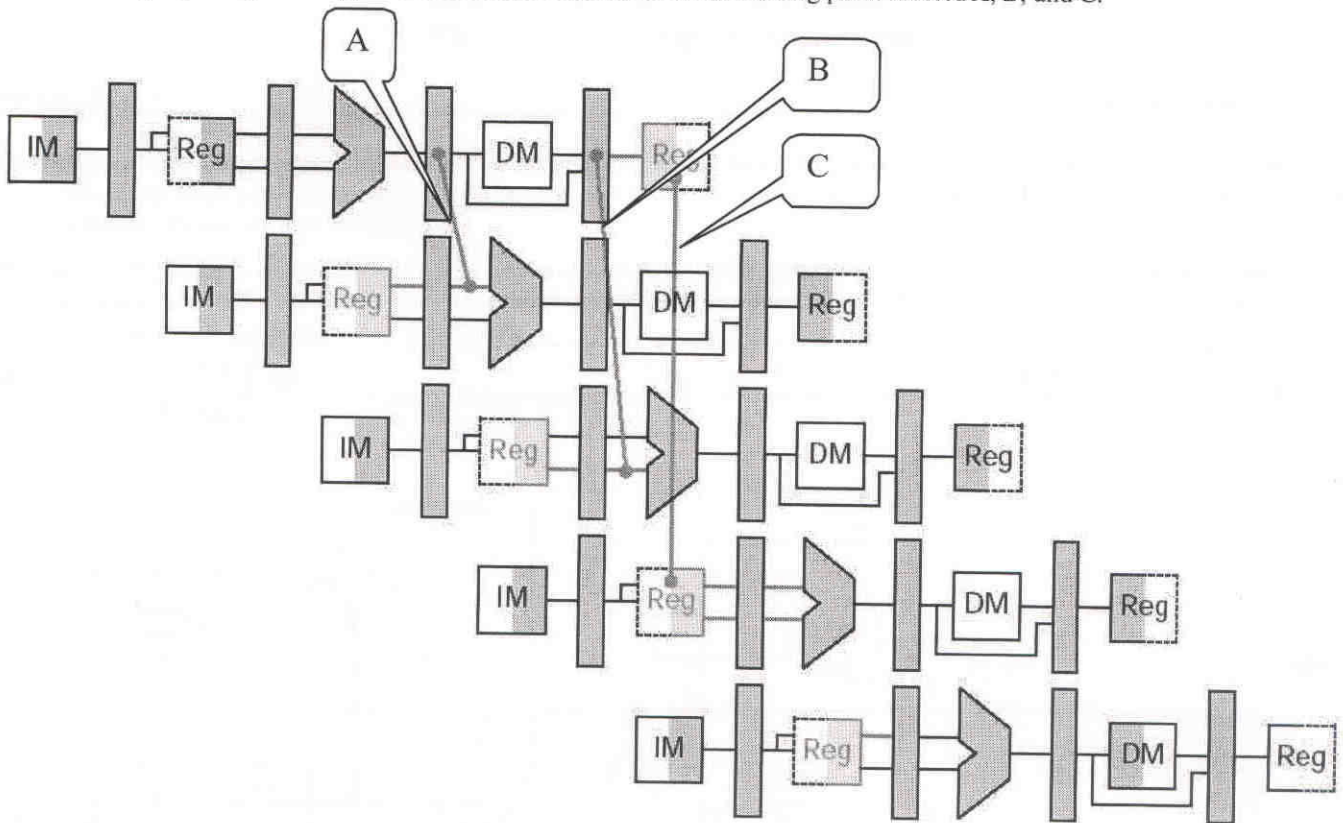Problem 4 [25 points] - The figure below shows three different forwarding paths labeled A, B, and C.



a. On the datapath on page 1, highlight the hardware and the signal lines that are used for the forwarding path A.

b. What is necessary for forwarding path C to work?

*Write Reg #10/2 half of cycle
Read Reg #6 second half of cycle*

c. Below is some control logic for handling the forwarding. Give a code sequence that will satisfy the forward logic below and cause the data to be forwarded to the first input of the ALU.

```

If (MEM/WB.RegisterRd
and (MEM/WB.RegisterRd ≠ 0)
and (EX/MEM.RegisterRd ≠ ID/EX.RegisterRs)
and (MEM/WB.RegisterRd = ID/EX.RegisterRs)) forwardA = 01
    
```

*add \$1, \$1, \$1 add \$1, x, x
sub \$2, \$1, \$1 sub \$1, x, x
add \$3, \$1, \$1 add x, \$1, x*

d. In the forwarding control logic above, why is the line “and (EX/MEM.RegisterRd ≠ ID/EX.RegisterRs)” needed?

*So this → add \$1, x, x will work right. i.e. sub is forwarded,
sub \$1, y, y not first add.
add z, \$1, w*